## **VE215 Fall 2017**

## Lab 1: DC Lab

## **Data Sheet**

Name:		Studer	Student ID:		
Lab Date:		TA Sign	TA Signature:		
				Table	
	1. Measuremer	nt of voltage, current	, and resistance.		
Resistance $[\Omega]$		1	. () 5.0		
Voltage (m) [V]		Vol			
Current (m) [A]		Cur	Current (s) [A]		
	Table 2. Volt	tage division and cu	rrent division.		
Resistance R1 $[\Omega]$		Resis	tance R2 [Ω]		
	Voltage	Voltage Division		Current Division	
	Current [A]	Voltage [V]	Current [A]	Voltage [V]	
Total					
R1					
R2					
		Table 3. Ohm's law			
Resis					
Voltage [V]			Current [A	\]	
	0.5 1.0				
3.0 4.0					
	5.0				
	Table	e4. Semiconductor	diodes		
Voltage [V]			Current [A]		