

Ve215 Electric Circuits

Sung-Liang Chen

Fall 2017

Chapter 14

Frequency Response

14.1 Introduction


In our sinusoidal steady-state analysis, we have learned how to find voltages and currents in a circuit with a constant $\omega = \omega_0$ frequency source. If we let the amplitude and phase angle of the sinusoidal source remain constant and vary the frequency, $f(\omega)$ we obtain the circuit's *frequency response*.

The frequency response may be regarded as a complete description of the sinusoidal steady-state behavior of a circuit as a function of frequency.

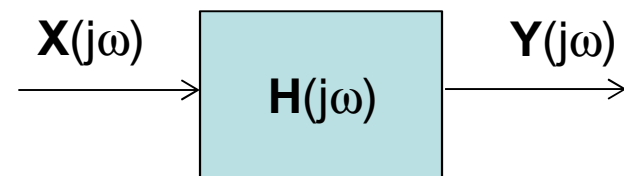14.2 Frequency Response

The frequency response $H(j\omega)$ of a circuit is the frequency-dependent ratio of a phasor output $Y(j\omega)$ (an element voltage or current) to a phasor input $X(j\omega)$ (source voltage or current).

$$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)}$$



There are four types of frequency response:

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} \quad (\text{Voltage gain})$$

$$H(j\omega) = \frac{I_o(j\omega)}{I_i(j\omega)} \quad (\text{Current gain})$$

$$H(j\omega) = \frac{V_o(j\omega)}{I_i(j\omega)} \quad (\text{Transfer impedance})$$

$$H(j\omega) = \frac{I_o(j\omega)}{V_i(j\omega)} \quad (\text{Transfer admittance})$$

The frequency response can be expressed in terms of its numerator polynomial $N(j\omega)$ and denominator polynomial $D(j\omega)$ as

$$H(j\omega) = \frac{N(j\omega)}{D(j\omega)} = \frac{\sum_{m=0}^M b_m (j\omega)^m}{\sum_{n=0}^N a_n (j\omega)^n}$$

Proof :

A linear network can be described by a linear constant-coefficient differential equation

$$\sum_{n=0}^N a_n \frac{d^n y(t)}{dt^n} = \sum_{m=0}^M b_m \frac{d^m x(t)}{dt^m}$$

Recall Chaps. 7 and 8:
First-order circuit
Second-order circuit

Transform the equation to the phasor domain,

$$\sum_{n=0}^N a_n (j\omega)^n Y(j\omega) = \sum_{m=0}^M b_m (j\omega)^m X(j\omega)$$

Recall Chap. 9:
 $d/dt \rightarrow j\omega$

$$Y(j\omega) \sum_{n=0}^N a_n (j\omega)^n = X(j\omega) \sum_{m=0}^M b_m (j\omega)^m$$

$$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)} = \frac{\sum_{m=0}^M b_m (j\omega)^m}{\sum_{n=0}^N a_n (j\omega)^n}$$

E.g., Section 8.5 series RLC

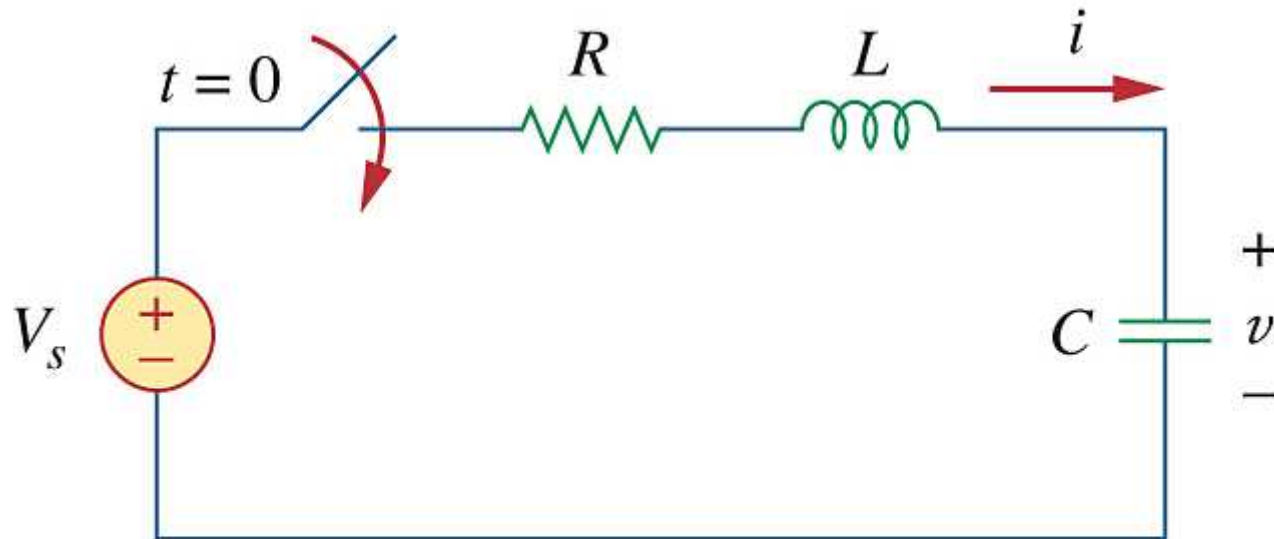


Figure 8.18 Step voltage applied to a series RLC circuit.

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} V_s$$

$$a_2 y'' + a_1 y' + a_0 y = b_0 x$$

V_s as the input
 v as the output (response)

Being a complex quantity, $H(j\omega)$ has a magnitude and a phase; that is, $H(j\omega) = H \angle \phi$. The plot of H versus ω is called the *magnitude frequency response*. The plot of ϕ versus ω is called the *phase frequency response*.

$$\mathbf{H(j\omega)=H(\omega)\angle\phi(\omega)}$$

$H(\omega)$: magnitude frequency response

$\phi(\omega)$: phase frequency response

Example 14.1 For the RC circuit in Fig. 14.2(a), obtain the frequency response $V_o(\omega) / V_s(\omega)$. Let $v_s = V_m \cos \omega t$.

Solution :

voltage division

$$H(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)} = \frac{1 / (j\omega C)}{R + 1 / (j\omega C)}$$

$$= \frac{1}{1 + j\omega RC}$$

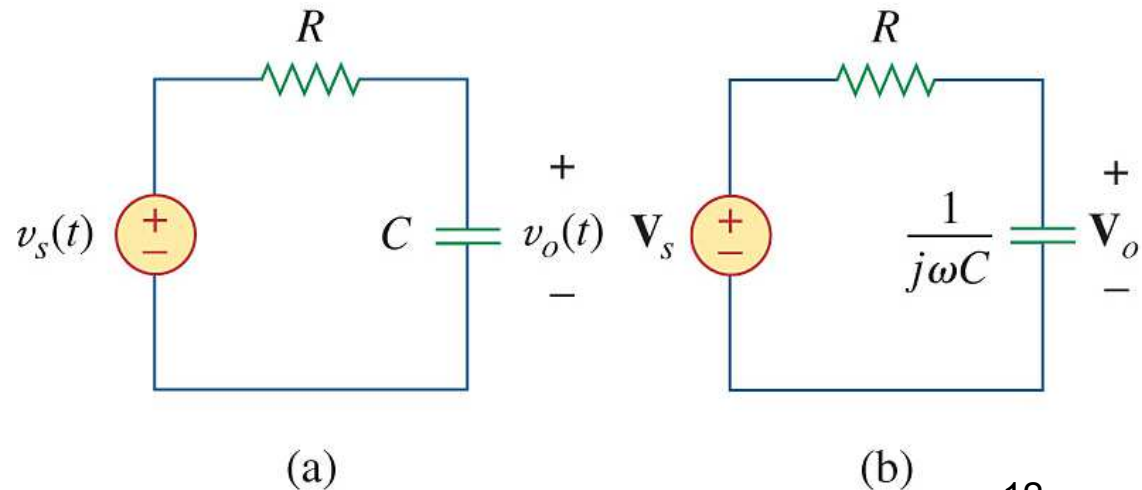


Figure 14.2

The magnitude and phase frequency responses are

$$H = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (\omega / \omega_0)^2}}$$

$$\phi = -\tan^{-1}(\omega RC) = -\tan^{-1}(\omega / \omega_0)$$

where $\omega_0 = \frac{1}{RC}$.

$$H = N/D$$

$$\angle H = \angle N - \angle D$$

$$H = \text{Re} + j \times \text{Im}$$

$$\angle H = \tan^{-1}(\text{Im}/\text{Re})$$

The plots of H and ϕ are shown in Fig. 14.3.

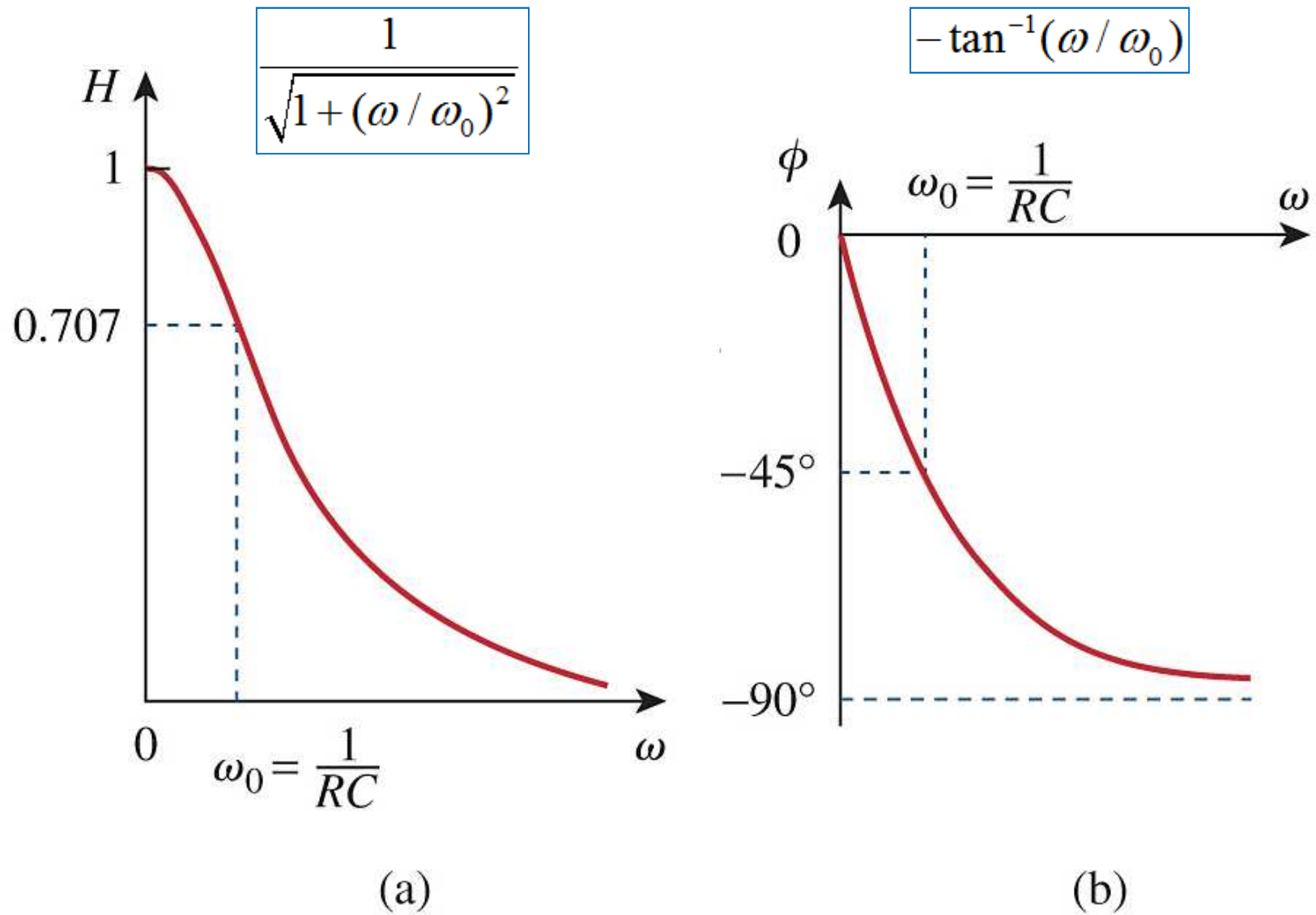


Figure 14.3 Frequency response of the RC circuit:
 (a) amplitude response, (b) phase response.


14.3 The Decibel Scale

In communication systems, gain is measured in bels. Historically, the *bel* is used to measure the ratio of two levels of power or power gain G ; that is,

$$G = \text{Number of bels} = \log_{10} \frac{P_2}{P_1}$$

$10^{G_{\text{bel}}} = \text{linear scale}$
E.g.,
0 bel \Leftrightarrow 1 time
1 bel \Leftrightarrow 10 times
2 bels \Leftrightarrow 100 times
...

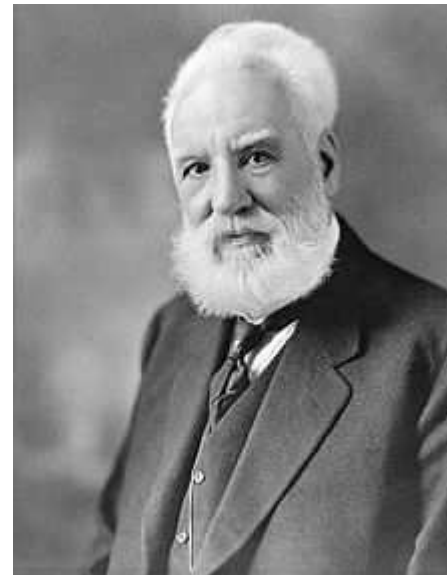Alexander Graham Bell (March 3, 1847 – August 2, 1922) was an eminent scientist, inventor, engineer and innovator who is credited with inventing the first practical telephone.



The *decibel* (dB) provides us with a unit of less magnitude. It is 1/10th of a bel and is given by

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1}$$

$10^{G_{\text{bel}}}$ = linear scale

E.g.,

0 bel \Leftrightarrow 1 time

1 bels \Leftrightarrow 10 times

2 bels \Leftrightarrow 100 times

...

$10^{G_{\text{dB}}/10}$ = linear scale

E.g.,

0 dB \Leftrightarrow 1 time


10 dB \Leftrightarrow 10 times


20 dB \Leftrightarrow 100 times

...

The gain G can be expressed in terms of voltage or current ratio. Consider the network shown in Fig. 14.8. If V_1 is the input voltage, V_2 is the output voltage, R_1 is the input resistance, and R_2 is the load resistance, then
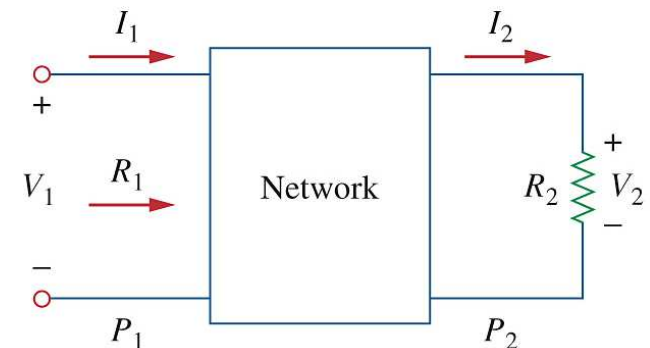
$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \left(\frac{V_2^2 / R_2}{V_1^2 / R_1} \right)$$



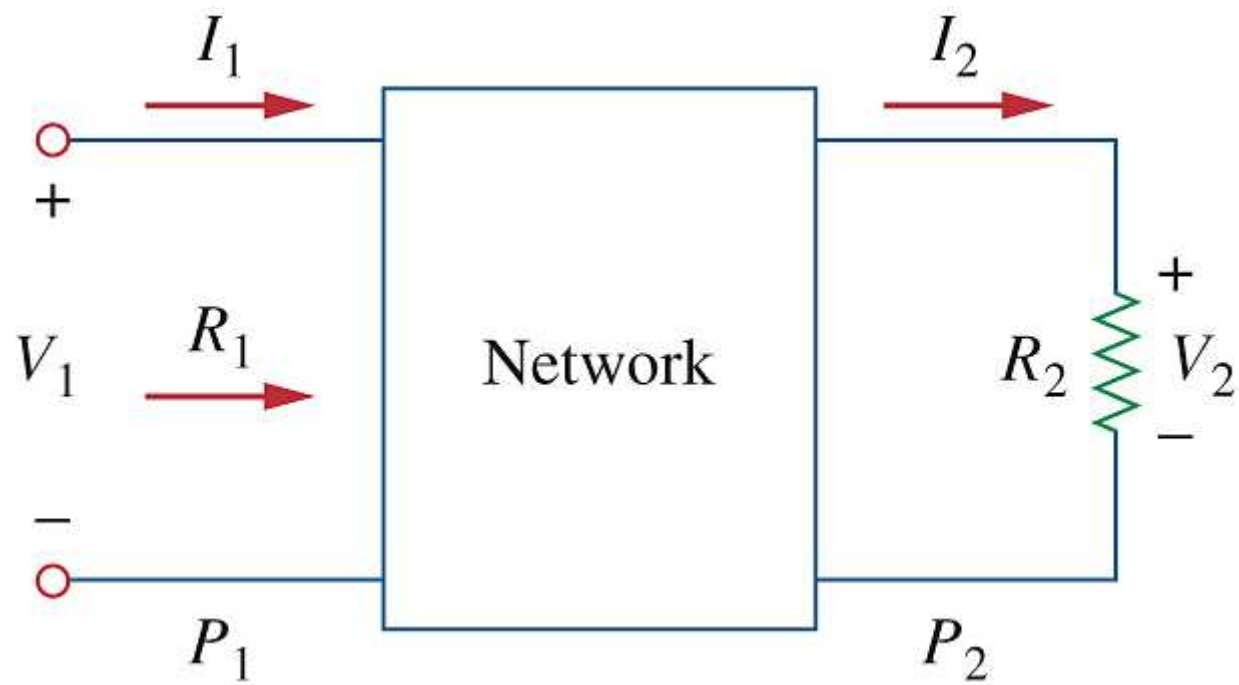


For the case when $R_2 = R_1$, a condition that is often assumed when comparing voltage levels,

$$G_{dB} = \underline{10} \log_{10} \left(\frac{V_2}{V_1} \right)^2 = \boxed{20} \log_{10} \frac{V_2}{V_1}$$

Similarly, for $R_1 = R_2$,
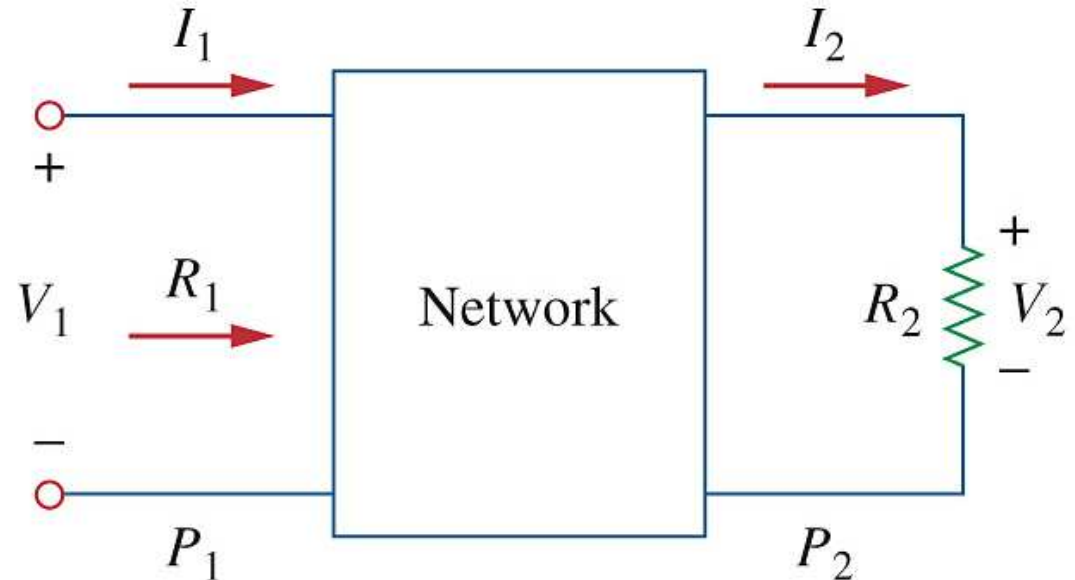
$$G_{dB} = 20 \log_{10} \frac{I_2}{I_1}$$



For power

$10^{G_{\text{dB}}/10}$ = linear scale

E.g.,

0 dB $\Leftrightarrow P_2/P_1=1$ time

10 dB $\Leftrightarrow P_2/P_1=10$ times

20 dB $\Leftrightarrow P_2/P_1=100$ times

...

Power \sim amplitude²

For amplitude (voltage/current)

$10^{G_{\text{dB}}/20}$ = linear scale

E.g.,

0 dB $\Leftrightarrow P_2/P_1=1$ time $\Leftrightarrow V_2/V_1=1$ time

10 dB $\Leftrightarrow P_2/P_1=10$ times $\Leftrightarrow V_2/V_1=(10)^{0.5}$ time= 3.16 times

20 dB $\Leftrightarrow P_2/P_1=100$ times $\Leftrightarrow V_2/V_1=10$ times


...

When we are talking about dB, we do not need to specify power or amplitude.
E.g., -3 dB means 0.5 times in power, and ~0.7 times in amplitude

14.4 Bode Plots

The frequency range required in plotting frequency response is often so wide that it is inconvenient to use a linear scale for the frequency axis. *Bode plots* are semilog plots in which the magnitude in decibels is plotted against the logarithm of the frequency, the phase in degrees is plotted against the logarithm of the frequency.

Bode plots

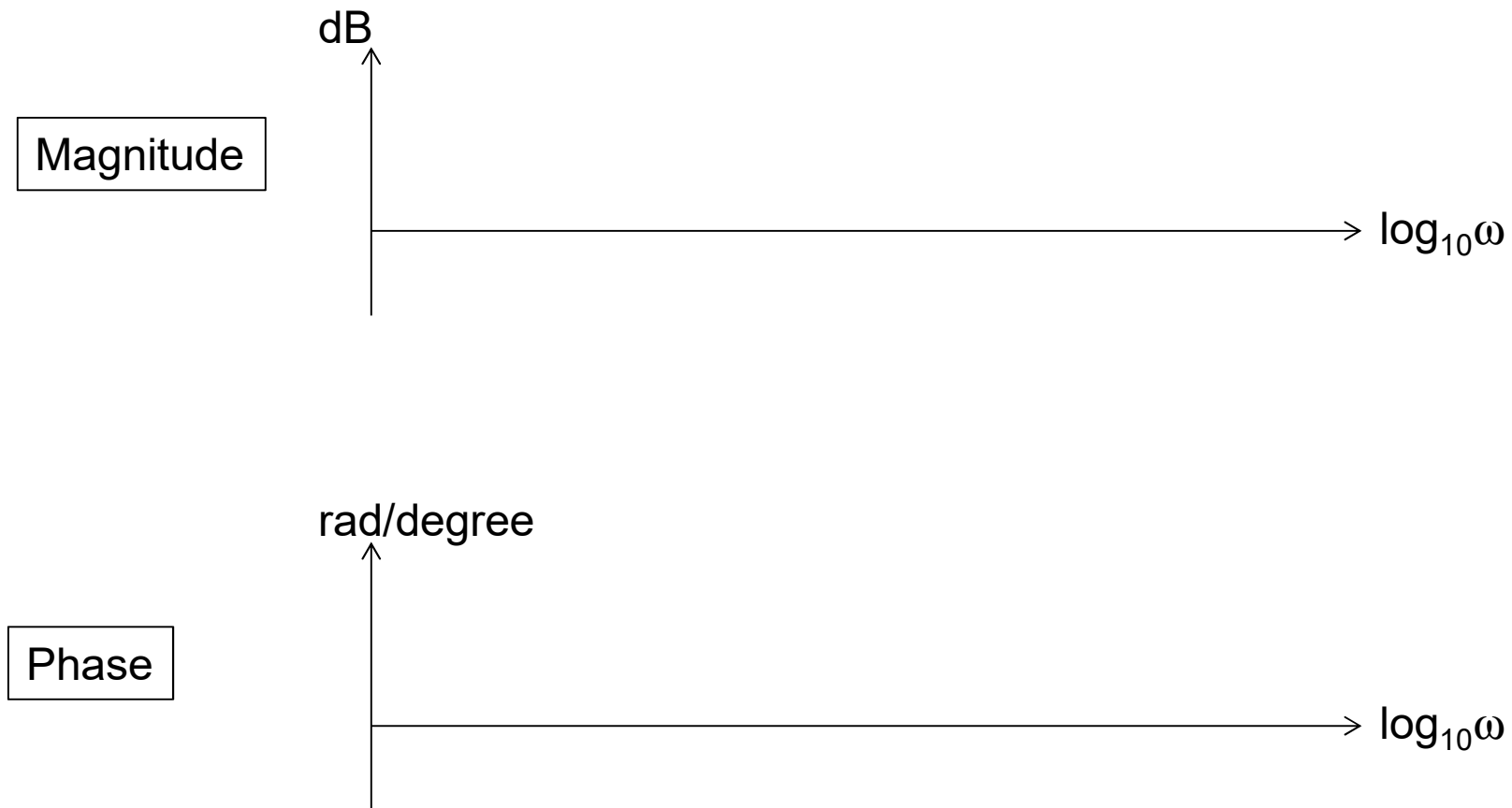

The frequency response may be written in factored form:

$$\begin{aligned}
 H(j\omega) &= \frac{N(j\omega)}{D(j\omega)} = \frac{\sum_{m=0}^M b_m (j\omega)^m}{\sum_{n=0}^N a_n (j\omega)^n} \\
 &= \frac{b_M (j\omega)^M + b_{M-1} (j\omega)^{M-1} + \dots + b_1 (j\omega) + b_0}{a_N (j\omega)^N + a_{N-1} (j\omega)^{N-1} + \dots + a_1 (j\omega) + a_0}
 \end{aligned}$$

$$\begin{aligned}
&= \frac{b_M (j\omega)^M + \frac{b_{M-1}}{b_M} (j\omega)^{M-1} + \dots + \frac{b_0}{b_M}}{a_N (j\omega)^N + \frac{a_{N-1}}{a_N} (j\omega)^{N-1} + \dots + \frac{a_0}{a_N}} \quad \downarrow \text{factorization} \\
&= \frac{b_M (j\omega + z_1)(j\omega + z_2) \dots (j\omega + z_M)}{a_N (j\omega + p_1)(j\omega + p_2) \dots (j\omega + p_N)} \\
&= \frac{b \prod_{m=1}^M (j\omega + z_m)}{\prod_{n=1}^N (j\omega + p_n)}
\end{aligned}$$

where $\tilde{b} = \frac{b_M}{a_N}$

All of the coefficients of $N(j\omega)$ are real,
therefore the roots of $N(j\omega) = 0$ must be
(1) Real (2) C.C.
either real or appear in complex conjugate
pairs. That implies z_m , $m = 1, 2, \dots, M$ are
either real or appear in complex conjugate
pairs. The same is true for p_n , $n = 1, 2, \dots, N$.

E.g., Section 8.5, series RLC

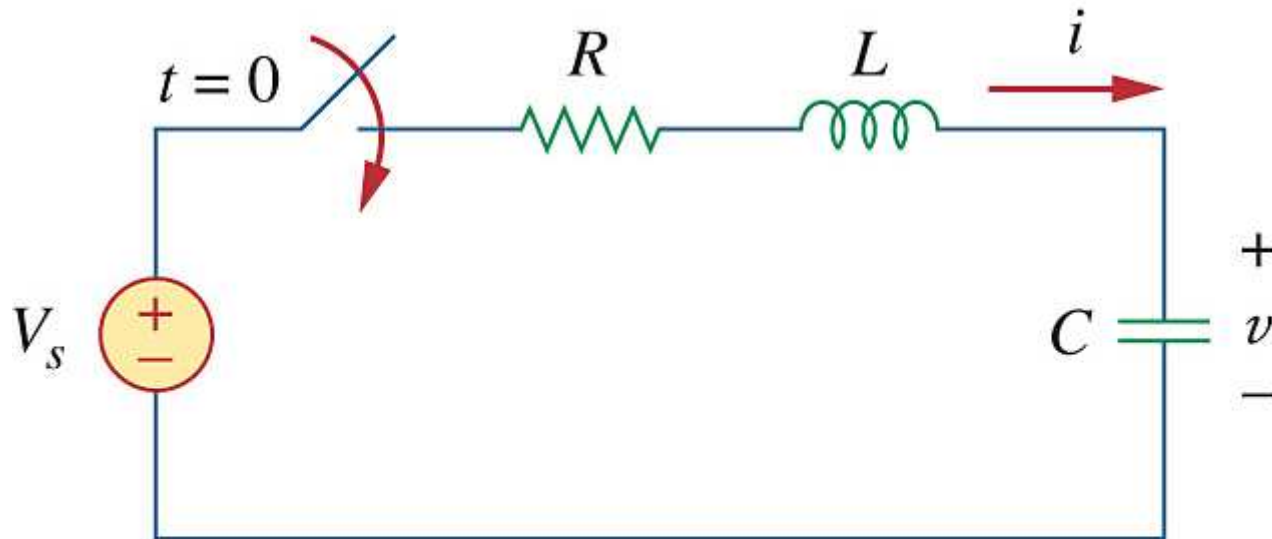


Figure 8.18 Step voltage applied to a series RLC circuit.

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} V_s$$

$$a_2 y'' + a_1 y' + a_0 y = b_0 x$$

The values of R , L , C are real
→ The coefficients are real

(1) Real

If z_m is real, we write

$$j\omega + z_m = \begin{cases} z_m (1 + j\omega / z_m), & z_m \neq 0 \\ j\omega, & z_m = 0 \end{cases}$$


(2) C.C.

If z_m is complex, we group factors $(j\omega + z_m)$

and $(j\omega + z_m^*)$ into real-valued quadratic factor

$$\begin{aligned} (j\omega + z_m)(j\omega + z_m^*) &= (j\omega)^2 + (z_m + z_m^*)j\omega + z_m z_m^* \\ &= (j\omega)^2 + 2 \operatorname{Re}(z_m)(j\omega) + |z_m|^2 \end{aligned}$$

$$\begin{aligned}
&= |z_m|^2 \left[1 + \frac{2 \operatorname{Re}(z_m)(j\omega)}{|z_m|^2} + \frac{(j\omega)^2}{|z_m|^2} \right] \\
&= |z_m|^2 \left[1 + \frac{2 \operatorname{Re}(z_m)}{|z_m|} \left(\frac{j\omega}{|z_m|} \right) + \left(\frac{j\omega}{|z_m|} \right)^2 \right] \\
&= \omega_k^2 \left[1 + 2\zeta_k (j\omega / \omega_k) + (j\omega / \omega_k)^2 \right]
\end{aligned}$$

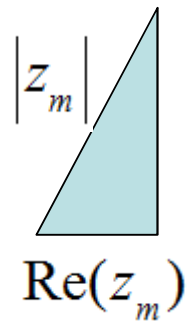

where $\omega_k = |z_m|$ and $\zeta_k = \operatorname{Re}(z_m) / |z_m|$. It is evident that $0 \leq |\zeta_k| \leq 1$.

So, $H(j\omega)$ may be represented in the *standard form*:

1. The b

2. $z_m=0$; $p_n=0$

$$H(j\omega) = \underline{K(j\omega)^{\pm 1}} \times$$

$$\frac{(1 + j\omega / z_1)[1 + j2\zeta_1(j\omega / \omega_k) + (j\omega / \omega_k)^2]}{(1 + j\omega / p_1)[1 + j2\zeta_2(j\omega / \omega_n) + (j\omega / \omega_n)^2]}$$

We will now plot straight-line-segment approximations (called *asymptotes*) associated with the factors in $H(j\omega)$.

4. $z_m=c.c.$; $p_n=c.c.$

3. $z_m=real$; $p_n=real$

1. The b

(1) For the gain K ,

$$H_{dB} = \underline{20} \log_{10} |K|$$

$$\phi = \begin{cases} 0^\circ, & K > 0 \\ 180^\circ, & K < 0 \end{cases}$$

Because of amplitude
(voltage/current)

as shown in Fig. 14.9.

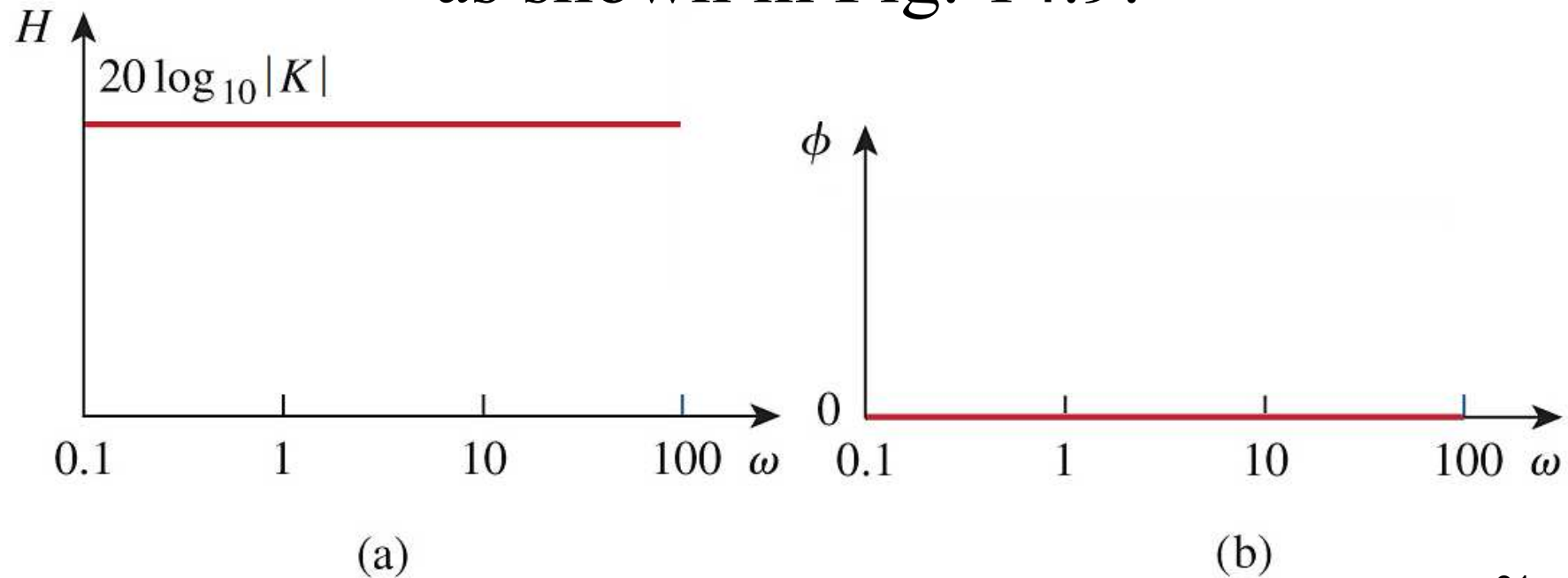


Figure 14.9 Bode plots for gain K : (a) magnitude plot, (b) phase plot.

$$2. \mathbf{z_m=0; p_n=0}$$

(2) For $j\omega$,

$$\underbrace{H_{dB}}_y = 20 \log_{10} |j\omega| = \underbrace{20}_{\text{slope}} \underbrace{\log_{10} \omega}_x$$

$$\phi = 90^\circ$$

These are shown in Fig. 14.10, where we notice that the slope of the magnitude plot is 20 dB/decade, where the word *decade* means a group or series of ten.

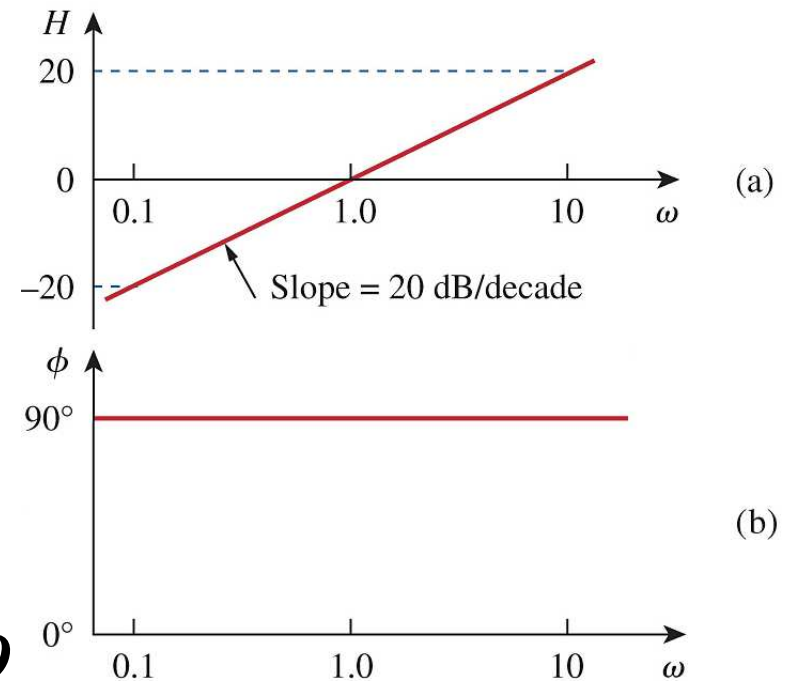


Figure 14.10 Bode plots for $j\omega$.

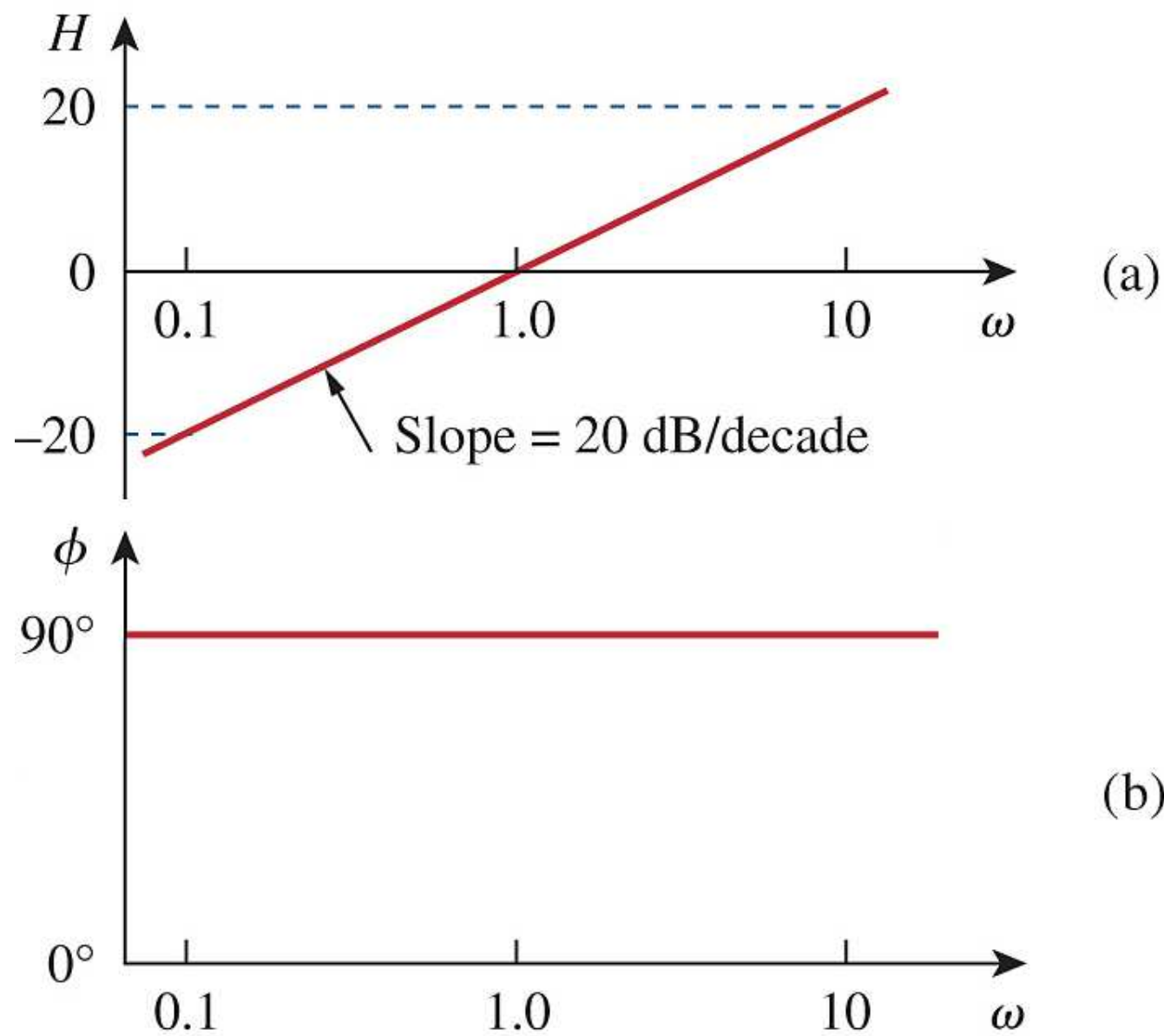


Figure 14.10 Bode plots for $j\omega$.

The Bode plots for $(j\omega)^{-1}$ are similar except that the slope of the magnitude plot is -20 dB/decade while the phase is -90° . In general, for $(j\omega)^N$, where N is an integer, the magnitude plot will have a slope of $20N$ dB/decade, while the phase is $90N^\circ$.

$$H_{dB} = 20 \log_{10} |(j\omega)^{-1}| = -20 \log_{10} \omega$$

$$\angle (j\omega)^{-1} = \angle 1 - \angle (j\omega) = 0^\circ - 90^\circ = -90^\circ$$

$$H_{dB} = 20 \log_{10} |(j\omega)^N| = 20N \log_{10} \omega$$

$$\angle (j\omega)^N = \angle (j\omega) + \angle (j\omega) + \dots = 90N^\circ$$

3. $z_m = \text{real}; p_n = \text{real}$

(3) For $(1 + j\omega / z_1)$,

$$H_{dB} = 20 \log_{10} |1 + j\omega / z_1|$$

$$\phi = \tan^{-1}(\omega / z_1)$$

We notice that

$$\begin{cases} H_{dB} = 20 \log_{10} 1 = 0 \\ \phi = 0^\circ \end{cases}, \omega \rightarrow 0$$

$$\begin{cases} H_{dB} = 20 \log_{10} (\omega / z_1) \\ \phi = 90^\circ \end{cases}, \omega \rightarrow \infty$$

0 dB at $\omega = z_1$
Slope = 20dB/decade

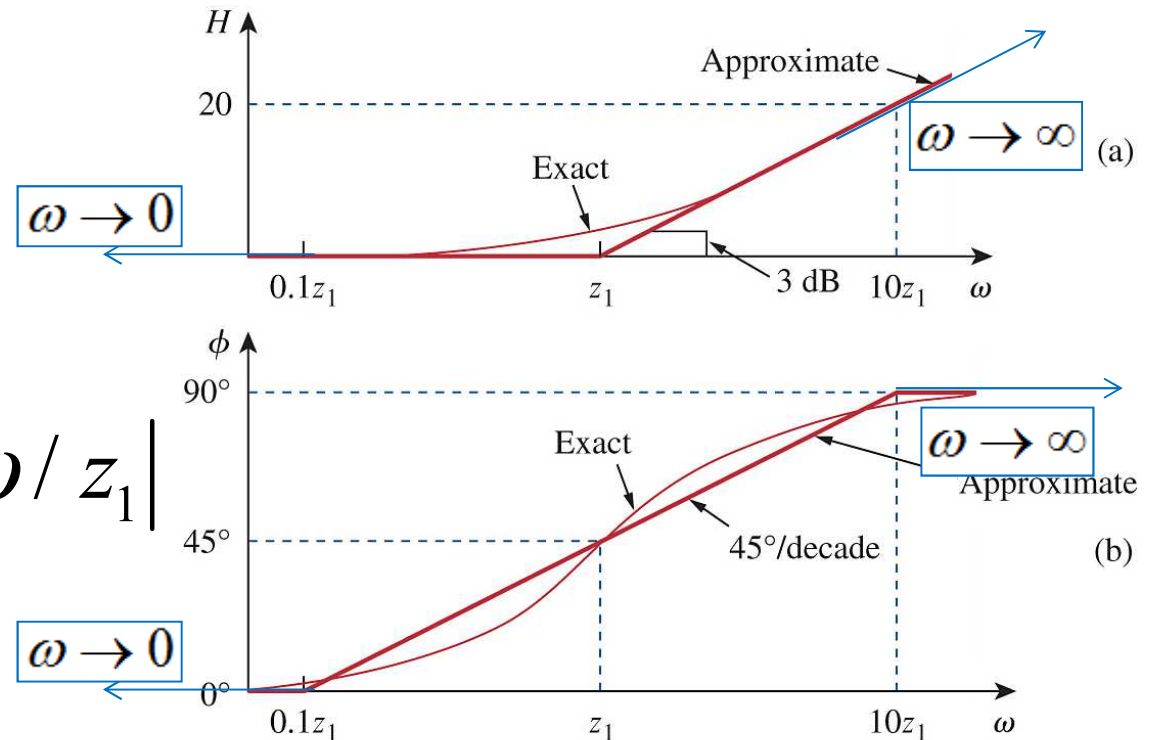


Figure 14.11 Bode plots for $1 + j\omega/z_1$: (a) magnitude plot, (b) phase plot.

Compare the approximate and exact curves

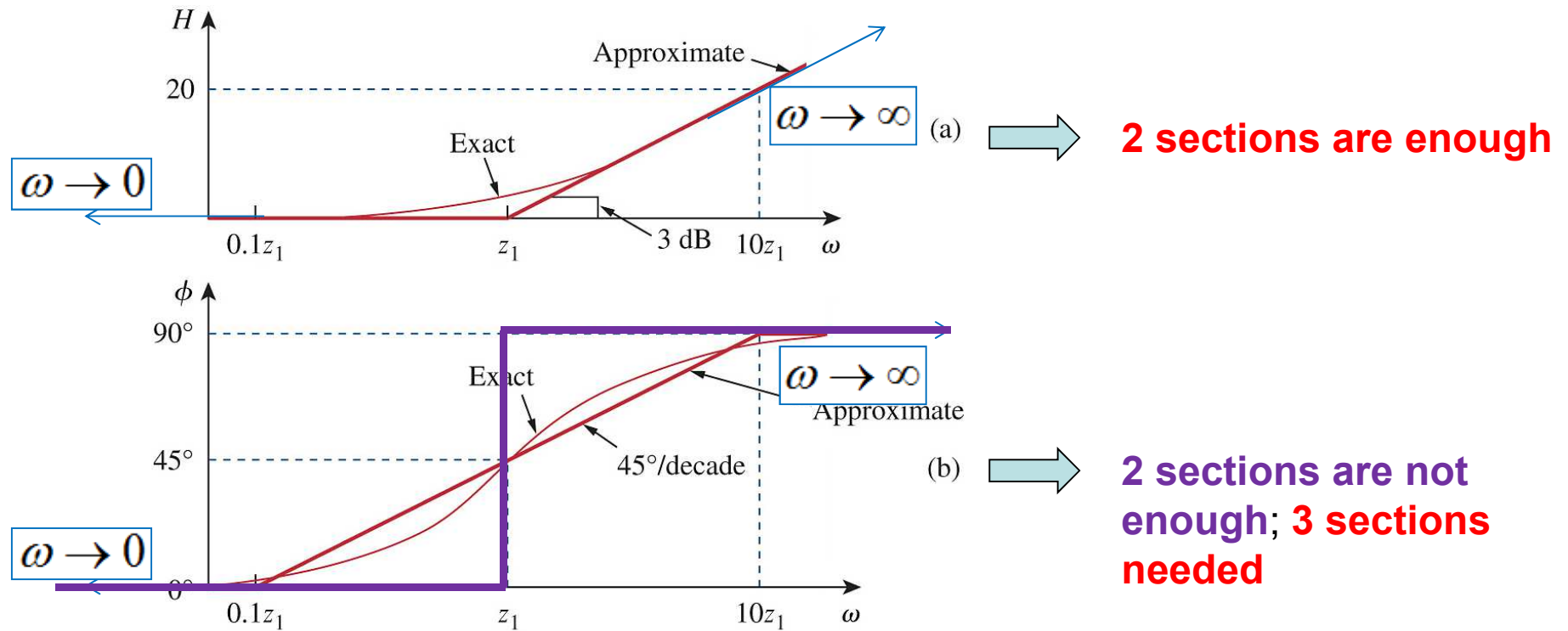


Figure 14.11 Bode plots for $1 + j\omega/z_1$: (a) magnitude plot, (b) phase plot.

As a straight-line approximation, we let

$$H_{dB} = \begin{cases} 0, & \omega \leq z_1 \\ 20 \log_{10}(\omega / z_1), & \omega \geq z_1 \end{cases}$$

$$\phi = \begin{cases} 0^\circ, & \omega \leq 0.1z_1 \\ 45^\circ + 45^\circ \log_{10}(\omega / z_1), & 0.1z_1 \leq \omega \leq 10z_1 \\ 90^\circ, & \omega \geq 10z_1 \end{cases}$$

as shown in Fig. 14.11. The frequency $\omega = z_1$ is called the *corner frequency* or *break frequency*.

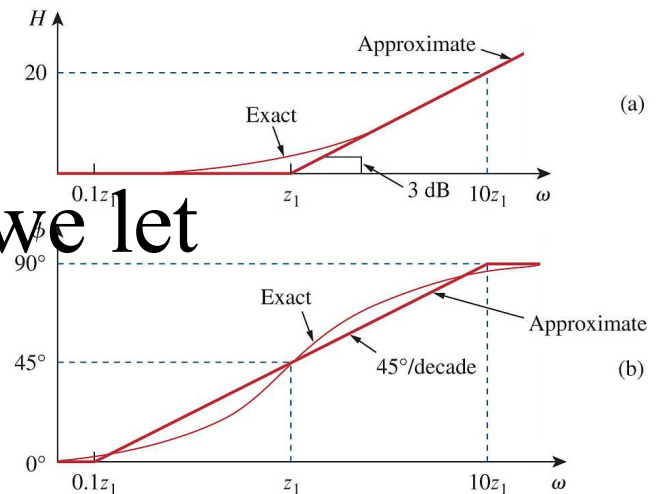


Figure 14.11 Bode plots for $1 + j\omega/z_1$: (a) magnitude plot, (b) phase plot.

At $\omega = z_1$, $\tan^{-1}(1) = 45^\circ$
Use a straight line to connect the three points $\omega = 0.1z_1, z_1, 10z_1$

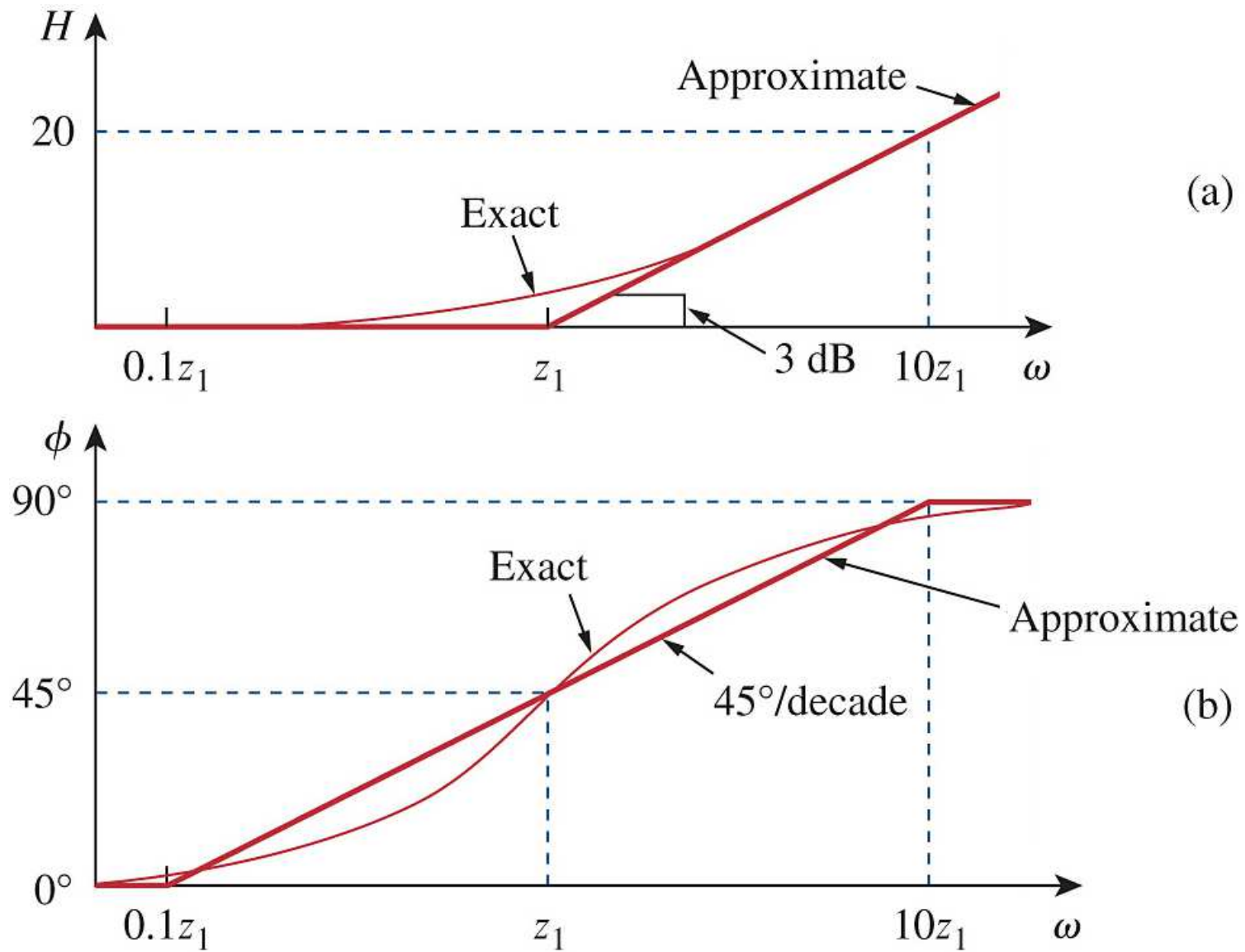


Figure 14.11 Bode plots for $1 + j\omega/z_1$: (a) magnitude plot, (b) phase plot.

The Bode plots for $1 / (1 + j\omega / p_1)$ are similar to those in Fig. 14.11 except that the corner frequency is at $\omega = p_1$, the magnitude has a slope of -20 dB/decade, and the phase has a slope of -45° per decade.

In general, for $(1 + j\omega / z_1)^N$, where N is an integer,

$$H_{dB} = \begin{cases} 0, & \omega \leq z_1 \\ 20N \log_{10}(\omega / z_1), & \omega \geq z_1 \end{cases}$$

$$\phi = \begin{cases} 0^\circ, & \omega \leq 0.1z_1 \\ 45N^\circ + 45N^\circ \log_{10}(\omega / z_1), & 0.1z_1 \leq \omega \leq 10z_1 \\ 90N^\circ, & \omega \geq 10z_1 \end{cases}$$

4. $\mathbf{z_m=c.c.}; \mathbf{p_n=c.c.}$

(4) For $1/[1+2\zeta_2(j\omega/\omega_n)+(j\omega/\omega_n)^2]$,

$$H_{dB} = -20 \log_{10} \left| 1 + 2\zeta_2(j\omega/\omega_n) + (j\omega/\omega_n)^2 \right|$$

$$\phi = -\tan^{-1} \left(\frac{2\zeta_2\omega/\omega_n}{1-\omega^2/\omega_n^2} \right)$$

We notice that

$$\begin{cases} H_{dB} = -20 \log_{10} 1 = 0 \\ \phi = 0^\circ \end{cases}, \quad \omega \rightarrow 0$$

$\tan^{-1}(0)=0^\circ$

$$\begin{cases} H_{dB} = -40 \log_{10} (\omega/\omega_n) \\ \phi = -180^\circ \end{cases}, \quad \omega \rightarrow \infty$$

$-\tan^{-1}(0)=0^\circ \text{ or } -180^\circ?$

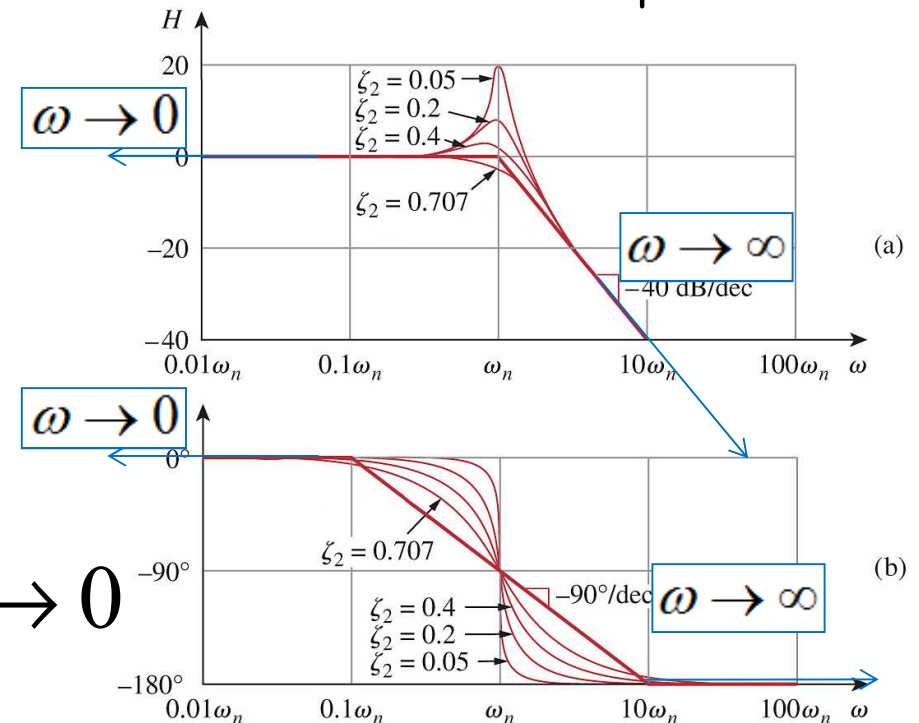


Figure 14.12 Bode plots of $1/[1+2\zeta_2(j\omega/\omega_n)+(j\omega/\omega_n)^2]$: (a) magnitude plot, (b) phase plot.

As a straight-line approximation, we let

$$H_{dB} = \begin{cases} 0, & \omega \leq \omega_n \\ -40 \log_{10}(\omega / \omega_n), & \omega \geq \omega_n \end{cases}$$

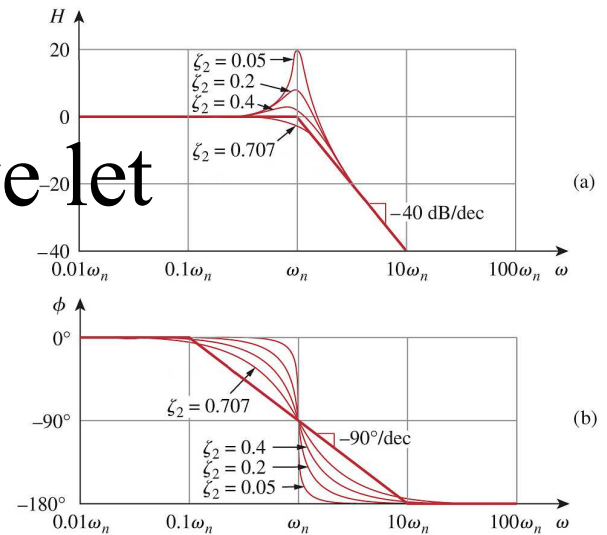


Figure 14.12 Bode plots of $1/[1+2\zeta_2(j\omega/\omega_n)+(j\omega/\omega_n)^2]$: (a) magnitude plot, (b) phase plot.

$$\phi = \begin{cases} 0^\circ, & \omega \leq 0.1\omega_n \\ -90^\circ - 90^\circ \log_{10}(\omega / \omega_n), & 0.1\omega_n \leq \omega \leq 10\omega_n \\ -180^\circ, & \omega \geq 10\omega_n \end{cases}$$

$\tan^{-1}(0)=0^\circ$
 $-\tan^{-1}(0)=0^\circ \text{ or } -180^\circ? \rightarrow -180^\circ$

as shown in Fig. 14.12. The frequency $\omega = \omega_n$ is called the *corner frequency* or *break frequency*.

At $\omega = \omega_n$, $\phi = -\tan^{-1}(\infty) = -90^\circ$
 Use a straight line to connect the three points $\omega = 0.1\omega_n$, ω_n , $10\omega_n$

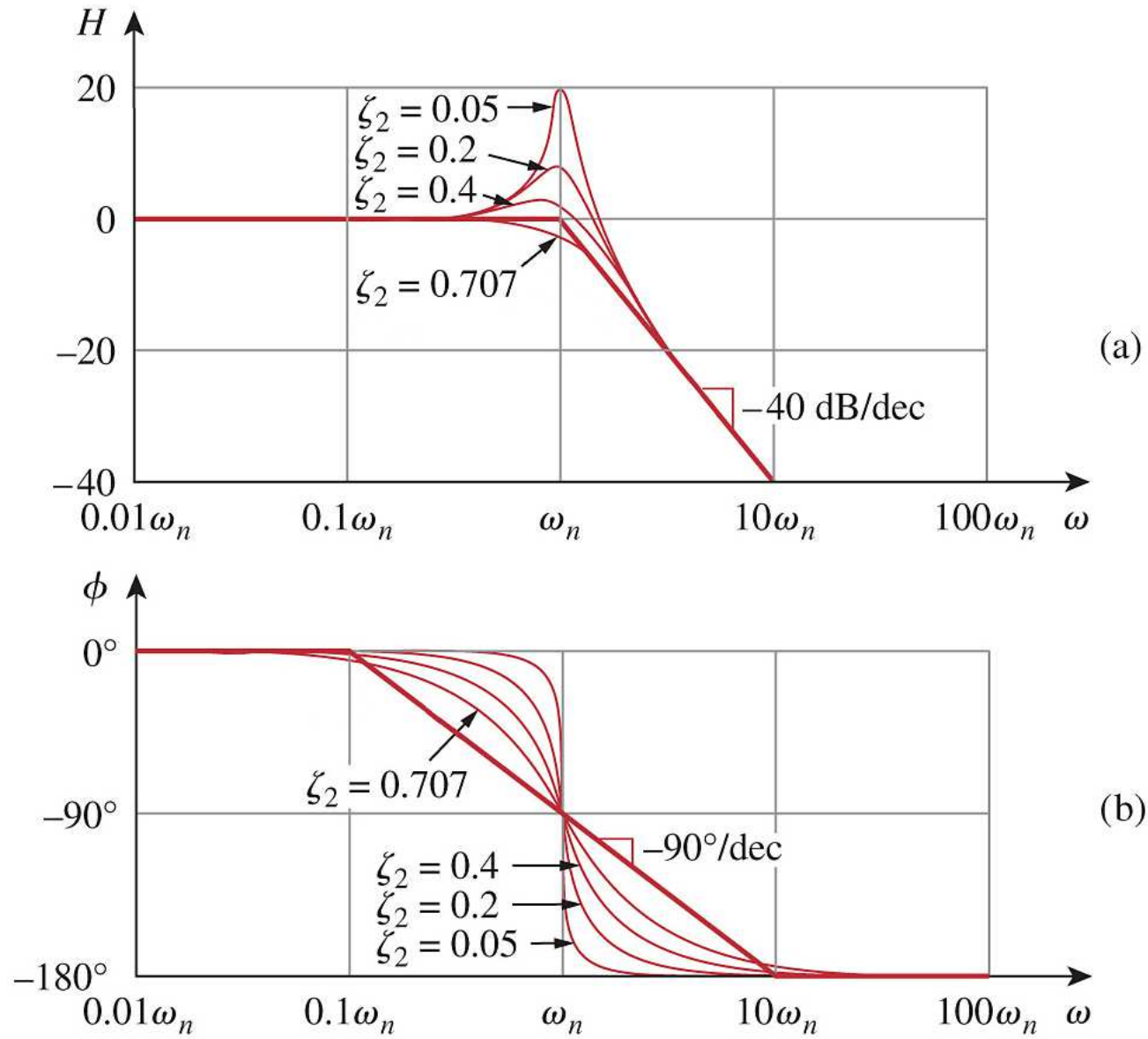


Figure 14.12 Bode plots of $1/[1+2\zeta_2(j\omega/\omega_n)+(j\omega/\omega_n)^2]$: (a) magnitude plot, (b) phase plot.

The Bode plots for $[1 + 2\zeta_1(j\omega / \omega_k) + (j\omega / \omega_k)^2]$ are similar to those in Fig. 14.12 except that the corner frequency is at $\omega = \omega_k$, the magnitude has a slope of +40 dB/decade, and the phase has a slope of +90° per decade.

Factor


Magnitude

Phase

1. The b or K



K

$20 \log_{10} K$


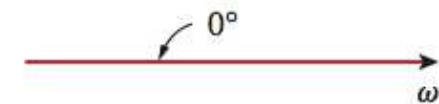


2. $z_m=0$; $p_n=0$

$(j\omega)^N$

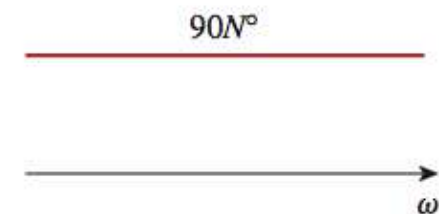
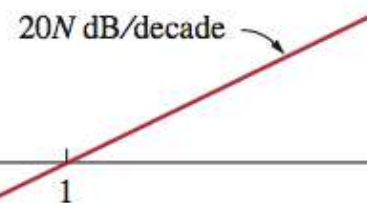


$\frac{1}{(j\omega)^N}$

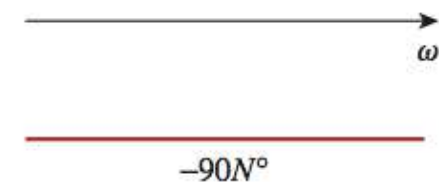
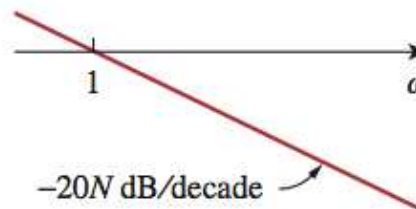


3. $z_m=\text{real}$; $p_n=\text{real}$

$\left(1 + \frac{j\omega}{z}\right)^N$

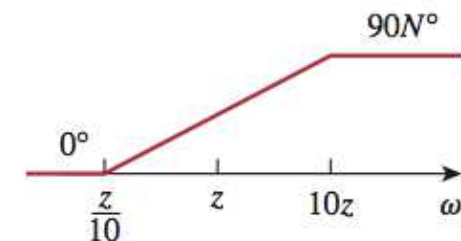
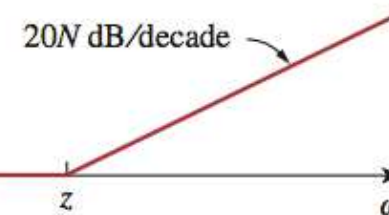


$$\frac{1}{(1 + j\omega/p)^N}$$

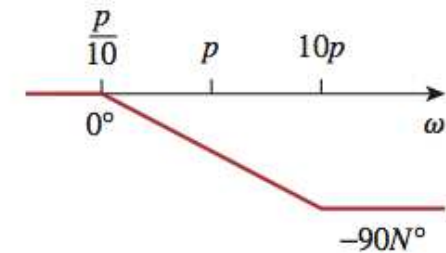
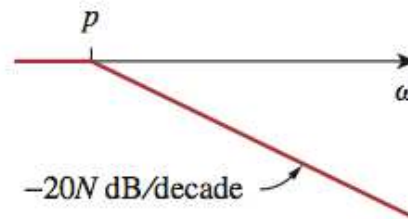


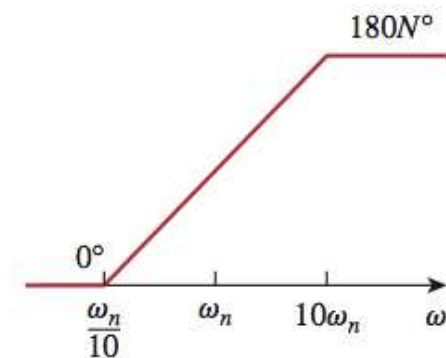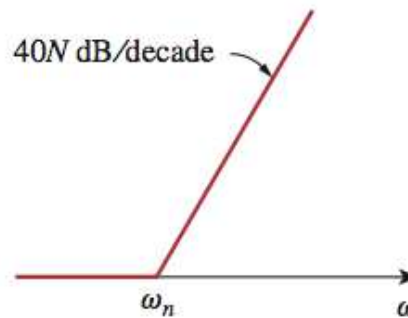4. $z_m = \text{c.c.}; p_n = \text{c.c.}$

$$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right]^N$$


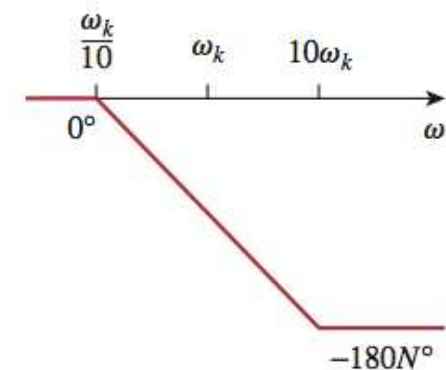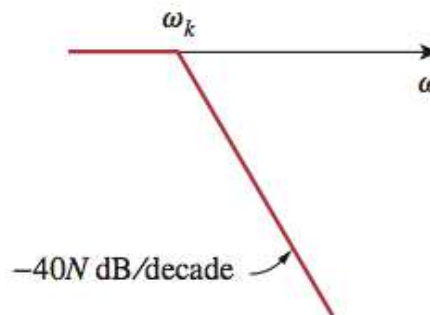
$$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$$



Zeros: upward turn

Poles: downward turn

Practice Problem 14.3 Draw the Bode plots for

$$H(j\omega) = \frac{5(j\omega + 2)}{j\omega(j\omega + 10)}$$

Solution :

$$H(j\omega) = \frac{(1 + j\omega/2)}{j\omega(1 + j\omega/10)}$$

Type 3, zero

Type 2, pole

Type 3, pole

$$H_{dB} = 20 \log_{10} \left| \frac{(1 + j\omega/2)}{j\omega(1 + j\omega/10)} \right|$$

$$= 20 \log_{10} |1 + j\omega / 2| + 20 \log_{10} \frac{1}{|j\omega|}$$

$$+ 20 \log_{10} \frac{1}{|1 + j\omega / 10|}$$

$$= 20 \log_{10} |1 + j\omega / 2| - 20 \log_{10} |j\omega|$$

$$- 20 \log_{10} |1 + j\omega / 10|$$

$$\phi = \tan^{-1}(\omega / 2) - 90^\circ - \tan^{-1}(\omega / 10)$$

The Bode plots are in Fig. 14.14.

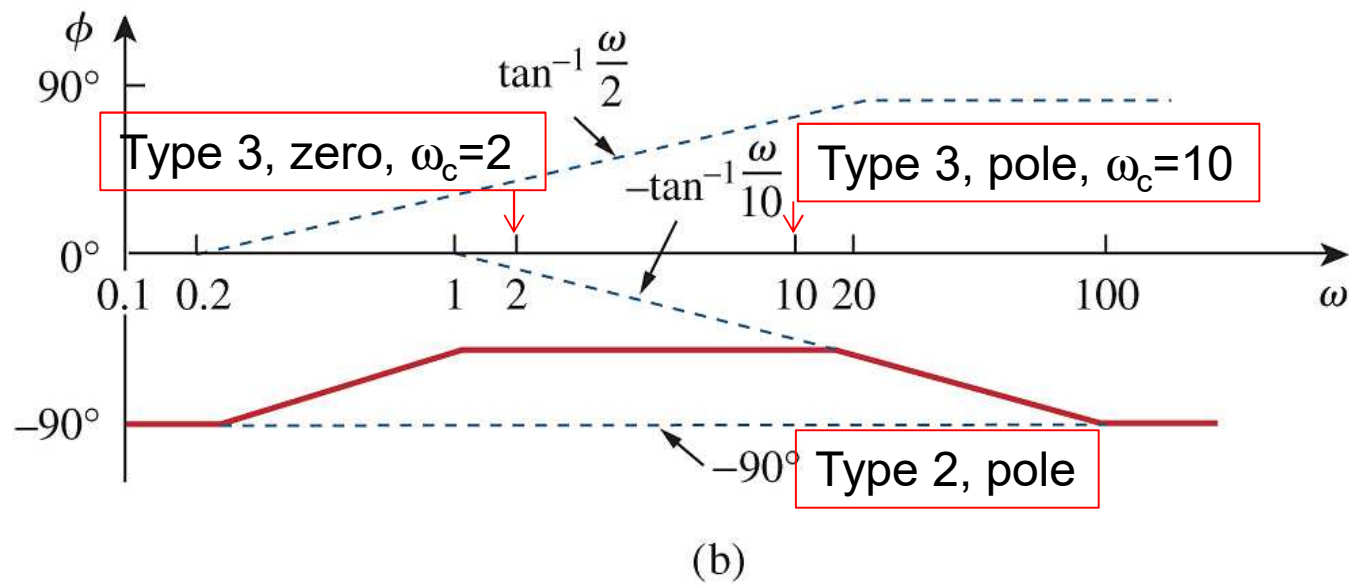
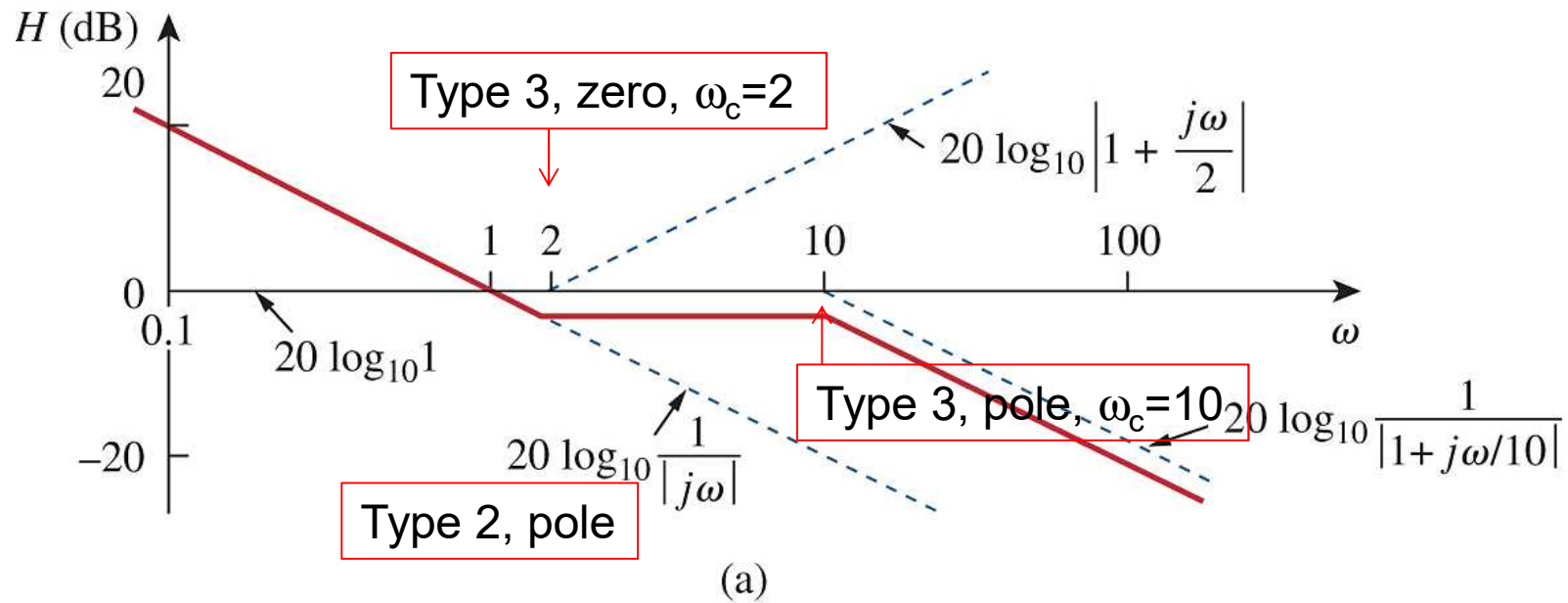


Figure 14.14

Example 14.4 Obtain the Bode plots for

$$H(j\omega) = \frac{j\omega + 10}{j\omega(j\omega + 5)^2}$$

Solution :

Annotations for the transfer function:

- Type 1 (points to the constant 0.4)
- Type 3, zero (points to the zero at $j\omega/10$)
- Type 2, pole (points to the pole at $j\omega$)
- Type 3, N=2, pole (points to the double pole at $j\omega/5$)

$$H(j\omega) = \frac{0.4(1 + j\omega/10)}{j\omega(1 + j\omega/5)^2}$$
$$H_{dB} = 20 \log_{10} \left| \frac{0.4(1 + j\omega/10)}{j\omega(1 + j\omega/5)^2} \right|$$

$$\begin{aligned}
 &= 20 \log_{10} 0.4 + 20 \log_{10} |1 + j\omega / 10| + \\
 &-20 \log_{10} |j\omega| - 40 \log_{10} |1 + j\omega / 5| \\
 \phi &= 0^\circ + \tan^{-1}(\omega / 10) - 90^\circ - 2 \tan^{-1}(\omega / 5)
 \end{aligned}$$

The Bode plots are in Fig. 14.15.

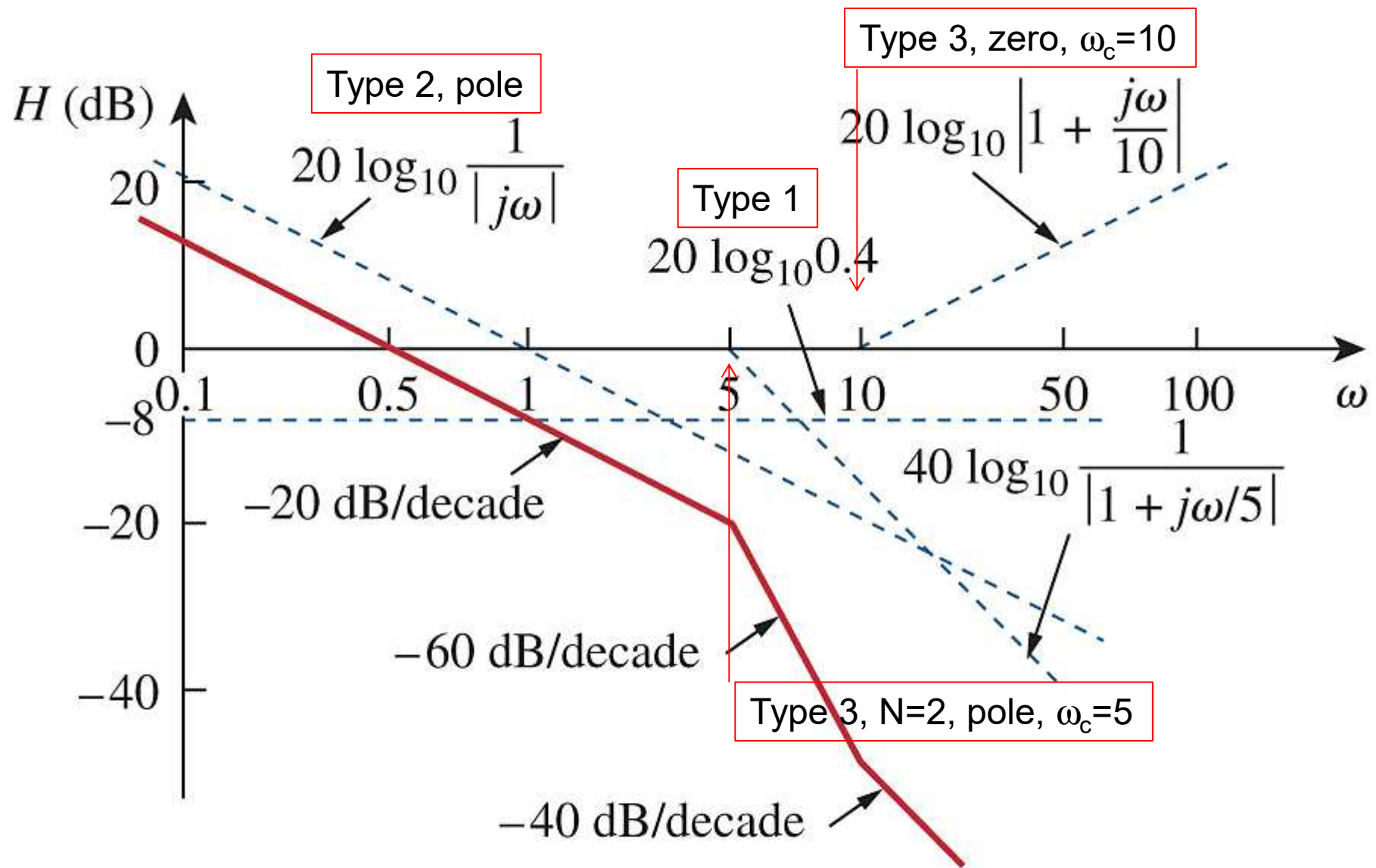


Figure 14.15(a)

Example 14.5 Draw the Bode plots for

$$H(j\omega) = \frac{j\omega + 1}{(j\omega)^2 + 12(j\omega) + 100}$$

Solution :

$$\begin{aligned}
 H(j\omega) &= \frac{0.01(1 + j\omega/1)}{1 + 0.12(j\omega) + (j\omega/10)^2} \\
 &= \frac{\text{Type 1} \quad 0.01(1 + j\omega/1) \quad \text{Type 3, zero}}{1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2} \\
 &\hspace{15em} \text{Type 4, pole}
 \end{aligned}$$

$$\begin{aligned}
H_{dB} &= 20 \log_{10} \left| \frac{0.01(1 + j\omega/1)}{1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2} \right| \\
&= 20 \log_{10} 0.01 + 20 \log_{10} |1 + j\omega/1| \\
&\quad - 20 \log_{10} |1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2| \\
\phi &= 0^\circ + \tan^{-1}(\omega/1) - \tan^{-1} \left[\frac{2 \times 0.6(\omega/10)}{1 - (\omega/10)^2} \right]
\end{aligned}$$

The Bode plots are in Fig. 14.17.

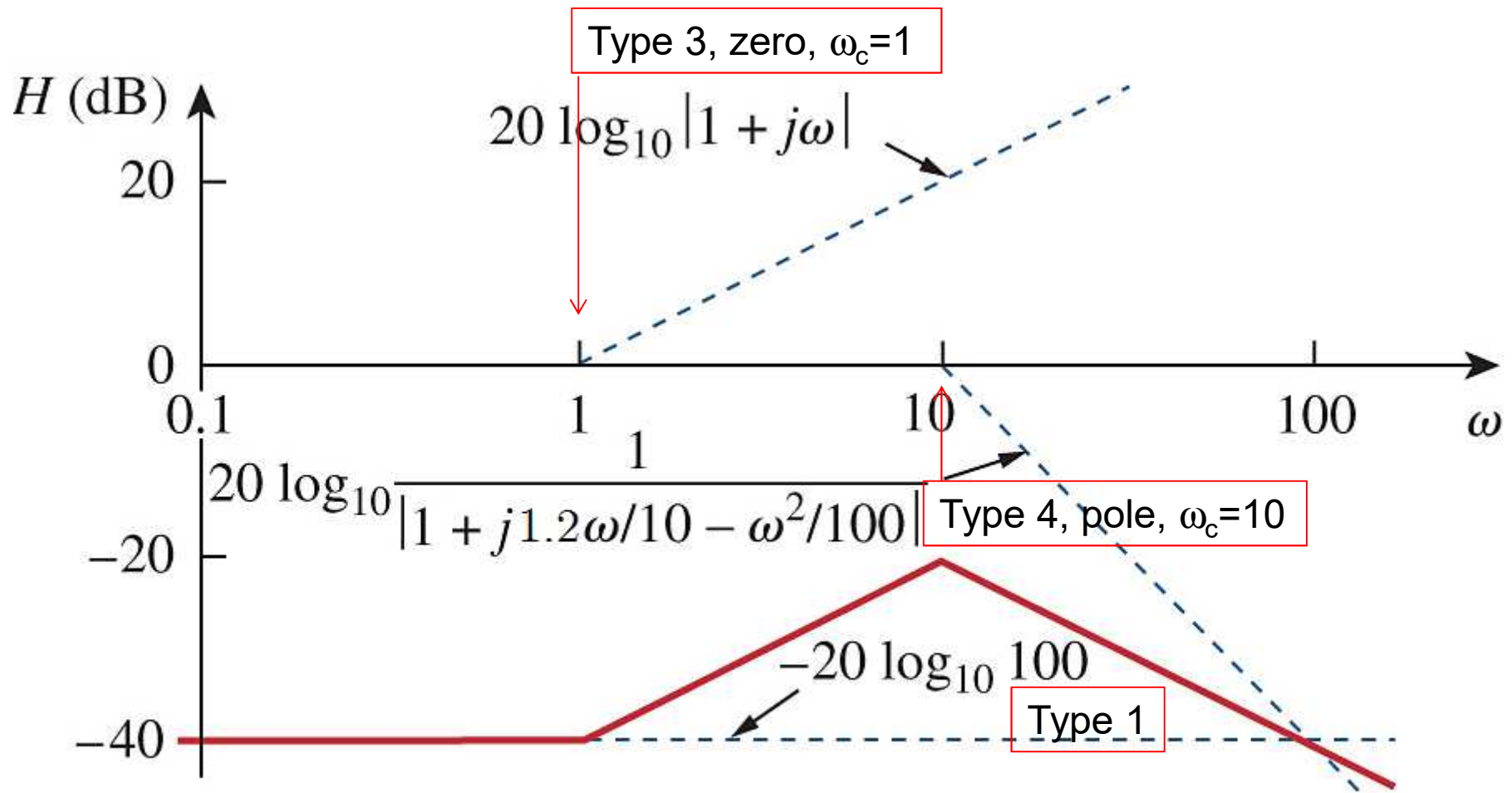


Figure 14.17(a)

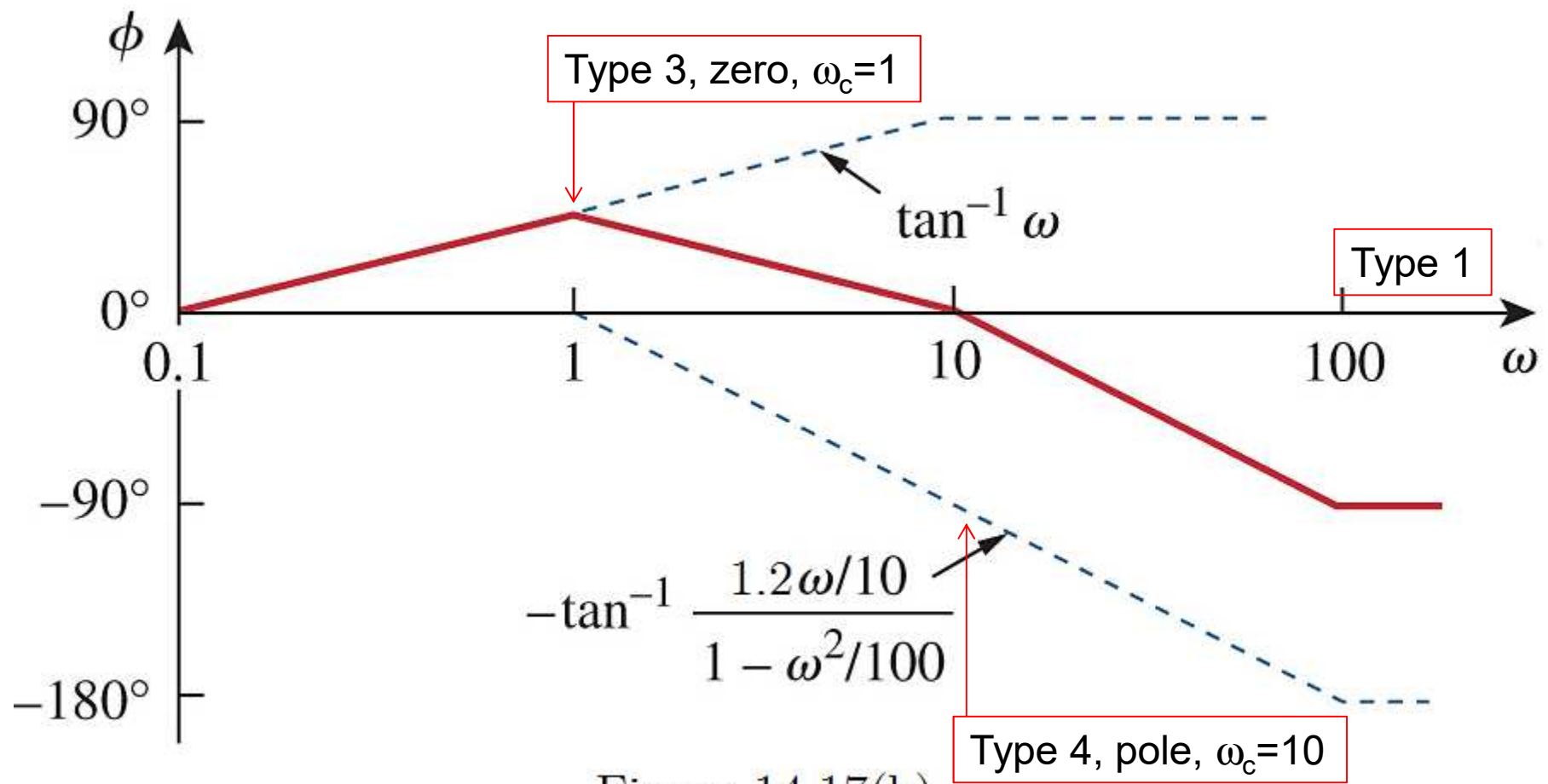


Figure 14.17(b)

14.5 Series Resonance

Resonance occurs in any circuits that has at least one inductor and one capacitor.

Consider the series *RLC* circuit shown in Fig. 14.21. The input impedance is

$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

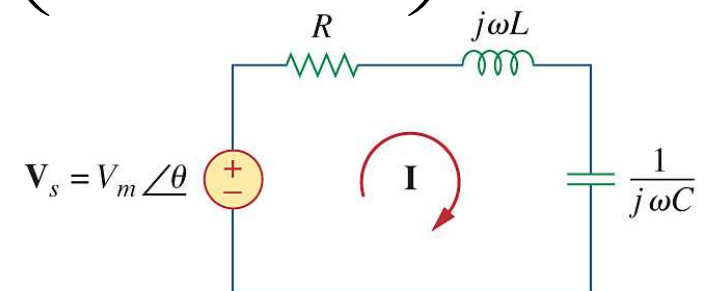


Figure 14.21 The series resonant circuit.

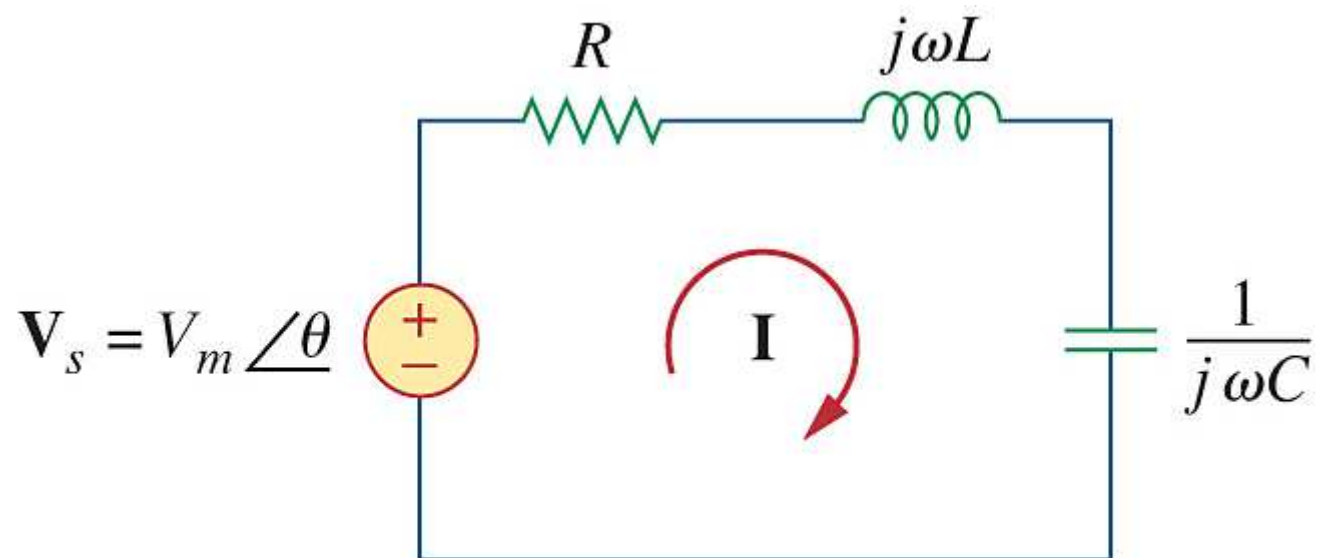


Figure 14.21 The series resonant circuit.

Resonance results when $\text{Im}(Z) = 0$, that is, the capacitive and inductive reactances are equal in magnitude. The value of ω that satisfies this condition is called the *resonant frequency* ω_0 . Thus, the resonance condition is

$$\omega_0 L = \frac{1}{\omega_0 C}$$

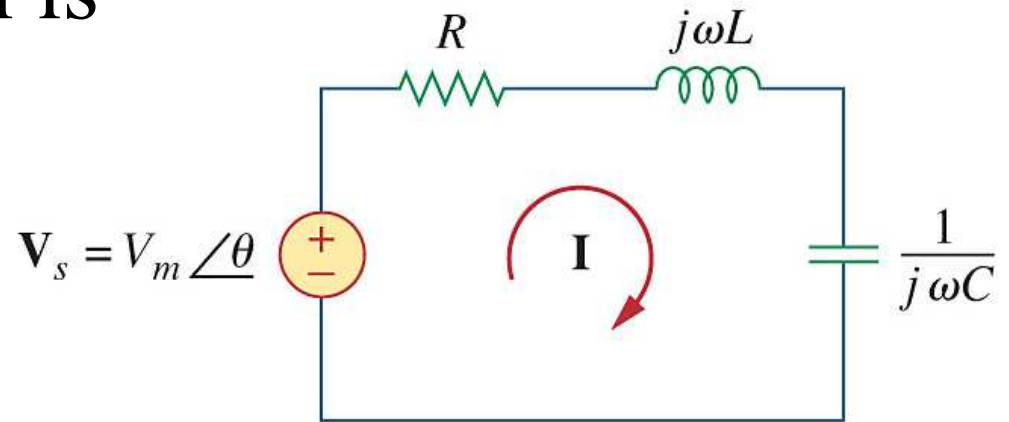


Figure 14.21 The series resonant circuit.

Resonance


$$\text{Im}(Z) = \omega L - \frac{1}{\omega C} = 0 \quad (14.24)$$

$$|Q_L| = |I^2 X| = I^2 \omega L$$

$$|Q_C| = |I^2 X| = I^2 / \omega C$$

$$|Q_L| = |Q_C|$$

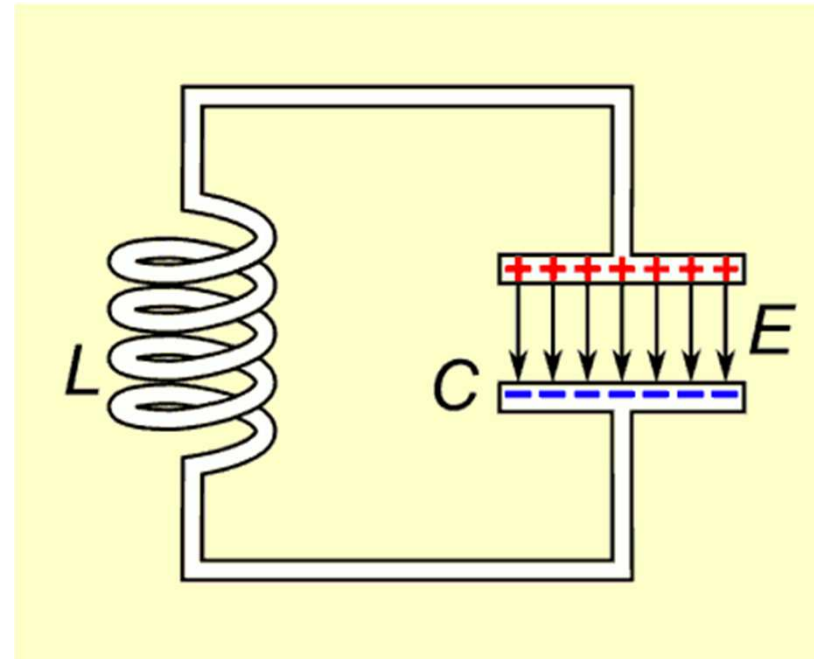
At resonance, the energies from inductive and capacitive circuits are equal.



Ease of Excitation at Resonance

It is easy to get an object to vibrate at its resonant frequencies, hard at other frequencies. A child's playground swing is an example of a pendulum, a resonant system with only one resonant frequency. With a tiny push on the swing each time it comes back to you, you can continue to build up the **amplitude** of swing. If you try to force it to swing a twice that frequency, you will find it very difficult, and might even lose teeth in the process!

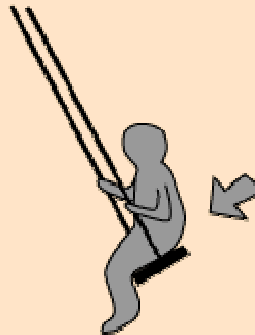Swinging a child in a playground swing is an easy job because you are helped by its natural frequency.



But can you swing it at some other frequency?

In circuit,

- Driving frequency should be resonant frequency ω_0
- Building up the amplitude (voltage/current)

$$\omega_0 = 2\pi f_0 = \frac{1}{\sqrt{LC}}$$

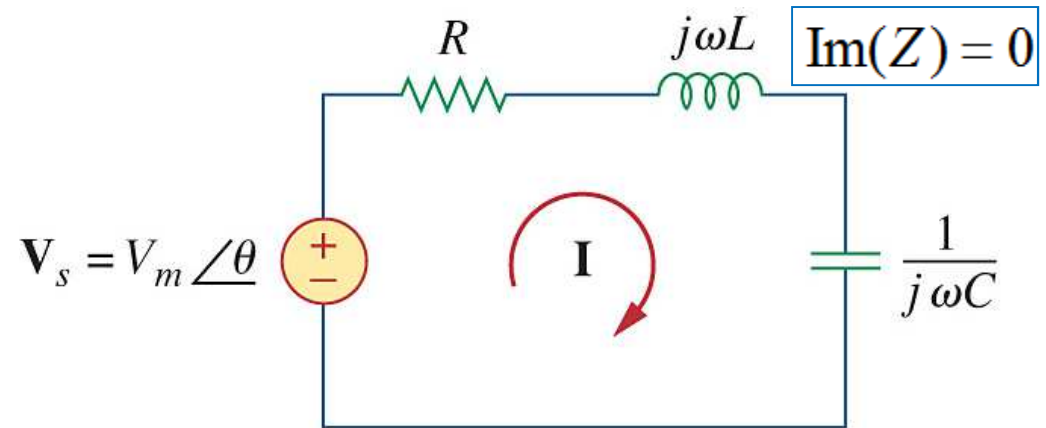


Figure 14.21 The series resonant circuit.

Note that at resonance:

1. The impedance is purely resistive, thus, $Z = R$. In other words, the LC series combination acts like a short circuit, and the entire voltage is across R .
2. The voltage V_s and the current I are in phase.

3. The magnitude of the current is maximum.

Proof :

Because $|\mathbf{Z}|$ achieves minimum

The circuit's current magnitude

$$I = \left| \frac{V_s}{Z} \right| = \left| \frac{V_m \angle \theta}{R + j(\omega L - \frac{1}{\omega C})} \right|$$
$$= \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \leq \frac{V_m}{R} = I_{\max}$$

$$\text{Im}(Z) = 0$$

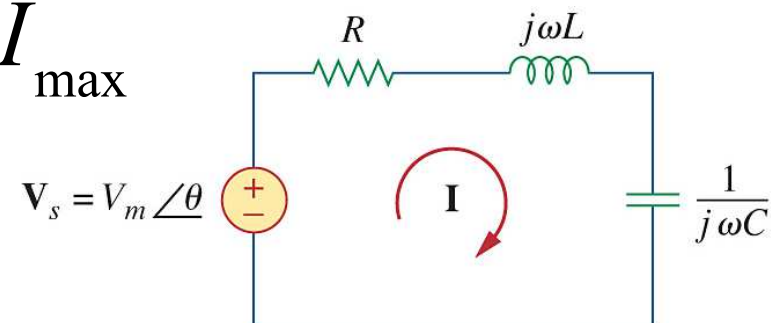


Figure 14.21 The series resonant circuit.

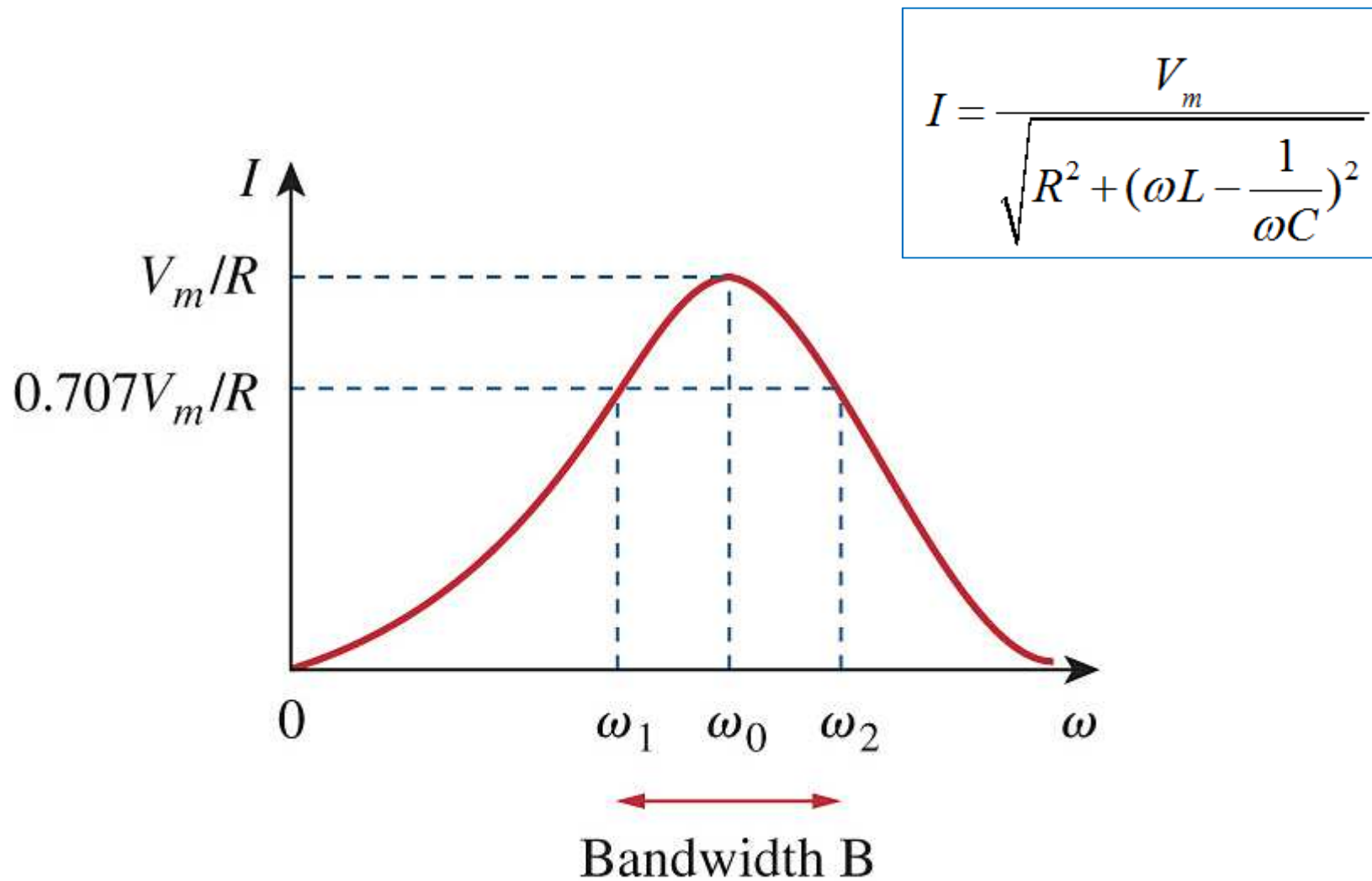


Figure 14.22 The current amplitude versus frequency for the series resonant circuit of Fig. 14.21.

The average power dissipated by the RLC circuit is

$$P(\omega) = \frac{1}{2} I^2 R = \frac{1}{2} \frac{V_m^2}{R^2 + (\omega L - 1/(\omega C))^2} R$$

The highest power dissipated occurs at resonance,

$$P(\omega_0) = \frac{1}{2} I_{\max}^2 R = \frac{1}{2} \frac{V_m^2}{R}$$

At certain frequencies $\omega = \omega_1, \omega_2$, the dissipated power is half the maximum value; that is,

$$P(\omega_1) = P(\omega_2) = \frac{1}{2} P(\omega_0) = \frac{V_m^2}{4R}$$

Hence, ω_1 and ω_2 are called the half -

power frequencies. $I(\omega_1) = I(\omega_2) = \frac{I_{\max}}{\sqrt{2}}$.

$$P(\omega) = \frac{1}{2} I^2 R$$

$$P(\omega_0) = \frac{1}{2} I_{\max}^2 R$$

$$\begin{array}{c} \downarrow \\ 1/2P(\omega_0) = 1/2P_{\max} \end{array}$$

The half-power frequencies are obtained by solving the equation

$$P = 1/2 \times I(\omega_{3dB})^2 R = 1/2 \times P_{\max}$$

$$\frac{1}{2} \frac{V_m^2}{R^2 + \left(\omega L - 1 / (\omega C) \right)^2} R = \frac{V_m^2}{4R}$$

$$\left(\omega L - 1 / (\omega C) \right)^2 = R^2$$

$$\omega L - 1 / (\omega C) = \pm R$$

$$LC\omega^2 \mp RC\omega - 1 = 0$$

$$\omega = \frac{\pm RC + \sqrt{(RC)^2 + 4LC}}{2LC}$$

$$= \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Neglect “-” solution

ω_1 and ω_2 are positive,

$$\omega = \pm \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

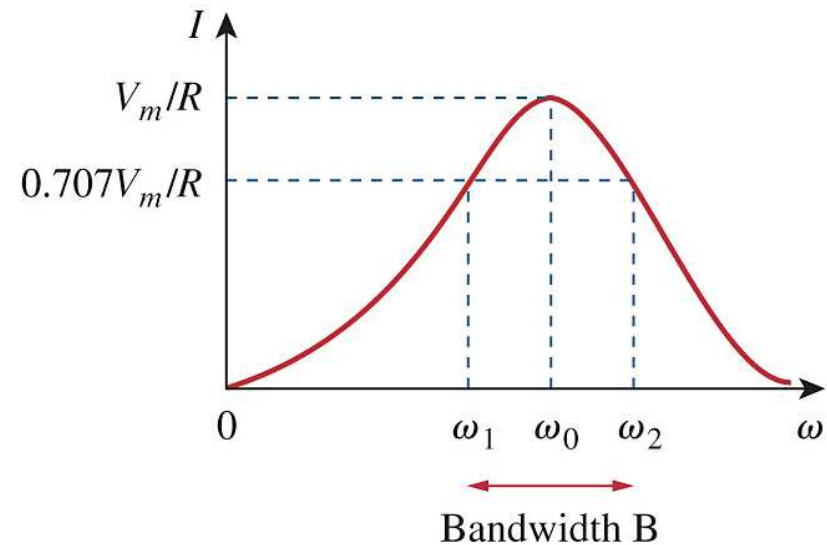


Figure 14.22 The current amplitude versus frequency for the series resonant circuit of Fig. 14.21.

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

We can relate the half-power frequencies and the resonant frequency,

$$\omega_1 \omega_2 = \frac{1}{LC} = \omega_0^2 \Rightarrow \omega_0 = \sqrt{\omega_1 \omega_2}$$

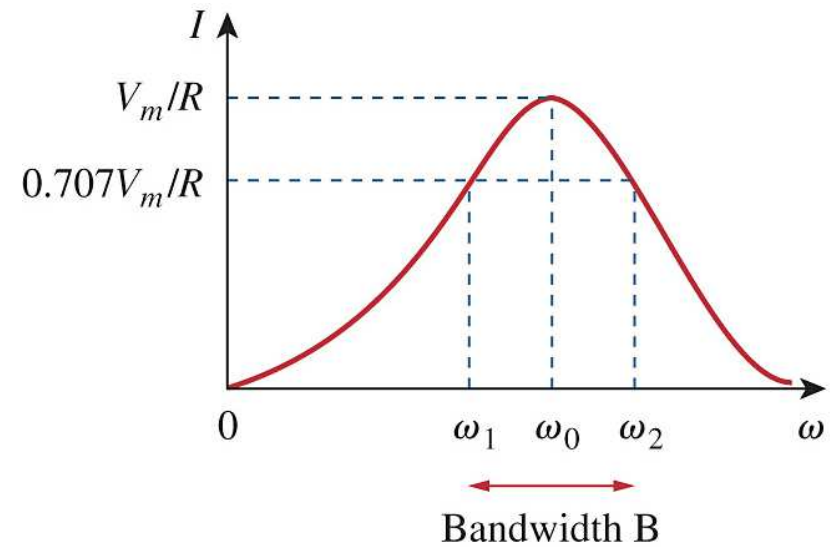


Figure 14.22 The current amplitude versus frequency for the series resonant circuit of Fig. 14.21.

showing that the resonant frequency is the geometric mean of the half-power

frequencies. Notice that ω_1 and ω_2 are in general not symmetrical around ω_0 because

the frequency response is not generally symmetrical. However, if the frequency

axis is a logarithm, we have $\log_{10} \omega_0 =$

$(\log_{10} \omega_1 + \log_{10} \omega_2) / 2$.

NOT arithmetic mean

The *half - power bandwidth* is defined as the difference between the two half-power frequencies,

$$BW = \omega_2 - \omega_1 = \frac{R}{L}$$

The "sharpness" of the resonance is measured quantitatively by the *quality factor* Q .

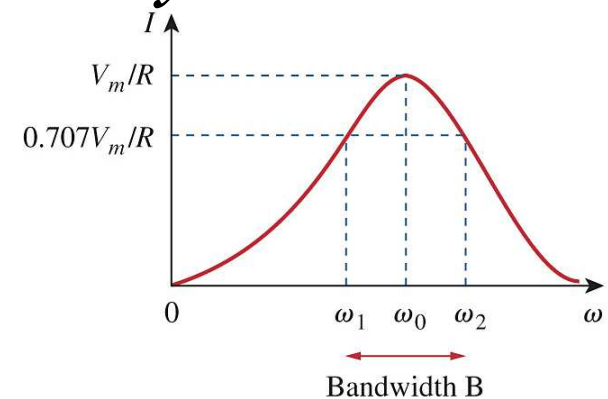


Figure 14.22 The current amplitude versus frequency for the series resonant circuit of Fig. 14.21.

The quality factor Q can be defined by

$$Q = 2\pi \frac{E_s}{E_d}$$

where E_s is the peak energy stored in the circuit and E_d is the energy dissipated in one period at resonance.

$$Q = 2\pi \frac{\frac{1}{2} L I_{\max}^2}{\underbrace{\frac{1}{2} I_{\max}^2 R (1/f_0)}_{E=P \times T}} = \frac{\omega_0 L}{R} \overset{\boxed{L=1/(\omega_0^2 C)}}{=} \frac{1}{\omega_0 R C}$$

Higher Q: more stored energy and/or less loss

The relationship between B and Q is

$$BW = \frac{R}{L} = \frac{\omega_0}{Q} \Rightarrow Q = \frac{\omega_0}{BW}$$

Thus, the quality factor of an RLC circuit can be defined as the ratio of its resonant frequency to its bandwidth.

For same ω ,

$Q \uparrow \Leftrightarrow BW \downarrow \Leftrightarrow \text{sharpness} \uparrow$

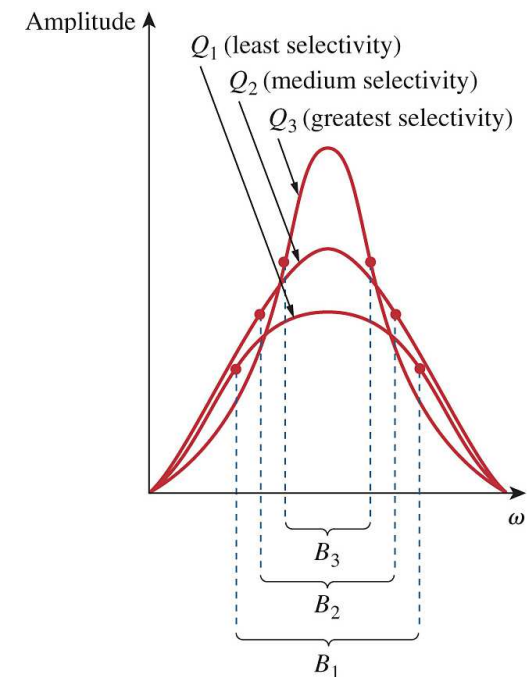


Figure 14.23 The higher the circuit Q , the smaller the bandwidth.

As illustrated in Fig. 14.23, the higher the value of Q , the more selective the circuit is. The *selectivity* of an *RLC* circuit is the ability of the circuit to respond to a certain frequency and discriminate against all other frequencies.

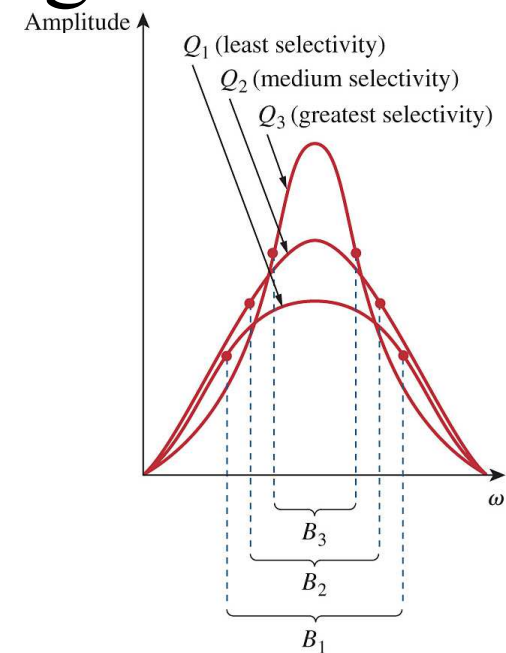


Figure 14.23 The higher the circuit Q , the smaller the bandwidth.

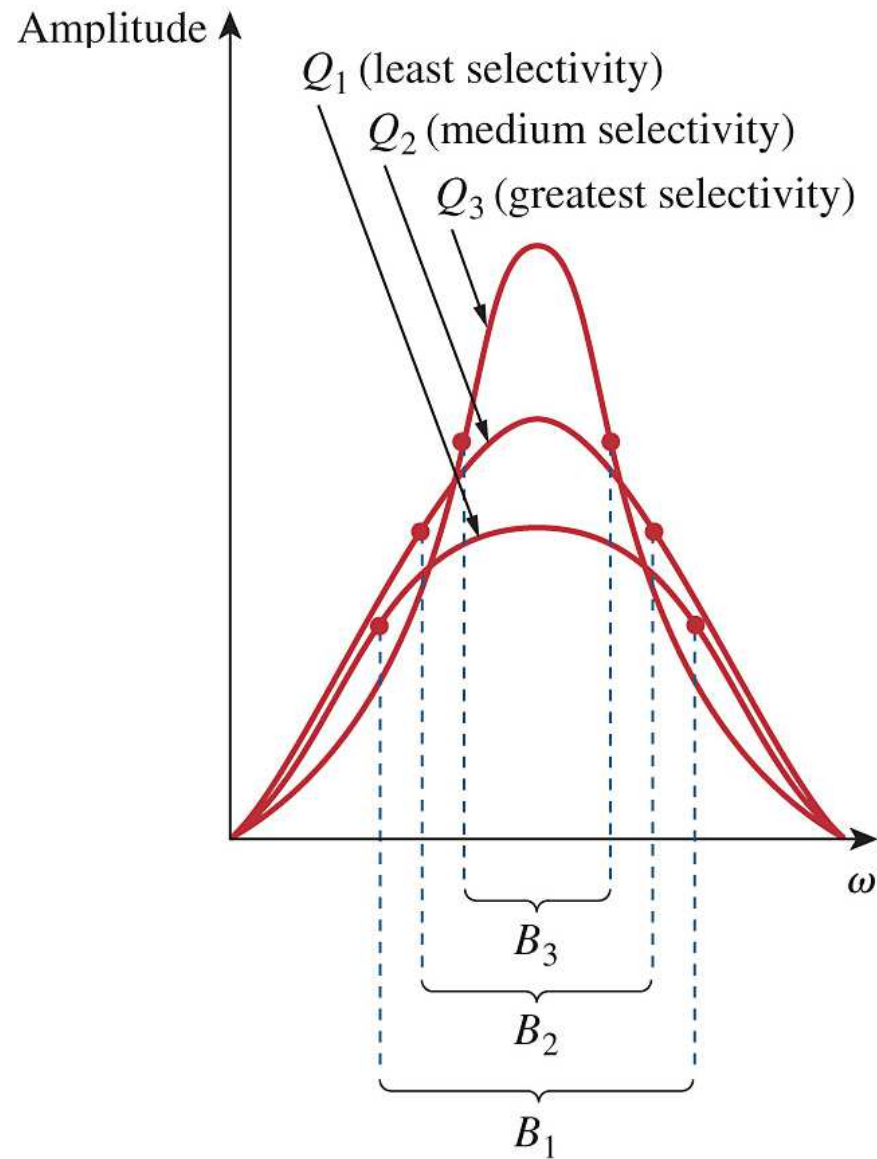


Figure 14.23 The higher the circuit Q , the smaller the bandwidth.

A resonant circuit is designed to operate at or near its resonant frequency. It is said to be a *high-Q circuit* when $Q \geq 10$. For high-Q circuits,

$$\omega_{1,2} = \mp \frac{\omega_0}{2Q} + \omega_0 \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \approx \mp \frac{\omega_0}{2Q} + \omega_0$$

$$= \mp \frac{BW}{2} + \omega_0$$

$$\begin{aligned} \omega_1 &= -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} & Q &= \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} \\ \omega_2 &= \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} & BW &= \frac{R}{L} = \frac{\omega_0}{Q} \end{aligned}$$

The inductor and capacitor voltages can
be much more than the source voltage at
resonance.

$$V_L = \frac{V_m}{R} \omega_0 L = \frac{V_m}{R} \frac{1}{\omega_0 C} = V_C$$

$$|V_C| = |I Z_C| = |I| \times |Z_C|$$

For high-Q circuits, $V_L = V_C = Q V_m$

$$|V_L| = |I Z_L| = |I| \times |Z_L|$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Practice Problem 14.7 A series-connected circuit has $R = 4\ \Omega$ and $L = 25\ \text{mH}$. (a) Calculate the value of C that will produce a quality factor of 50. (b) Find ω_1 , ω_2 , and BW . (c) Determine the average power dissipated at $\omega = \omega_0$, ω_1 , ω_2 . Take $V_m = 100\ \text{V}$.

Solution :

$$(a) \quad Q = \frac{\omega_0 L}{R}$$

$$\omega_0 = \frac{QR}{L} = \frac{50 \times 4}{25 \times 10^{-3}} = 8000 \text{ (rad/s)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{8000^2 \times 25 \times 10^{-3}} \\ = 6.25 \times 10^{-7} \text{ (F)} = 0.625 \mu\text{F}$$

(b)

$$\frac{R}{2L} = \frac{4}{2 \times 25 \times 10^{-3}} = 80 \text{ (rad)}$$

$$\begin{aligned} & \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ &= \sqrt{80^2 + 8000^2} \\ &\approx 8000.40 \text{ (rad)} \end{aligned}$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$= -80 + 8000.40 = 7920.40 \text{ (rad/s)}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$= 80 + 8000.40 = 8080.40 \text{ (rad/s)}$$

$$BW = \omega_2 - \omega_1 = 8080.40 - 7920.40$$

$$= 160 \text{ (rad/s)}$$

(c)

$$P(\omega_0) = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} \times \frac{100^2}{4} = 1250 \text{ (W)}$$

$$P(\omega_1) = P(\omega_2) = \frac{1}{2} P(\omega_0)$$

$$= \frac{1}{2} \times 1250$$

$$= 625 \text{ (W)}$$

14.6 Parallel Resonance

The parallel RLC circuit in Fig. 14.25 is the dual of the series RLC circuit. So we will avoid needless repetition.

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

Resonance occurs when $\text{Im}(Y) = 0$,

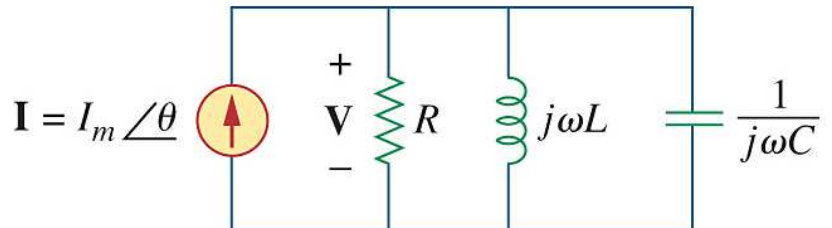
$$\omega_0 C - \frac{1}{\omega_0 L} = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$


Figure 14.25 The parallel resonant circuit.

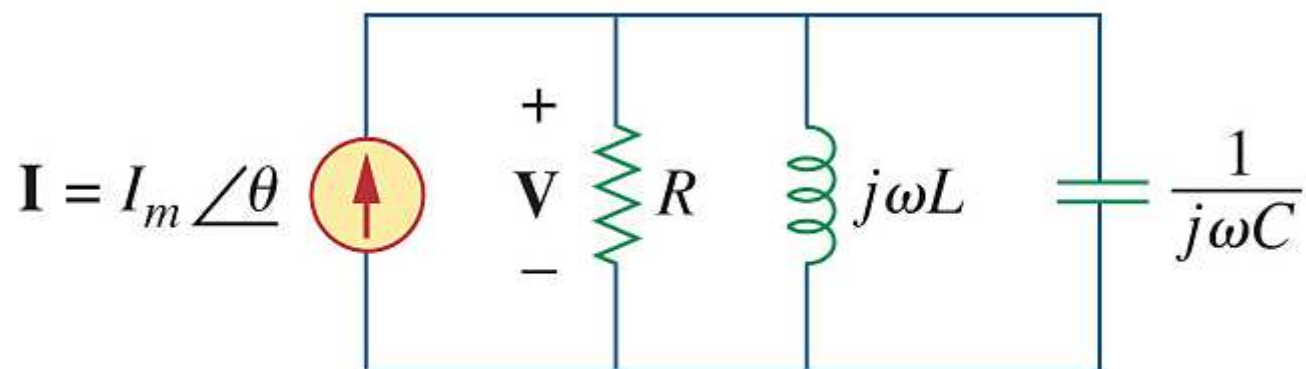


Figure 14.25 The parallel resonant circuit.

The magnitude of voltage V is sketched in Fig. 14.26 as a function of frequency.

Notice that at resonance, the parallel LC combination acts like an open circuit, so $\text{Im}(Y) = 0$ that the entire current flows through R .

Also, the inductor and capacitor currents can be much more than the source current at resonance.

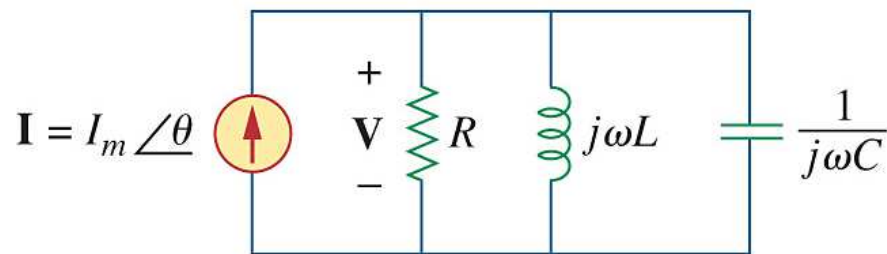


Figure 14.25 The parallel resonant circuit.

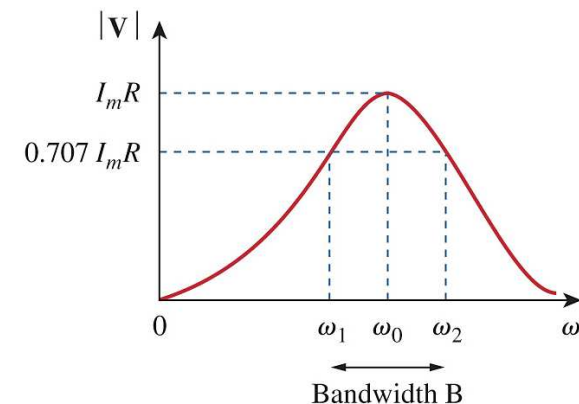


Figure 14.26 The voltage amplitude versus frequency for the parallel resonant circuit of Fig. 14.25.

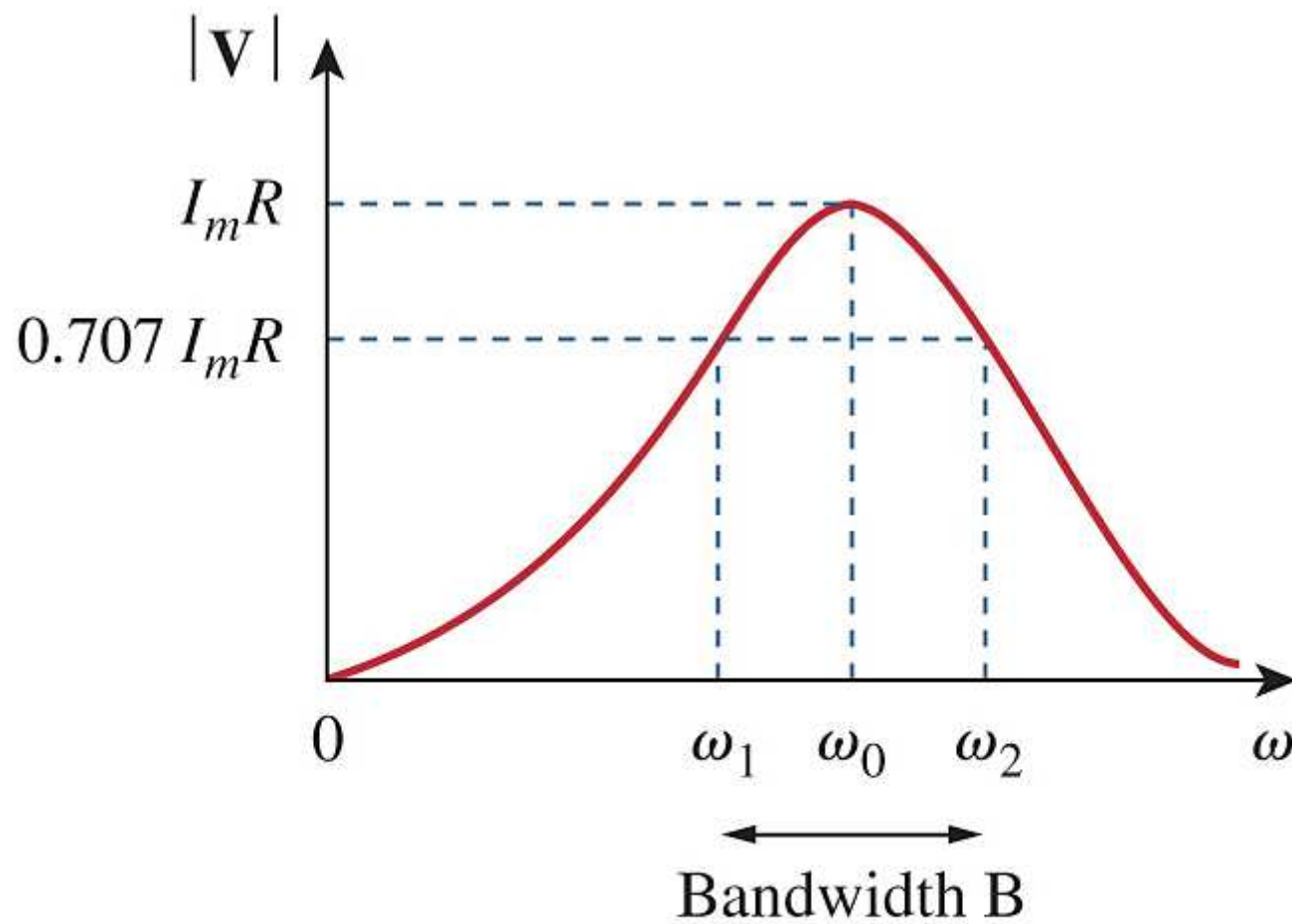


Figure 14.26 The voltage amplitude versus frequency for the parallel resonant circuit of Fig. 14.25.

Recall Chapter 8

TABLE 8.1

Dual pairs.

Resistance R	Conductance G
Inductance L	Capacitance C
Voltage v	Current i
Voltage source	Current source
Node	Mesh
Series path	Parallel path
Open circuit	Short circuit
KVL	KCL
Thevenin	Norton

By exploiting duality, we have

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$BW = \frac{R}{L} = \frac{\omega_0}{Q}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

$$BW = \omega_2 - \omega_1 = \frac{1}{RC}$$

$$Q = \frac{\omega_0}{BW} = \omega_0 RC = \frac{R}{\omega_0 L}$$

Practice Problem 14.8 A parallel resonant circuit has $R = 100 \text{ k}\Omega$ and $L = 20 \text{ mH}$, and $C = 5 \text{ nF}$. Calculate ω_0 , ω_1 , ω_2 , Q , and BW .

Solution :

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$$

$$= 10^5 \text{ (rad/s)}$$

$$\frac{1}{2RC} = \frac{1}{2 \times 100 \times 10^3 \times 5 \times 10^{-9}} = 1000 \text{ (rad/s)}$$

$$\sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} = \sqrt{1000^2 + (10^5)^2}$$
$$\approx 100,005.00 \text{ (rad/s)}$$

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$= -1000 + 100,005.00 = 99,005.00 \text{ (rad/s)}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$= 1000 + 100,005.00 = 101,005.00 \text{ (rad/s)}$$

$$BW = \omega_2 - \omega_1 = 101,005.00 - 99,005.00$$

$$= 2000 \text{ (rad/s)}$$

$$Q = \frac{\omega_0}{B} = \frac{10^5}{2000} = 50$$

Practice Problem 14.9 Calculate the resonant frequency of the circuit in Fig. 14.29. A more general case

Solution :

$$Z = j\omega L + R \parallel \frac{1}{j\omega C} = j\omega L + \frac{R}{1 + j\omega RC}$$

$$= j\omega L + \frac{R - j\omega R^2 C}{1 + (\omega RC)^2}$$

$$= \frac{R}{1 + (\omega RC)^2} + j \left(\omega L - \frac{\omega R^2 C}{1 + (\omega RC)^2} \right)$$

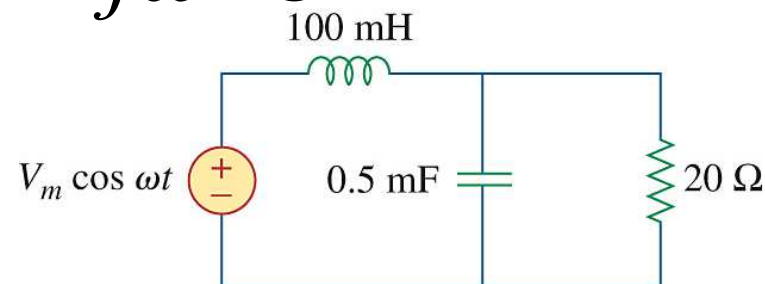


Figure 14.29

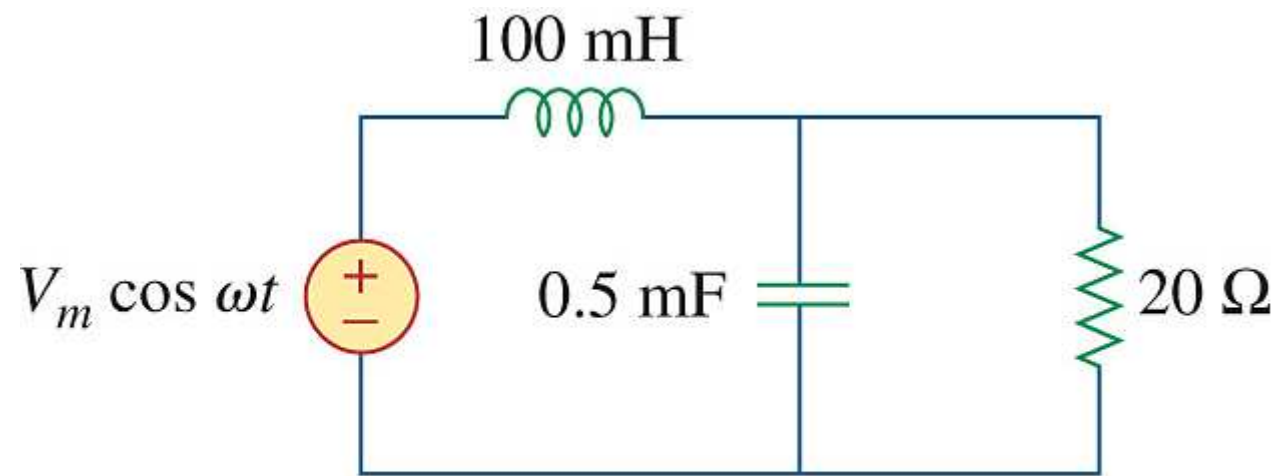


Figure 14.29

When $\omega = \omega_0$, $\text{Im}(Z) = 0$,

$$\omega_0 L - \frac{\omega_0 R^2 C}{1 + (\omega_0 RC)^2} = 0$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{1}{(RC)^2}}$$

$$= \sqrt{\frac{1}{100 \times 10^{-3} \times 0.5 \times 10^{-3}} - \frac{1}{(20 \times 0.5 \times 10^{-3})^2}}$$

$$= 100 \text{ (rad/s)}$$

14.7 Passive Filters


A *filter* is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.

A filter is a *passive filter* if it consists of only passive elements R , L , and C . It is said to be an *active filter* if it consists of active elements in addition to passive elements.

As shown in Fig. 14.30, there are four types of filters whether passive or active:

1. A *lowpass filter* passes low frequencies and rejects high frequencies, as shown ideally in Fig. 14.30(a).

2. A *highpass filter* passes high frequencies and rejects low frequencies, as shown ideally in Fig. 14.30(b).

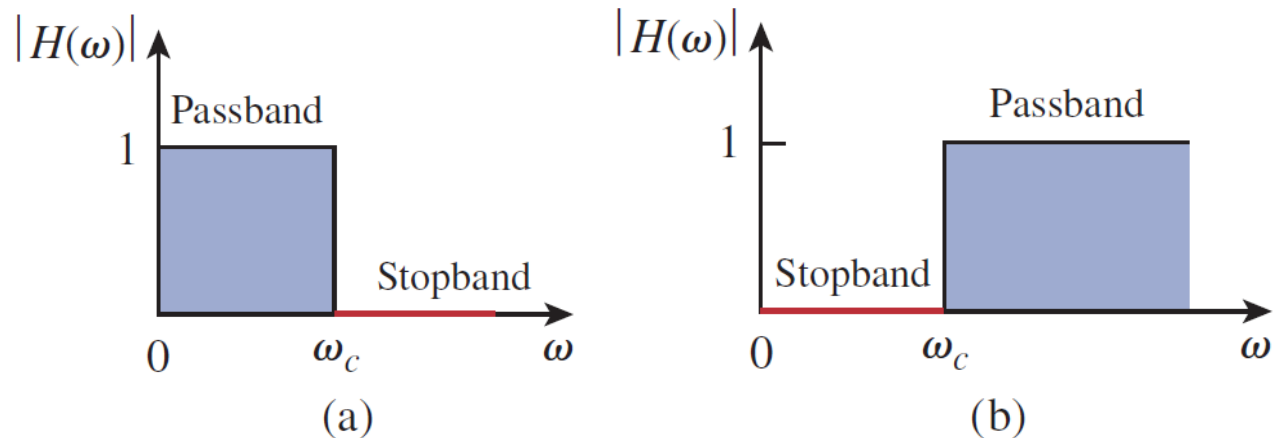


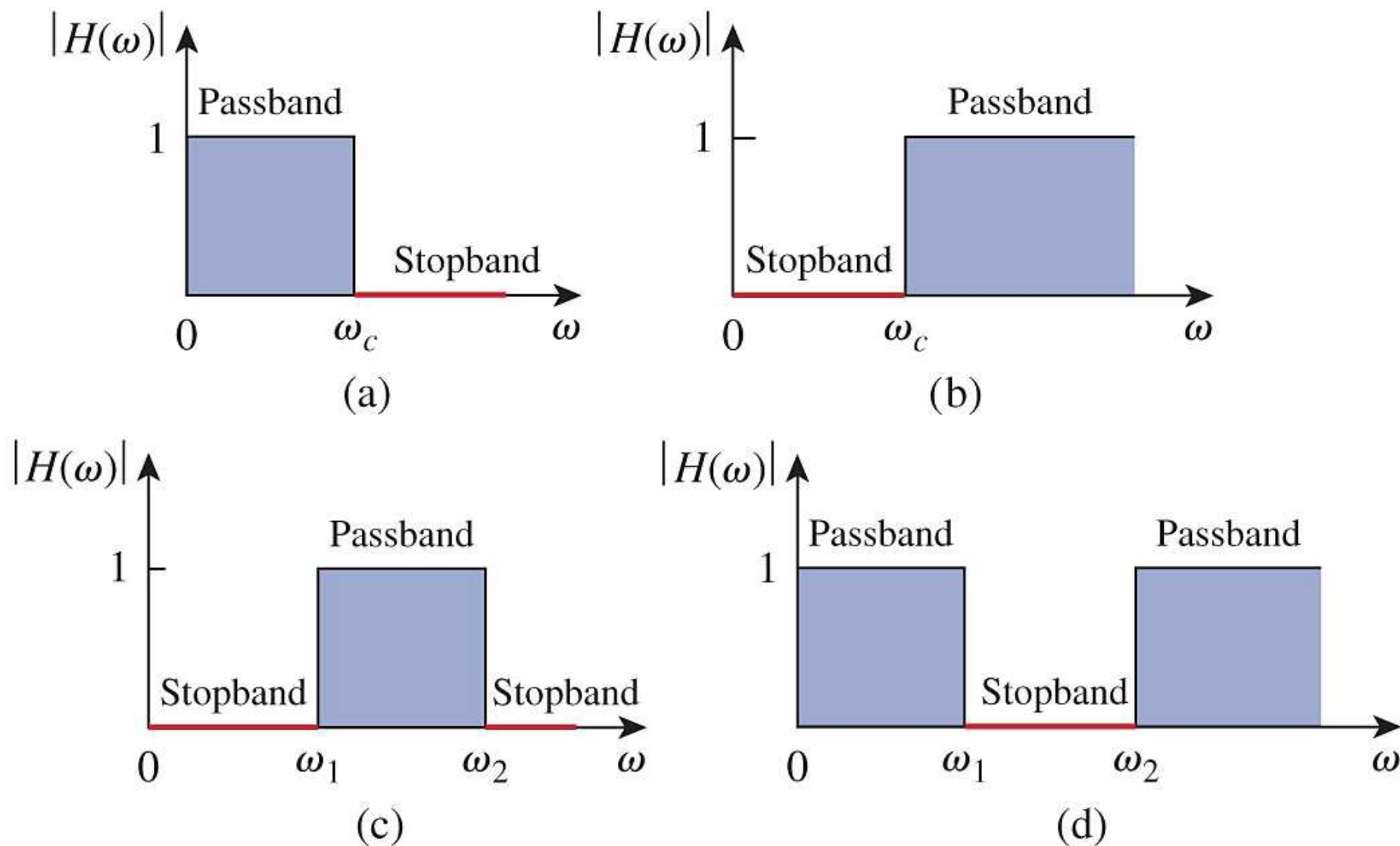


Figure 14.30 Ideal frequency response of four types of filter: (a) lowpass filter, (b) highpass filter, (c) bandpass filter, (d) bandstop filter.

3. A *bandpass filter* passes frequencies within a frequency band and blocks frequencies outside the band, as shown ideally in Fig. 14.30(c).

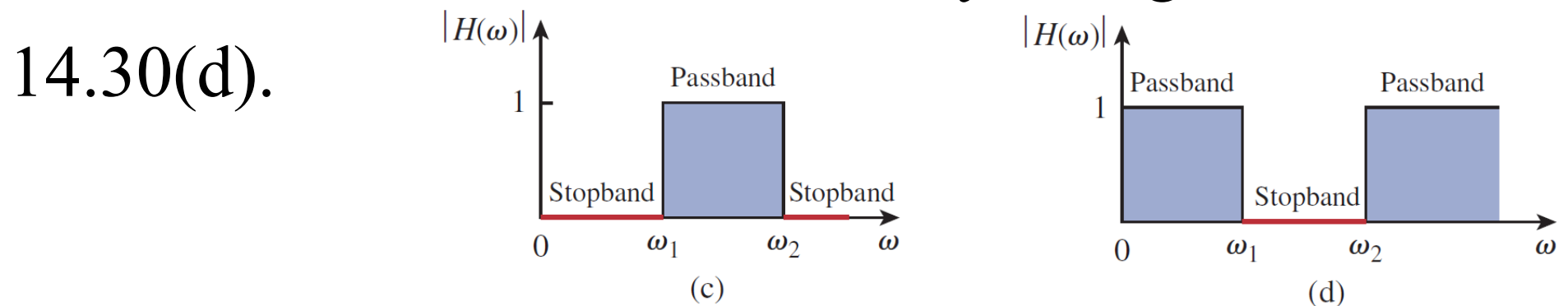2. A *bandstop filter* (or *bandreject filter*, or *notch filter*) passes frequencies outside a frequency band and blocks frequencies within the band, as shown ideally in Fig.



Lowpass Filter Figure 14.31 shows a lowpass filter. The frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{1 + j\omega RC}$$

Figure 14.32 shows the plot of $|H(j\omega)|$, along with the ideal characteristic.

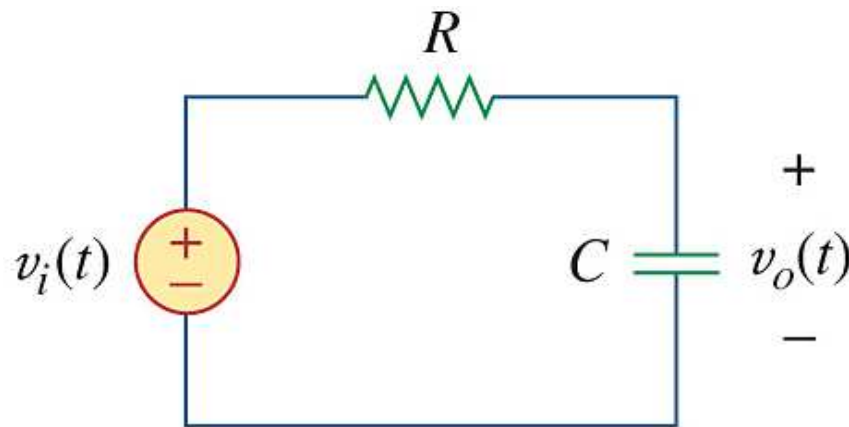


Figure 14.32 A lowpass filter.

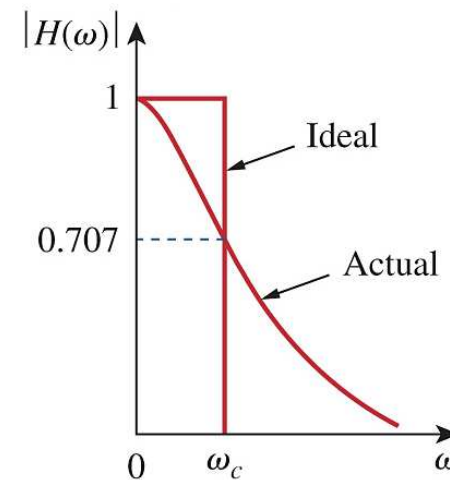


Figure 14.32 Ideal and actual frequency response of a lowpass filter.

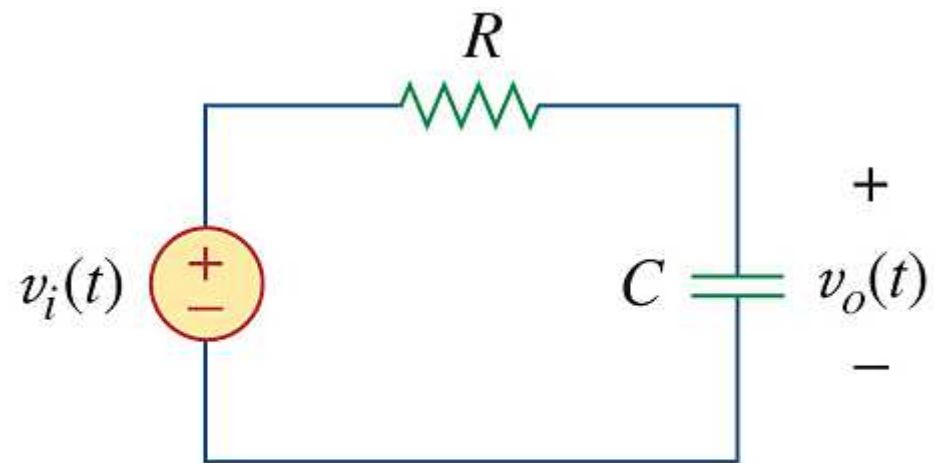


Figure 14.32 A lowpass filter.

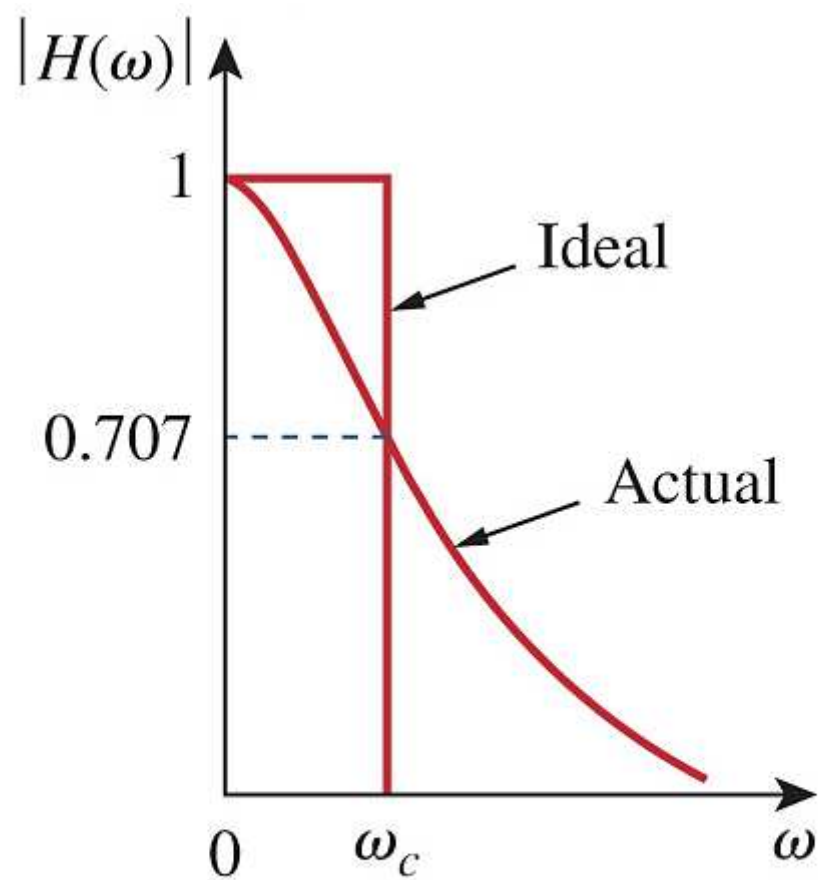


Figure 14.32 Ideal and actual frequency response of a lowpass filter.

The half-power frequency, which is equivalent to the corner frequency on the Bode plots but in the context of filters is usually known as the cutoff frequency ω_c , is obtained by setting $|H(j\omega)| = 1 / \sqrt{2}$,

$$|H(j\omega_c)| = \left| \frac{1}{1 + j\omega_c RC} \right| = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{1}{RC}$$

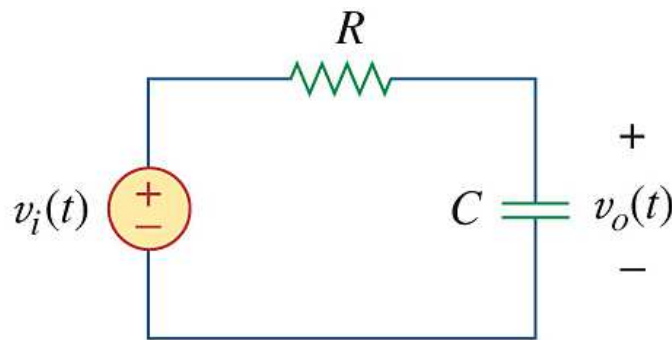


Figure 14.32 A lowpass filter.

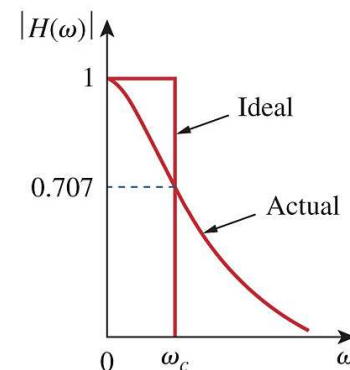


Figure 14.32 Ideal and actual frequency response of a lowpass filter.

Highpass Filter Figure 14.33 shows a highpass filter. The frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega RC}{1 + j\omega RC}$$

Figure 14.34 shows the plot of $|H(j\omega)|$.

Again, the cutoff frequency is $\omega_c = \frac{1}{RC}$.

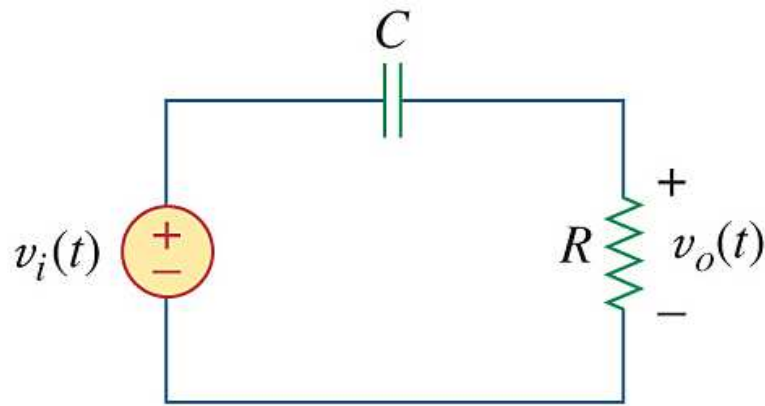


Figure 14.34 A highpass filter.

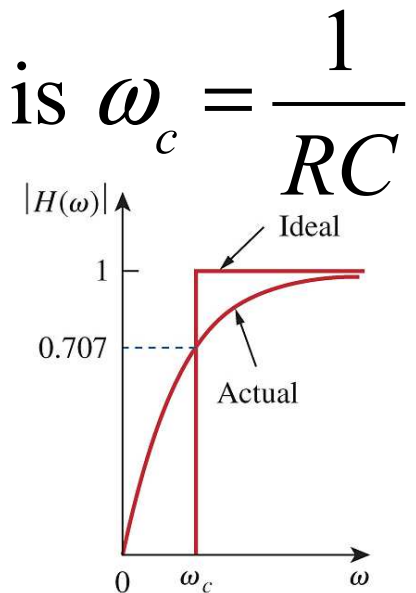


Figure 14.34 Ideal and actual frequency response of a highpass filter.

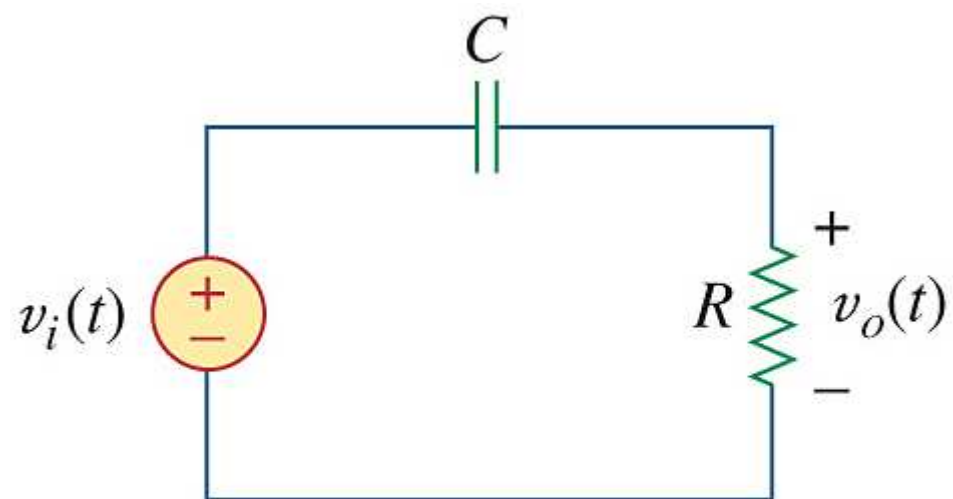


Figure 14.34 A highpass filter.

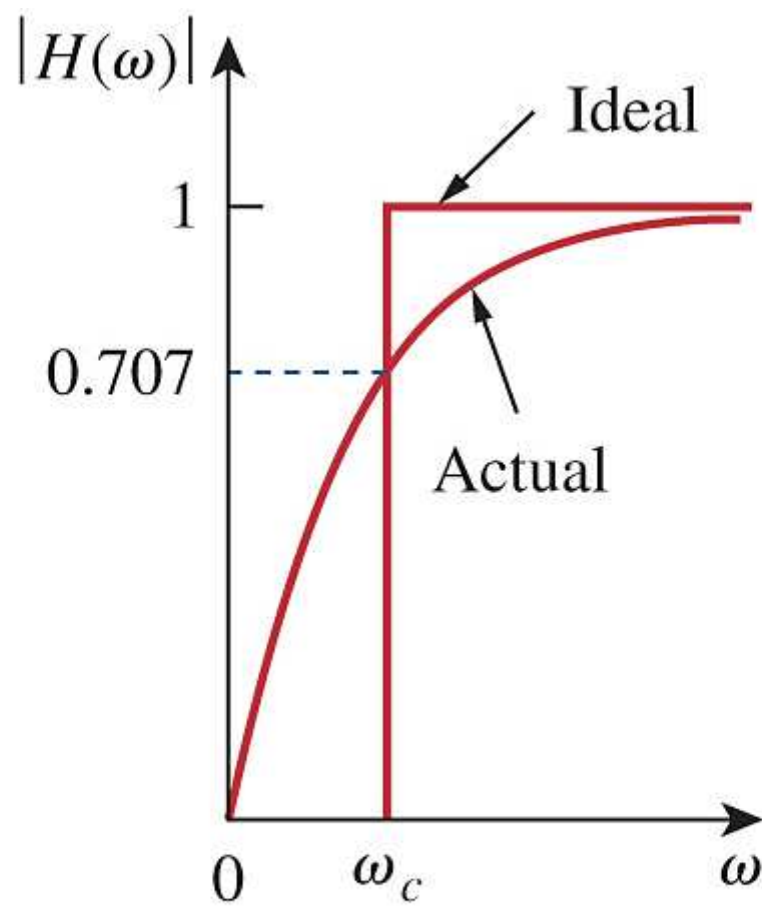


Figure 14.34 Ideal and actual frequency response of a highpass filter.

Bandpass Filter Figure 14.35 shows a bandpass filter. The frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

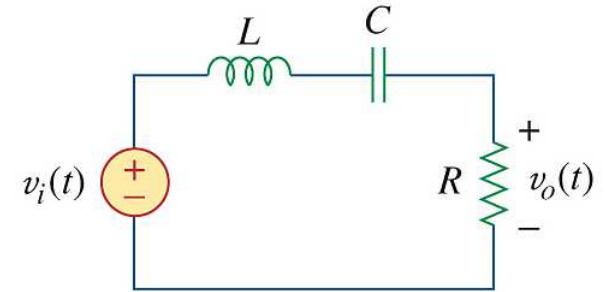


Figure 14.35 A bandpass filter.

Figure 14.36 shows the plot of $|H(j\omega)|$.

ω_0 is called the *center frequency*. ω_1 is called the *lower cutoff frequency*. ω_2 is called the *upper cutoff frequency*.

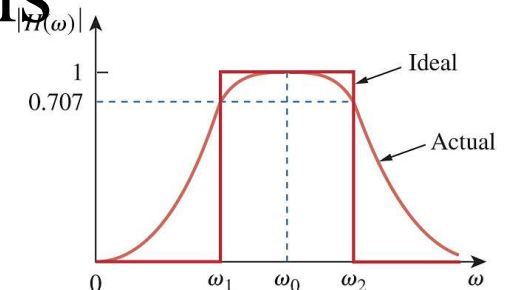


Figure 14.36 Ideal and actual frequency response of a bandpass filter.

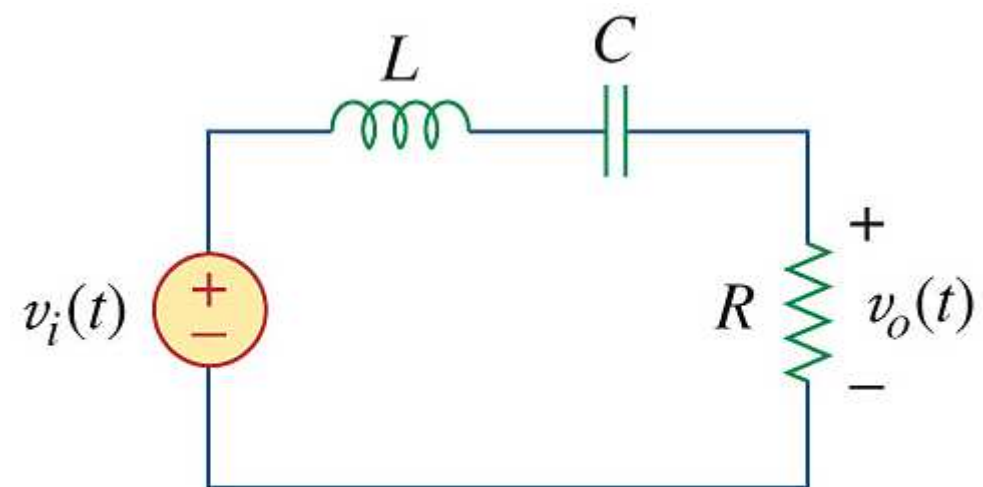


Figure 14.35 A bandpass filter.

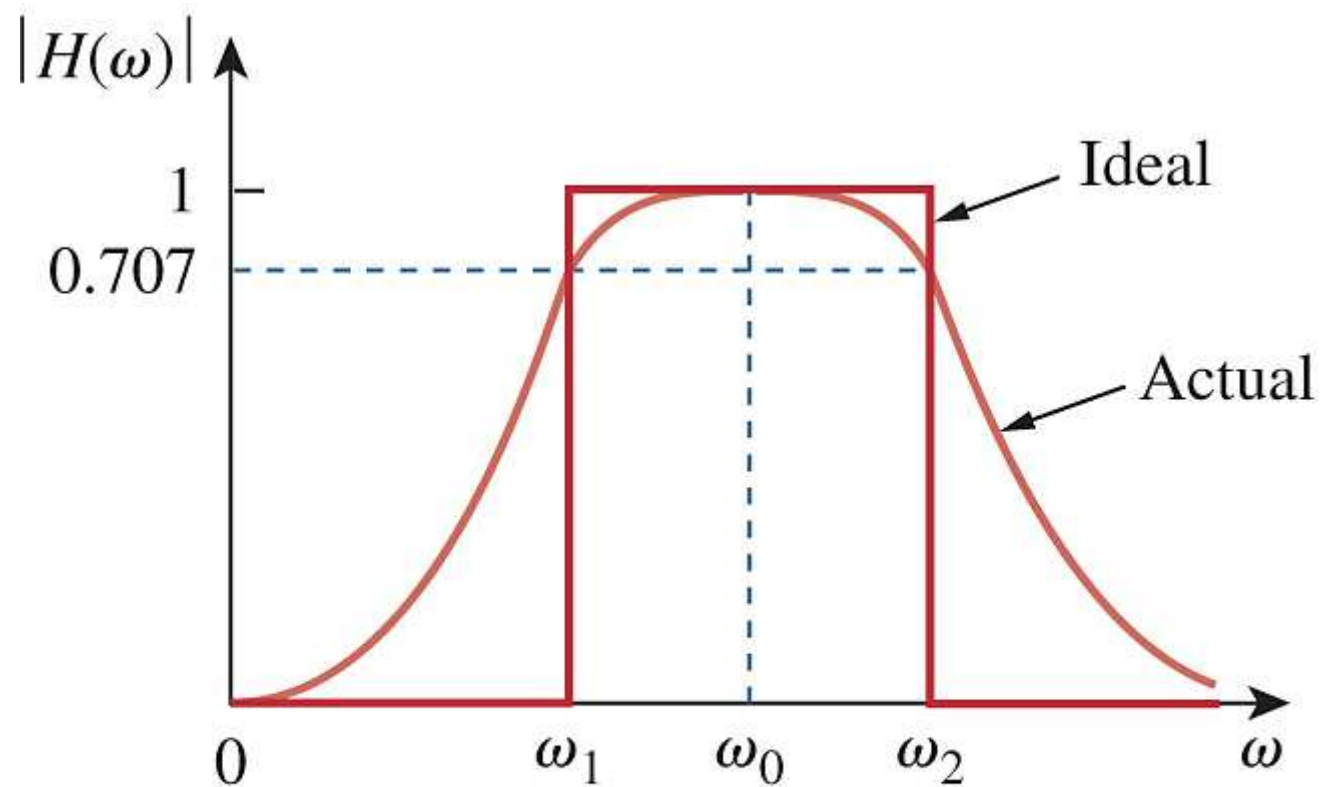


Figure 14.36 Ideal and actual frequency response of a bandpass filter.

Bandstop Filter Figure 14.37 shows a bandstop filter. The frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j[\omega L - 1/(\omega C)]}{R + j[\omega L - 1/(\omega C)]}$$

Figure 14.38 shows the plot of $|H(j\omega)|$.

Again, ω_0 is the center frequency. ω_1 and ω_2 are the cutoff frequencies.

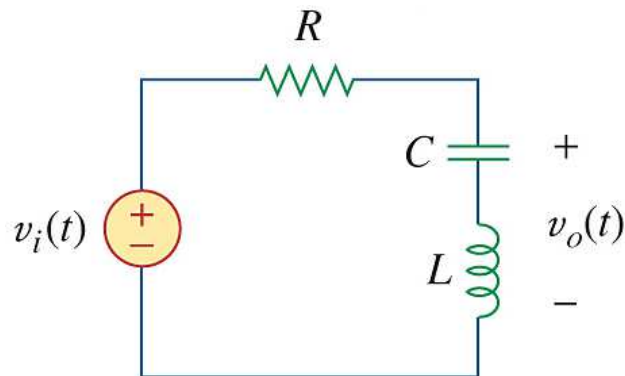


Figure 14.37 A bandstop filter.

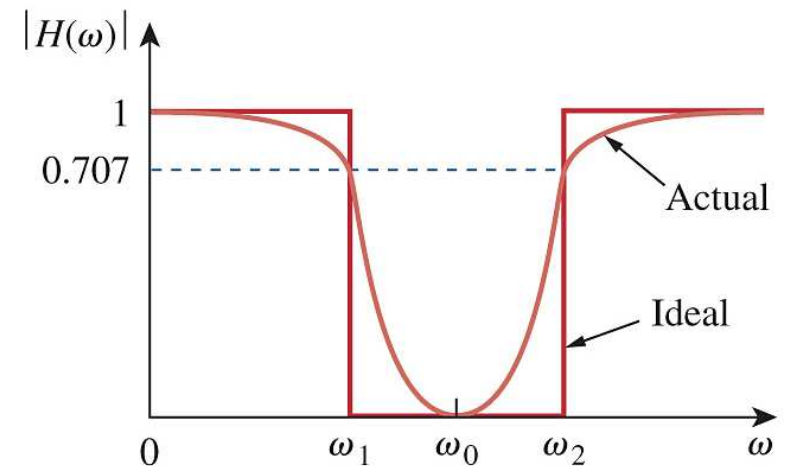


Figure 14.38 Ideal and actual frequency response of a bandstop filter.

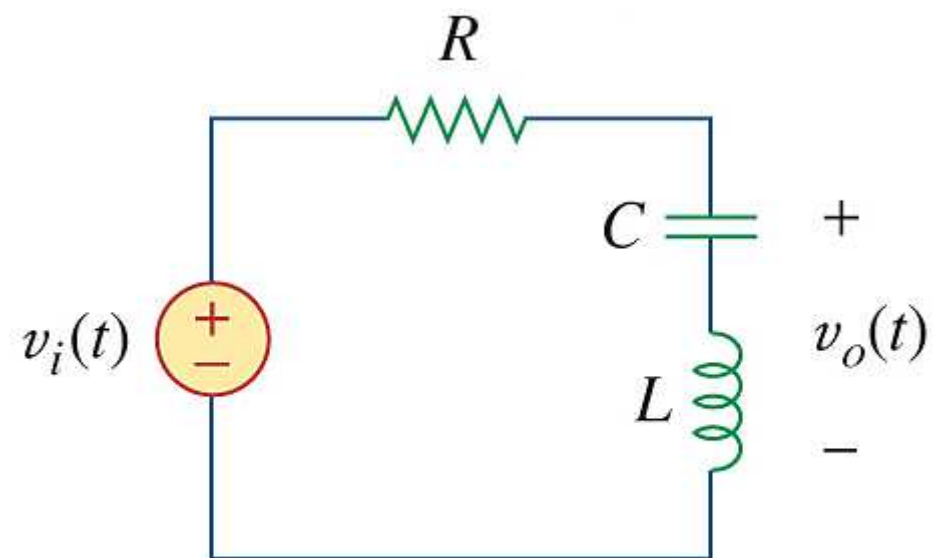


Figure 14.37 A bandstop filter.

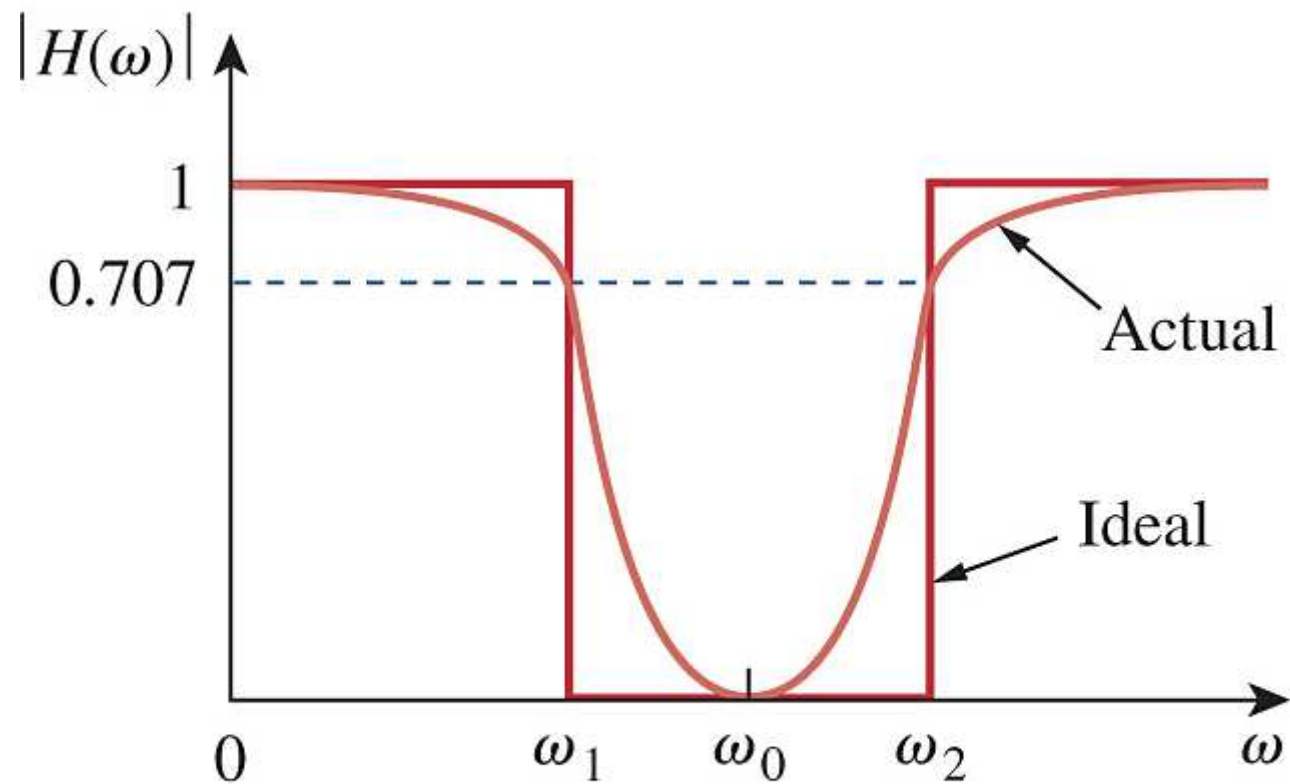


Figure 14.38 Ideal and actual frequency response of a bandstop filter.

The bandpass filter and the bandstop filter are complementary.

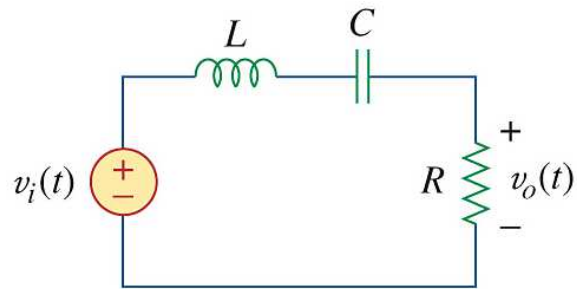


Figure 14.35 A bandpass filter.

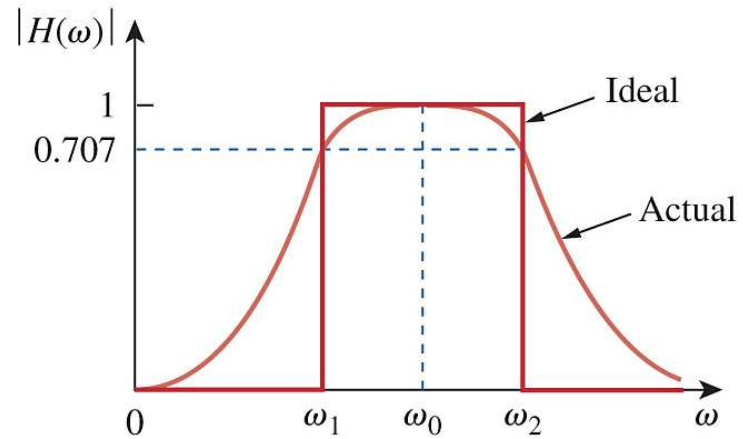


Figure 14.36 Ideal and actual frequency response of a bandpass filter.

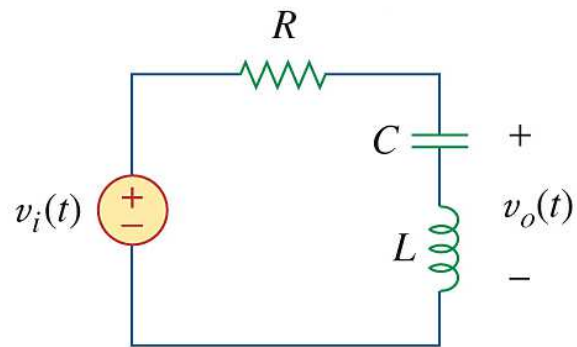


Figure 14.37 A bandstop filter.

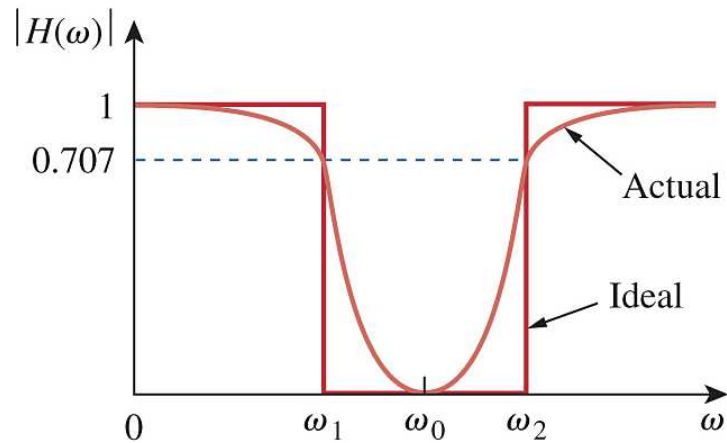


Figure 14.38 Ideal and actual frequency response of a bandstop filter.

Practice Problem 14.10 For the circuit in Fig 14.40, obtain the frequency response $V_o(j\omega) / V_i(j\omega)$. Identify the type of filter the circuit represents and determine the cutoff frequency. Take $R_1 = R_2 = 100 \, \Omega$, $L = 2 \, \text{mH}$.

Solution :

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_2 \parallel (j\omega L)}{R_1 + R_2 \parallel (j\omega L)}$$

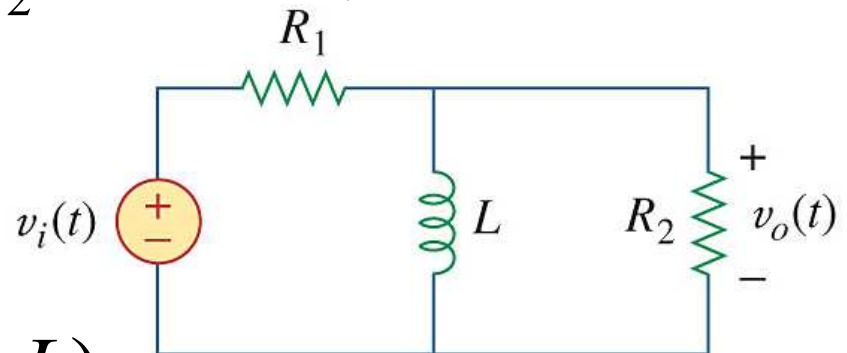


Figure 14.40

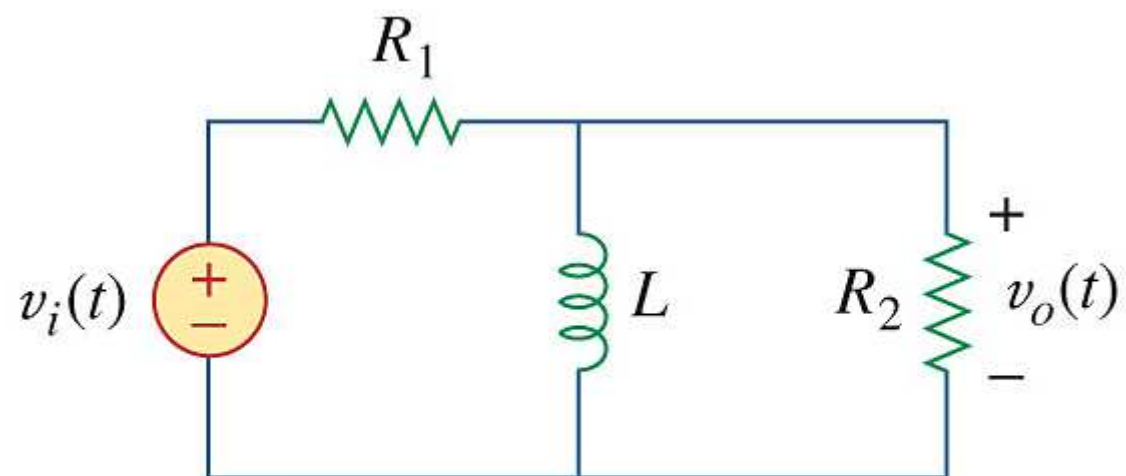


Figure 14.40

$$\begin{aligned}
&= \frac{j\omega R_2 L}{R_1 R_2 + j\omega(R_1 + R_2)L} \\
&= \frac{R_2}{R_1 + R_2} \frac{j\omega L}{\frac{R_1 R_2}{R_1 + R_2} + j\omega L} \\
&= \frac{R_2}{R_1 + R_2} \frac{j\omega L}{R_1 \parallel R_2 + j\omega L} \\
&= \frac{R_2}{R_1 + R_2} \frac{j\omega L / (R_1 \parallel R_2)}{1 + j\omega L / (R_1 \parallel R_2)}
\end{aligned}$$

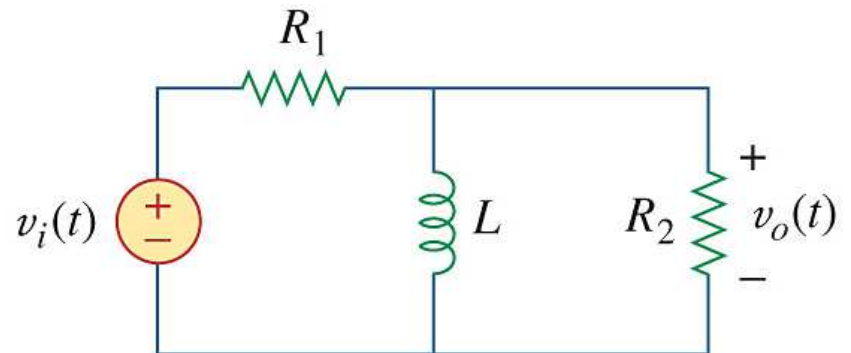


Figure 14.40

Recall highpass filter $H(j\omega)$

$$H(j\omega) = \frac{\tilde{V}_o(j\omega)}{\tilde{V}_i(j\omega)} = \frac{j\omega RC}{1 + j\omega RC}$$

$$= \frac{R_2}{R_1 + R_2} \frac{j\omega / \omega_c}{1 + j\omega / \omega_c}$$

Recall highpass filter $H(j\omega)$

$$H(j\omega) = \frac{\tilde{V}_o(j\omega)}{\tilde{V}_i(j\omega)} = \frac{j\omega RC}{1 + j\omega RC}$$

It is a highpass filter with a cutoff frequency of

$$\omega_c = \frac{R_1 \parallel R_2}{L} = \frac{100 \parallel 100}{2 \times 10^{-3}}$$

$$= 25,000 \text{ (rad/s)}$$

Question : What is the magnitude Bode Plot?

14.8 Active Filters

Active filters consists of combinations of resistors, capacitors, and op amps. They offer some advantages over passive filters: First, they are often smaller and less expensive. Second, they can provide gain. Third, they can be combined with buffer amplifiers to isolate each stage of the filter from source and load impedance effects.

However, active filters are less reliable and less stable. The practical limit of most active filters is about 100 kHz – most active filters operate well below that frequency.

First - Order Lowpass Filter Figure 14.42 shows a first-order op amp circuit. It is used as an active low-pass filter. The frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f \parallel [1 / (j\omega C_f)]}{R_i}$$

Inverting amplifier:
 $H(j\omega) = -Z_f/Z_1$

$$= -\frac{R_f}{R_i} \frac{1}{1 + j\omega R_f C_f} = -\frac{R_f}{R_i} \frac{1}{1 + j\omega / \omega_c}$$

$$\omega_c = 1 / (R_f C_f)$$

Recall lowpass filter $H(j\omega)$

$$H(j\omega) = \frac{\tilde{V}_o(j\omega)}{\tilde{V}_i(j\omega)} = \frac{1}{1 + j\omega RC}$$

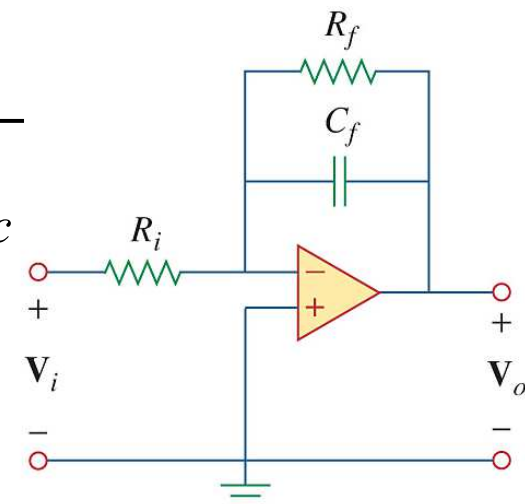


Figure 14.42 Active first-order lowpass filter.

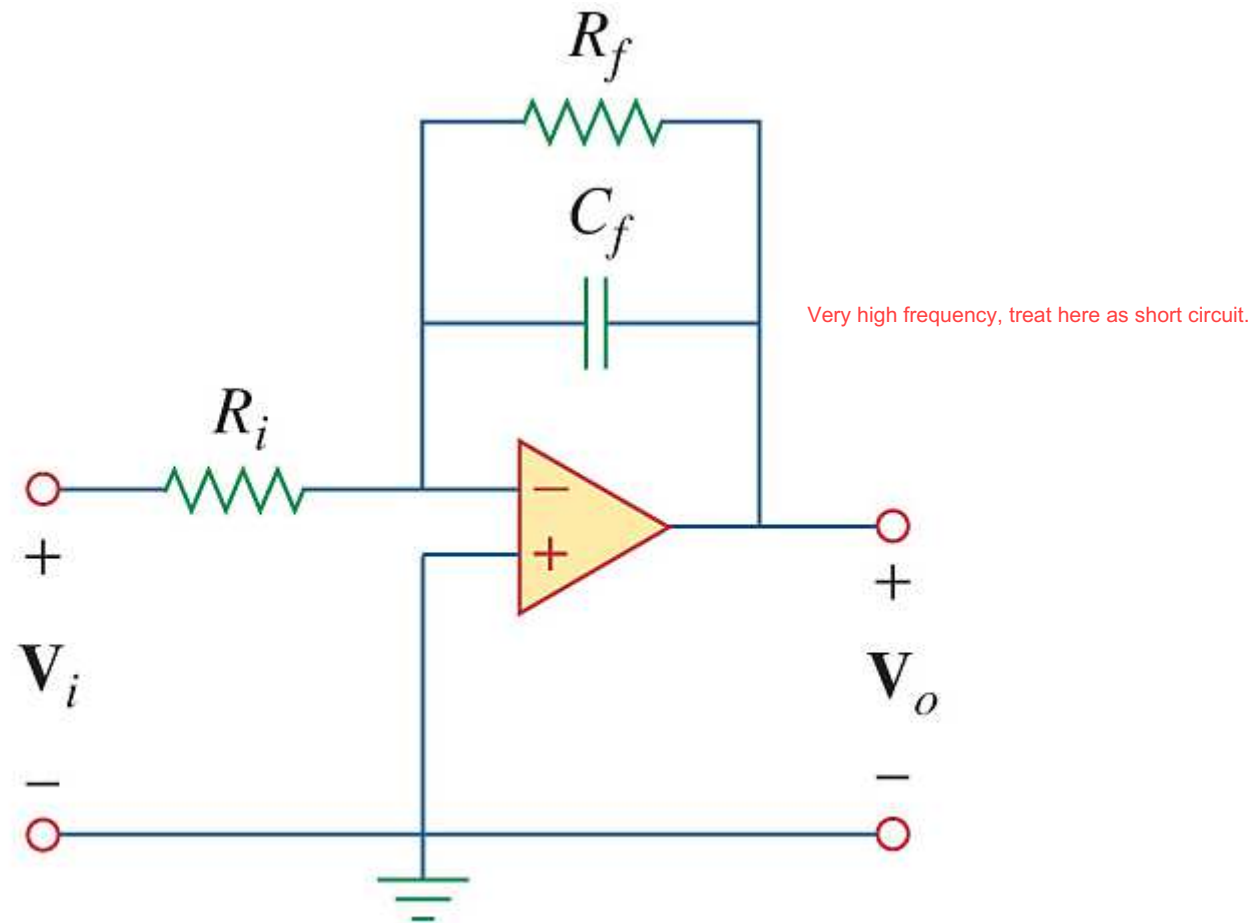


Figure 14.42 Active first-order lowpass filter.

First - Order Highpass Filter Figure 14.43 shows an active first-order high-pass filter. The frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{R_f}{R_i + 1/(j\omega C_i)}$$

Inverting amplifier:
 $H(j\omega) = -Z_f/Z_1$

$$= -\frac{R_f}{R_i} \frac{1}{1 + 1/(j\omega R_i C_i)} = -\frac{R_f}{R_i} \frac{j\omega / \omega_c}{1 + j\omega / \omega_c}$$

$$\omega_c = 1/(R_i C_i)$$

Recall highpass filter $H(j\omega)$

$$H(j\omega) = \frac{\tilde{V}_o(j\omega)}{\tilde{V}_i(j\omega)} = \frac{j\omega RC}{1 + j\omega RC}$$

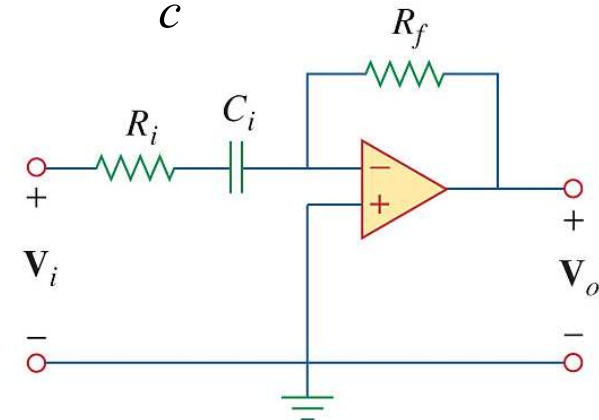


Figure 14.43 Active first-order highpass filter.

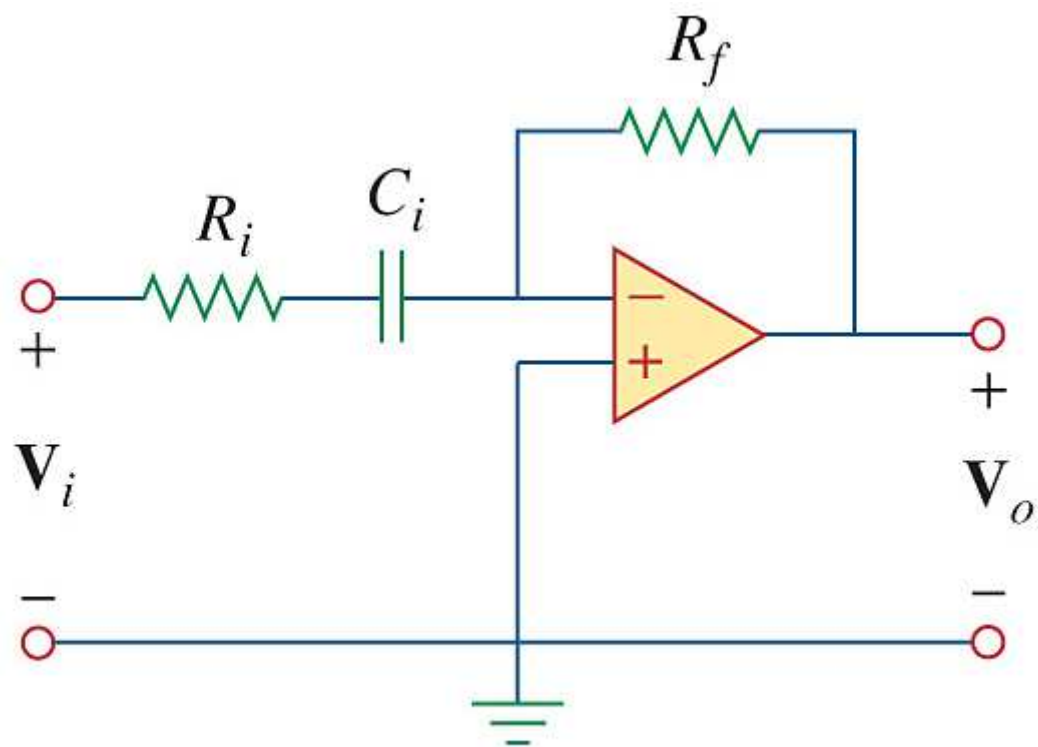


Figure 14.43 Active first-order highpass filter.

Bandpass Filter By cascading a unity-gain lowpass filter, a unity-gain highpass filter, and an inverter with gain $-R_f / R_i$, as shown in Fig. 14.44(a), we can construct a bandpass filter whose frequency response is that in Fig. 14.44(b).

Question : Why?

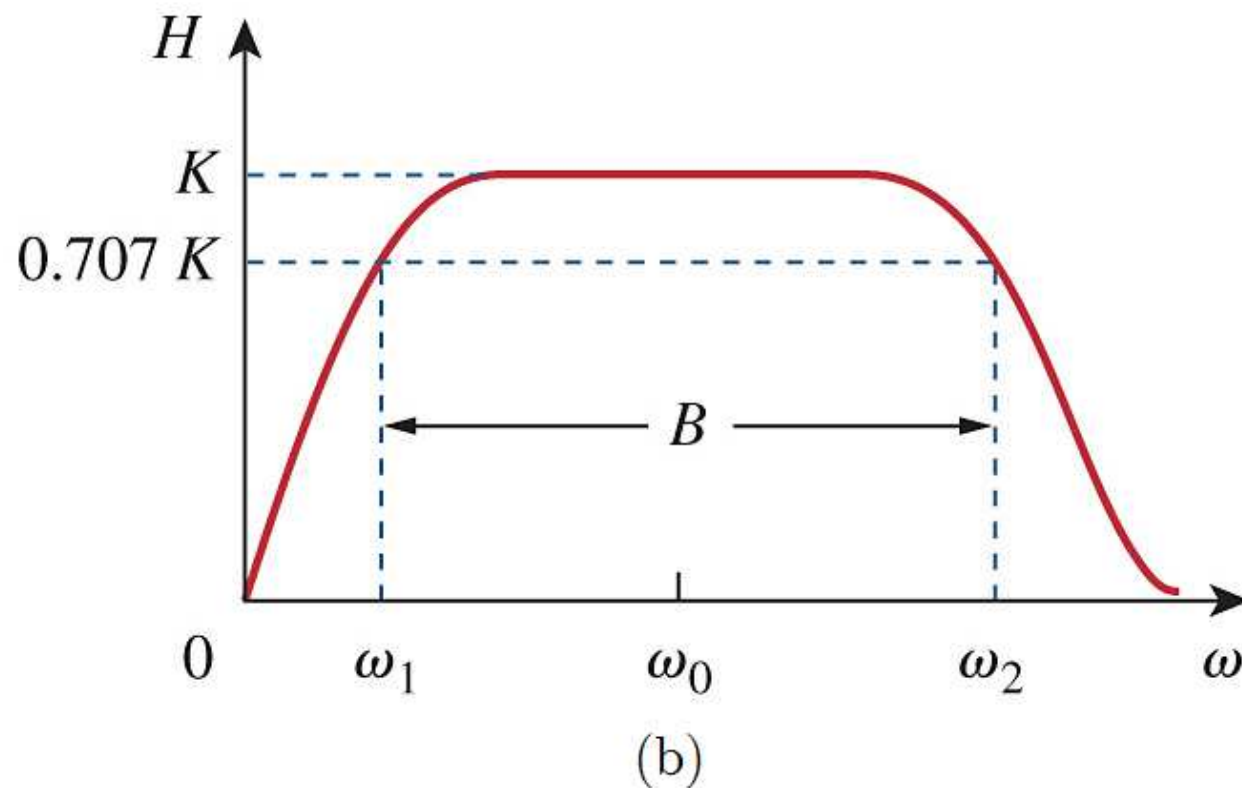
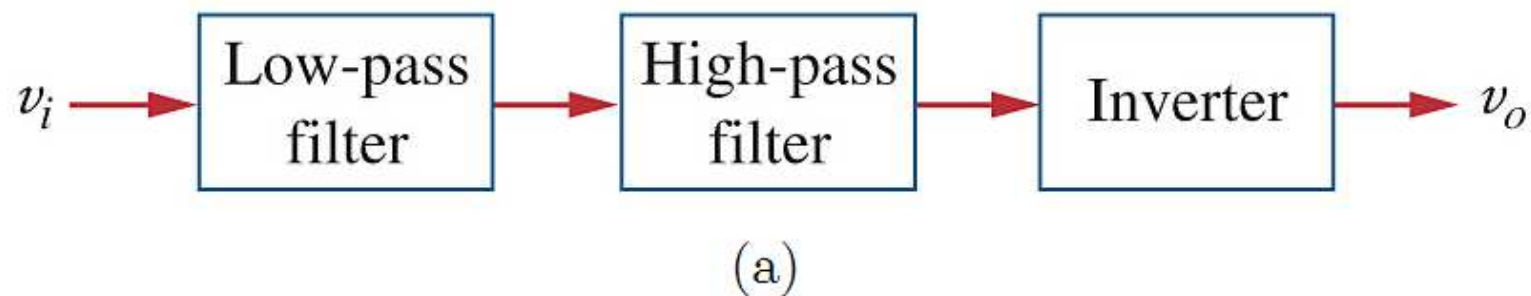


Figure 14.44 Active bandpass filter: (a) block diagram, (b) frequency response.

The actual construction of the bandpass filter is shown in Fig. 14.45. Its frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$$

$$= \left(-\frac{R}{R} \frac{1}{1 + j\omega RC_1} \right) \left(-\frac{R}{R} \frac{j\omega RC_2}{1 + j\omega RC_2} \right) \left(-\frac{R_f}{R_i} \right)$$

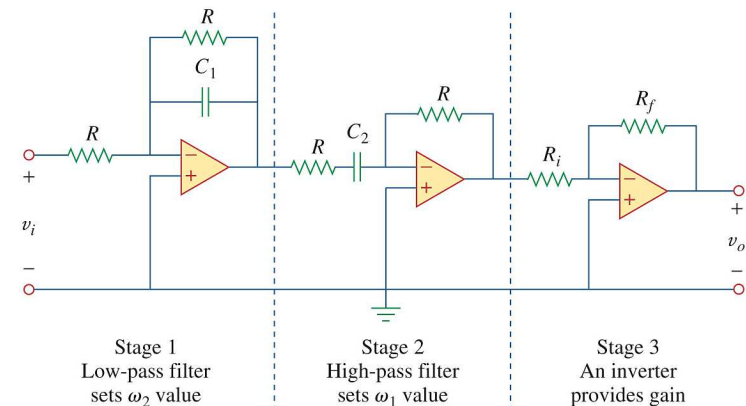


Figure 14.45 Active bandpass filter.


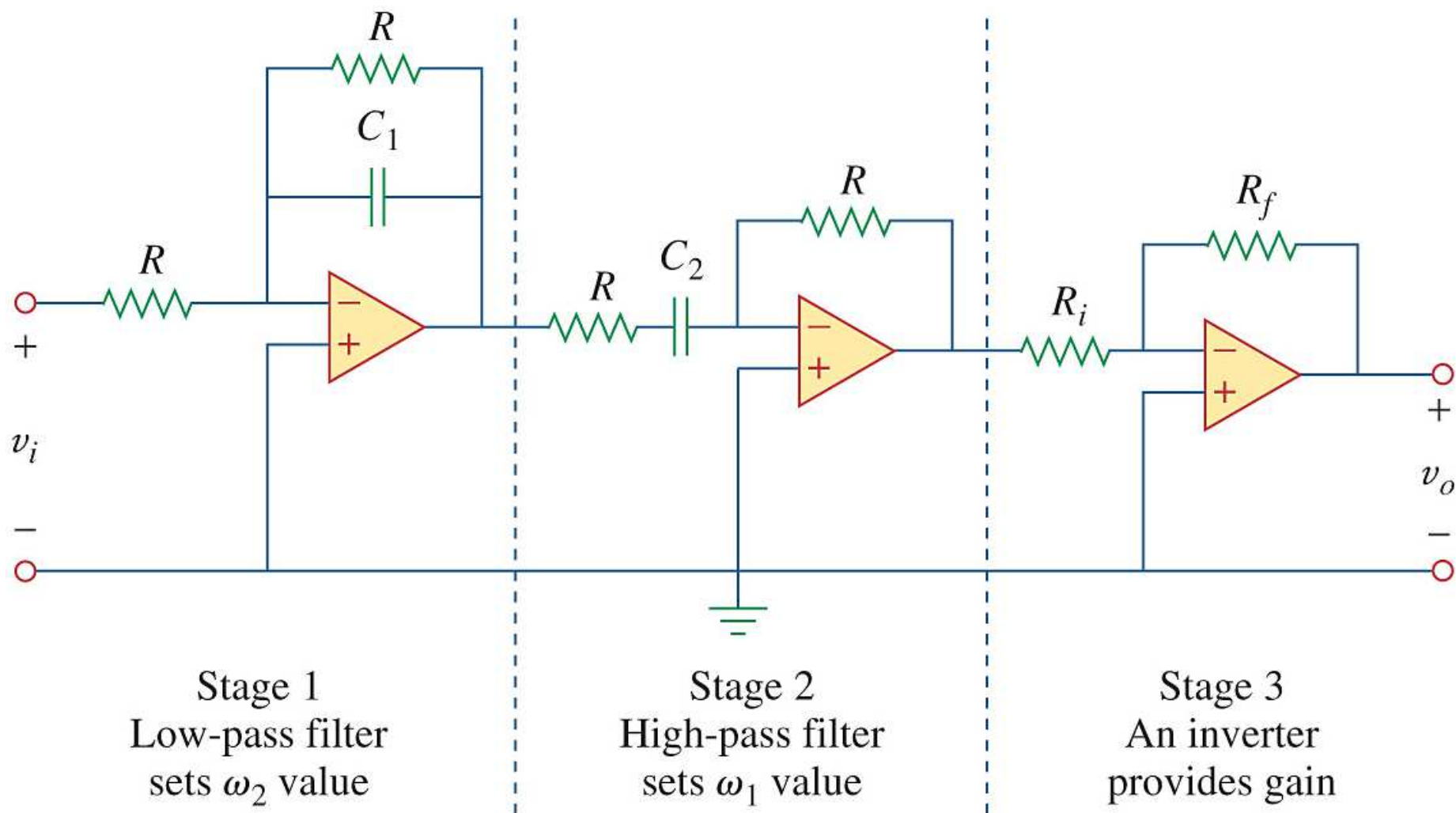


Figure 14.45 Active bandpass filter.
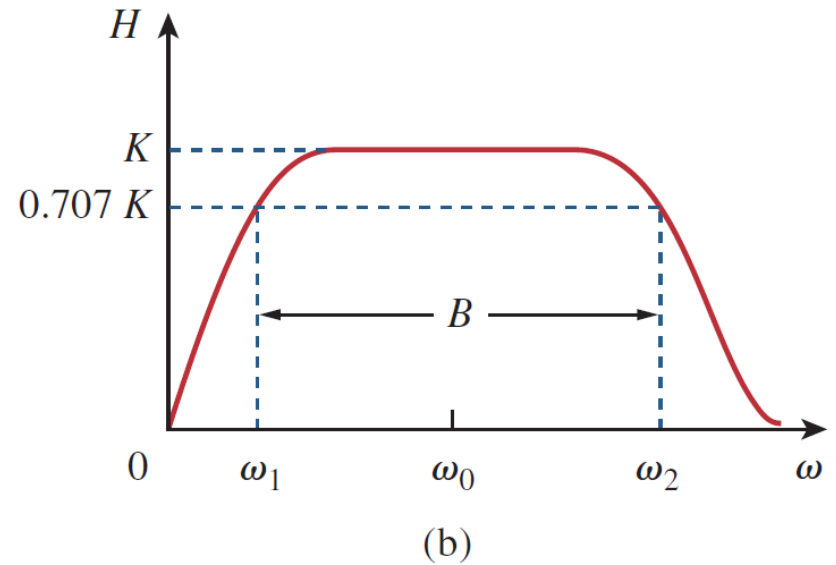
$$\begin{aligned}
&= -\frac{R_f}{R_i} \frac{1}{1 + j\omega RC_1} \frac{j\omega RC_2}{1 + j\omega RC_2} \\
&= -\frac{R_f}{R_i} \frac{1}{1 + j\omega / \omega_2} \frac{j\omega / \omega_1}{1 + j\omega / \omega_1} \\
&= -\frac{R_f}{R_i} \frac{j\omega / \omega_1}{(1 + j\omega / \omega_1)(1 + j\omega / \omega_2)}
\end{aligned}$$



The lowpass section sets the upper cutoff frequency as $\omega_2 = 1 / (RC_1)$. The highpass section sets the lower cutoff frequency as $\omega_1 = 1 / (RC_2)$.


Question : What is the magnitude Bode plot for the bandpass filter?

The center frequency of the bandpass filter is

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

The bandwidth of the bandpass filter is

$$BW = \omega_2 - \omega_1$$

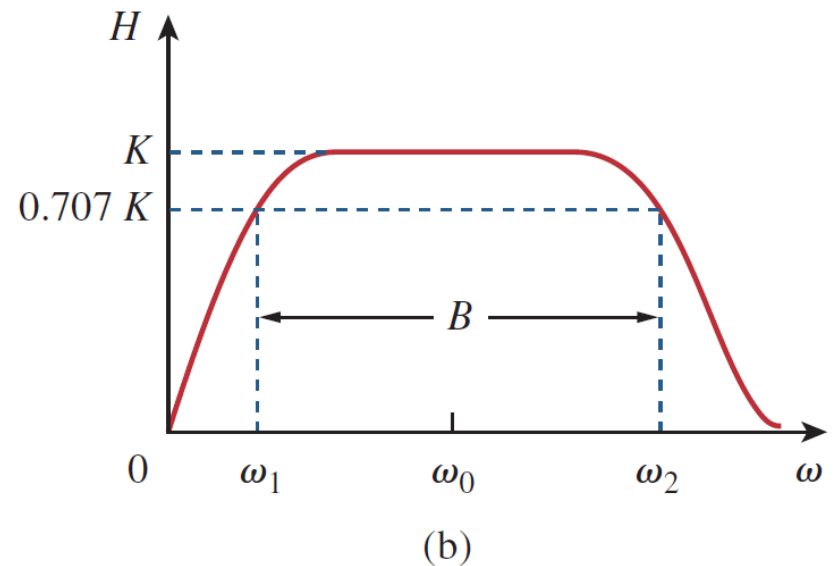


The *passband gain* K is

$$K = |H(j\underline{\omega_0})|$$

$$= \left| -\frac{R_f}{R_i} \frac{j\omega_0 / \omega_1}{(1 + j\omega_0 / \omega_1)(1 + j\omega_0 / \omega_2)} \right|$$


$$= \frac{R_f}{R_i} \frac{\omega_0 / \omega_1}{\sqrt{1 + (\omega_0 / \omega_1)^2} \sqrt{1 + (\omega_0 / \omega_2)^2}}$$
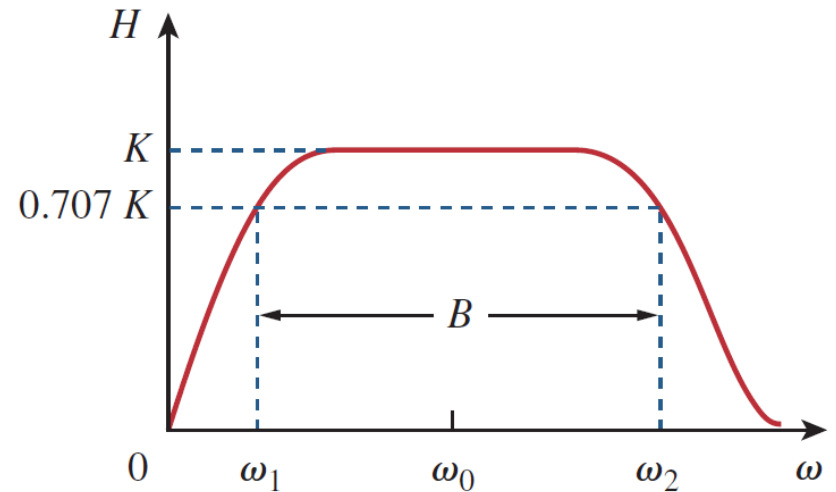
$$= \frac{R_f}{R_i} \frac{\sqrt{\omega_2 / \omega_1}}{\sqrt{1 + \omega_2 / \omega_1} \sqrt{1 + \omega_1 / \omega_2}} = \frac{R_f}{R_i} \frac{\omega_2}{\omega_1 + \omega_2}$$



(b)

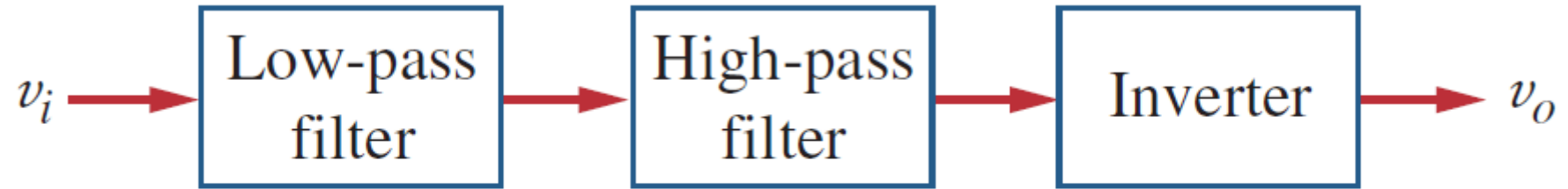$\times \omega_1 \omega_2$ on both numerator and denominator



(a)



Bandreject Filter A bandreject filter can be constructed by parallel combination of a lowpass filter and a highpass filter and an adder, as shown in Fig. 14.46(a). The frequency response is shown in Fig. 14.46(b).

Question : Why?

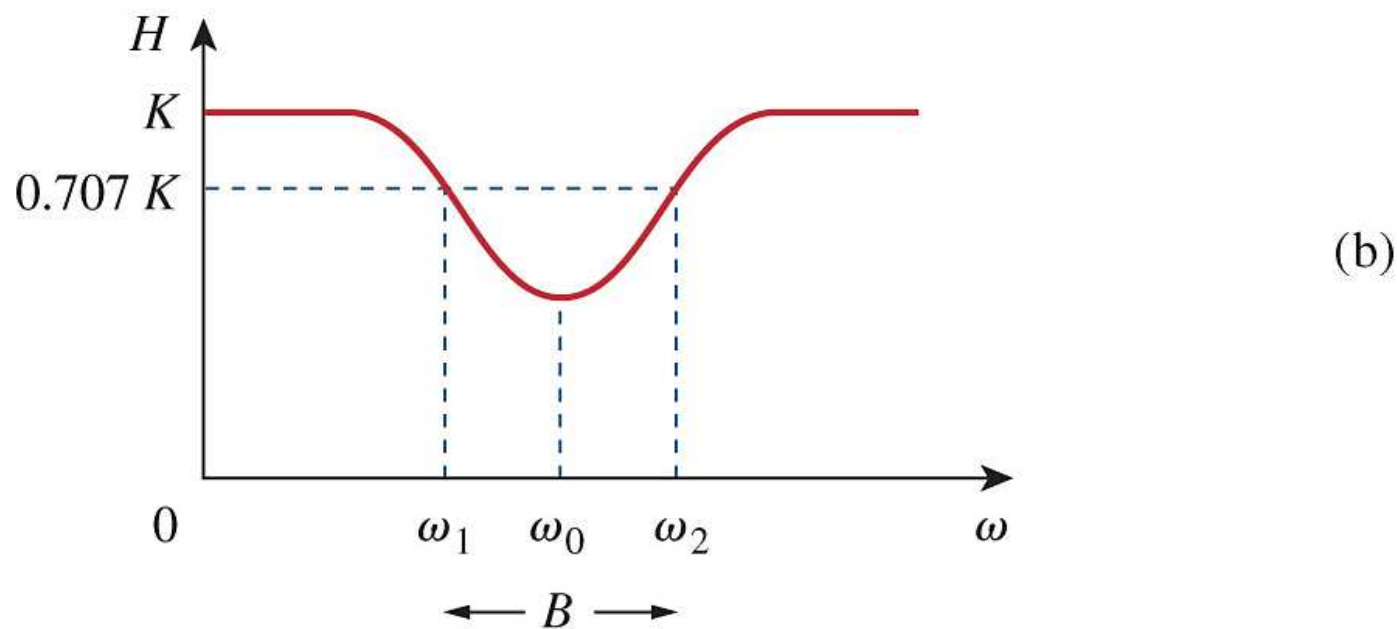
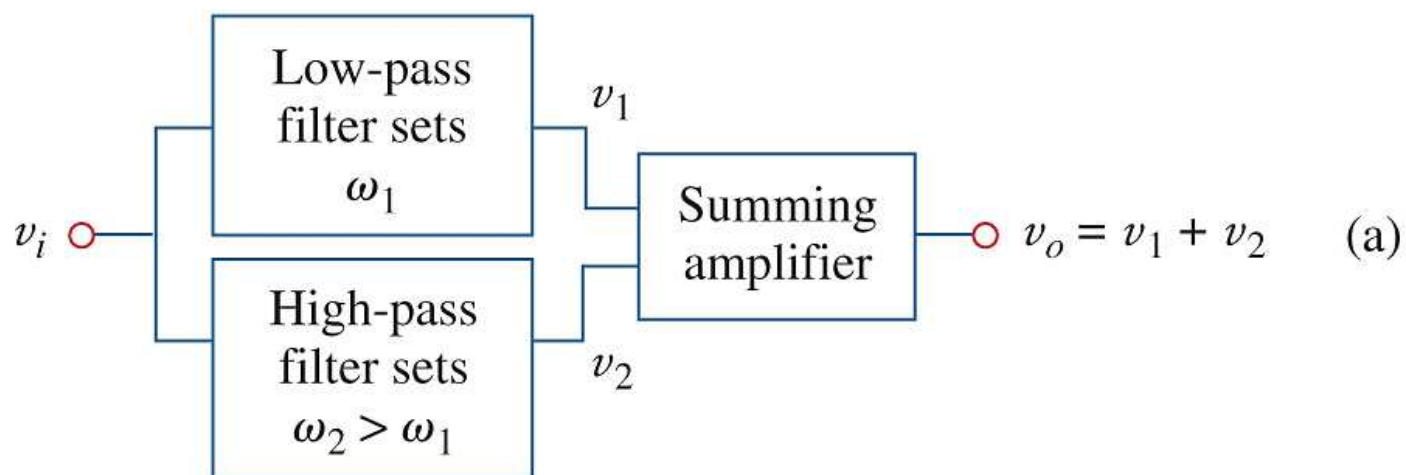


Figure 14.46 Active bandreject filter: (a) block diagram, (b) frequency response.

The actual construction of the bandreject filter is shown in Fig. 14.46. Its frequency response is

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$$

$$= \frac{R_f}{R_i} \left(\frac{1}{1 + j\omega RC_1} + \frac{j\omega RC_2}{1 + j\omega RC_2} \right)$$

Let

$$\omega_1 = 1 / (RC_1), \omega_2 = 1 / (RC_2).$$

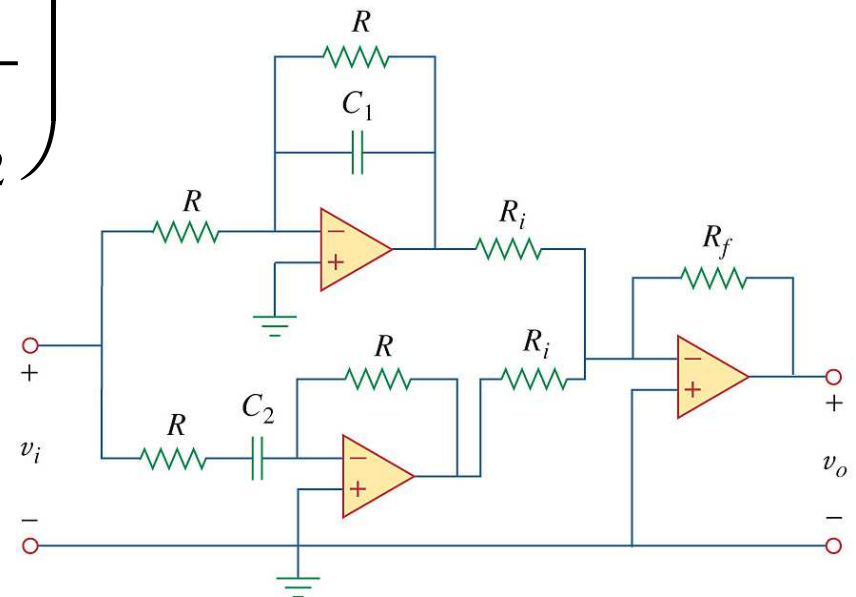


Figure 14.47 Active bandreject filter.


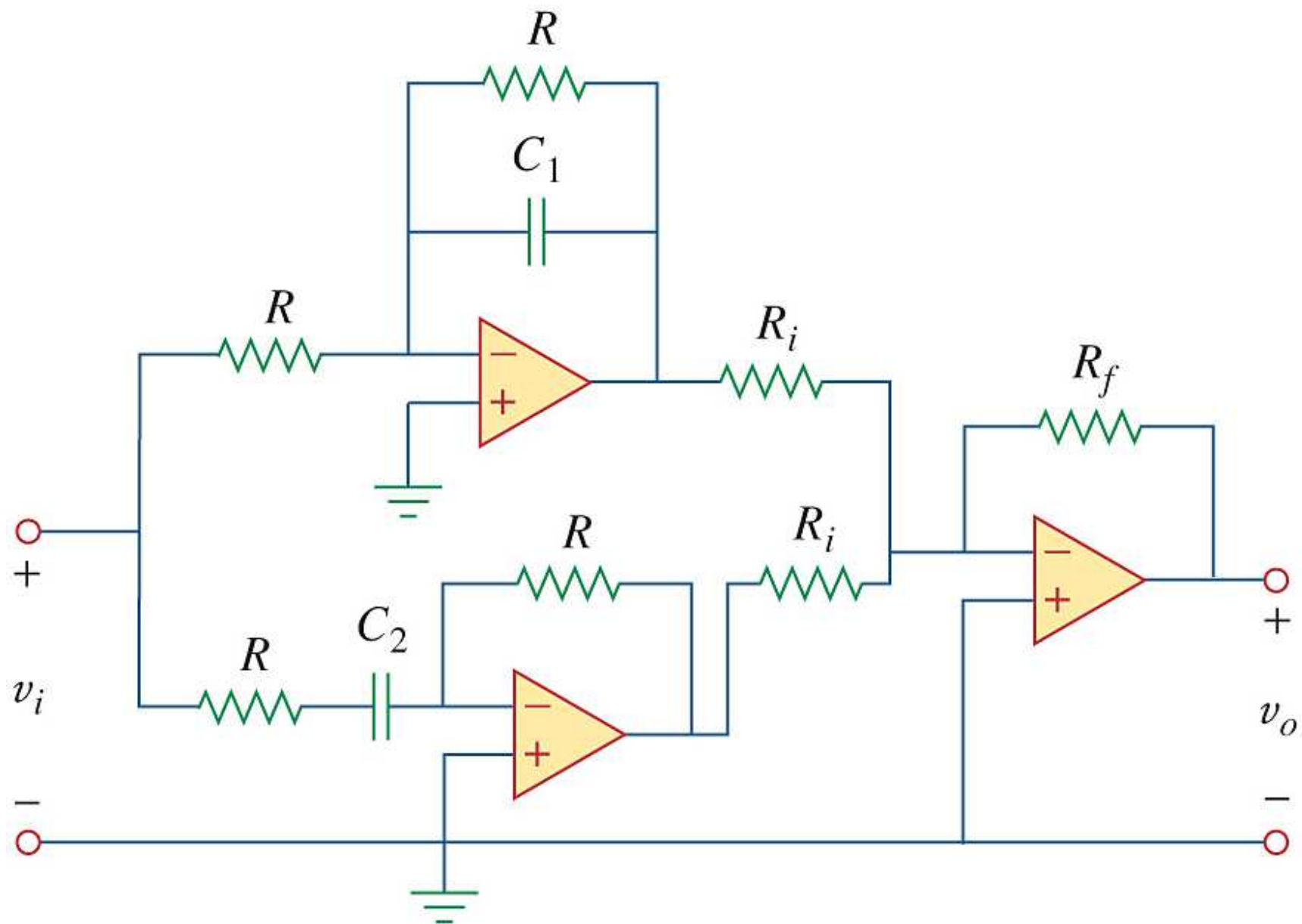


Figure 14.47 Active bandreject filter.

$$\begin{aligned}
 H(j\omega) &= \frac{R_f}{R_i} \left(\frac{1}{1 + j\omega / \omega_1} + \frac{j\omega / \omega_2}{1 + j\omega / \omega_2} \right) \\
 &= \frac{R_f}{R_i} \frac{1 + 2(j\omega) / \omega_2 + (j\omega)^2 / (\omega_1 \omega_2)}{(1 + j\omega / \omega_1)(1 + j\omega / \omega_2)} \\
 &= K \frac{1 + 2\zeta(j\omega) / \omega_0 + (j\omega / \omega_0)^2}{(1 + j\omega / \omega_1)(1 + j\omega / \omega_2)} \\
 K &= \frac{R_f}{R_i}, \omega_0 = \sqrt{\omega_1 \omega_2}, \zeta = \sqrt{\frac{\omega_1}{\omega_2}}
 \end{aligned}$$

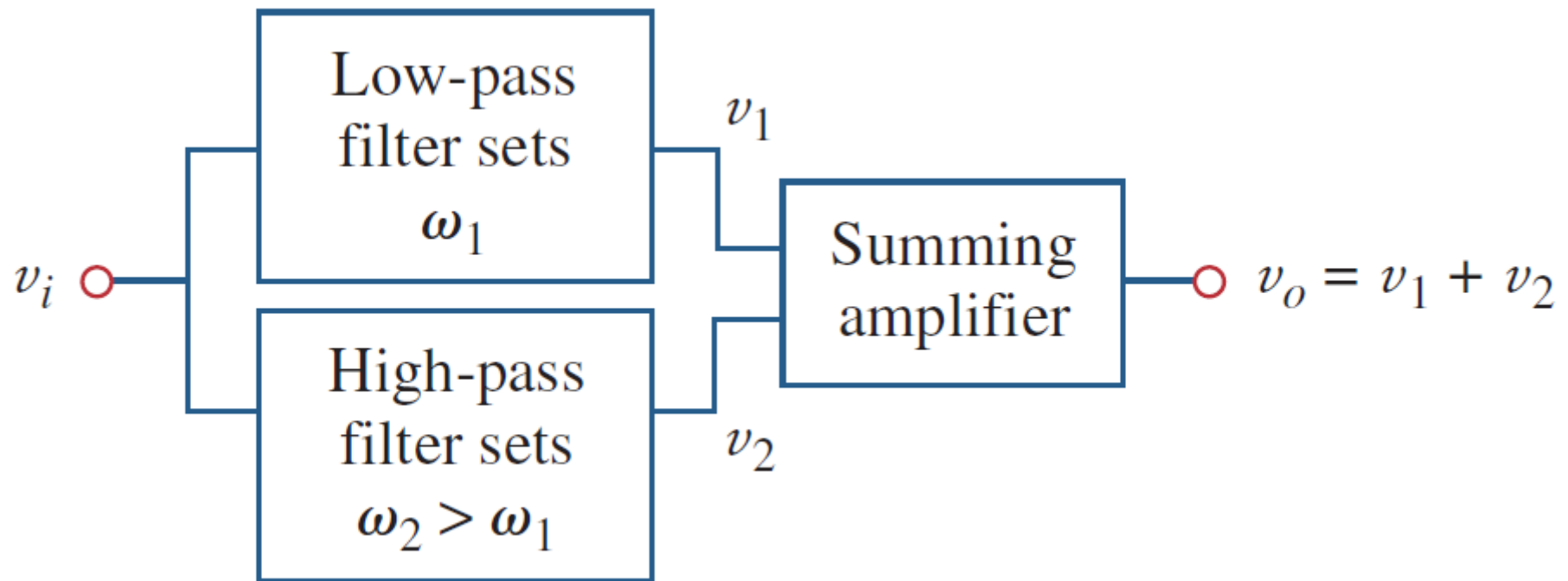Question : What is the magnitude Bode plot?



Why not cascading?

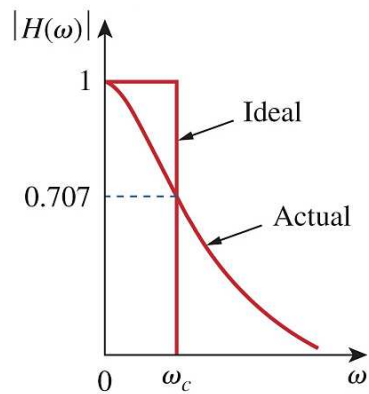


Figure 14.32 Ideal and actual frequency response of a lowpass filter.


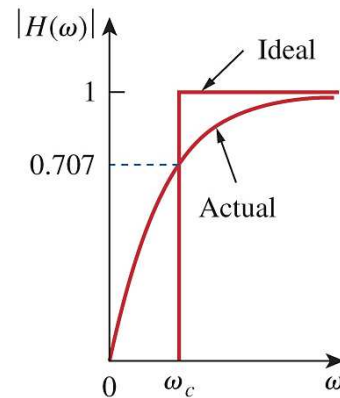


Figure 14.34 Ideal and actual frequency response of a highpass filter.

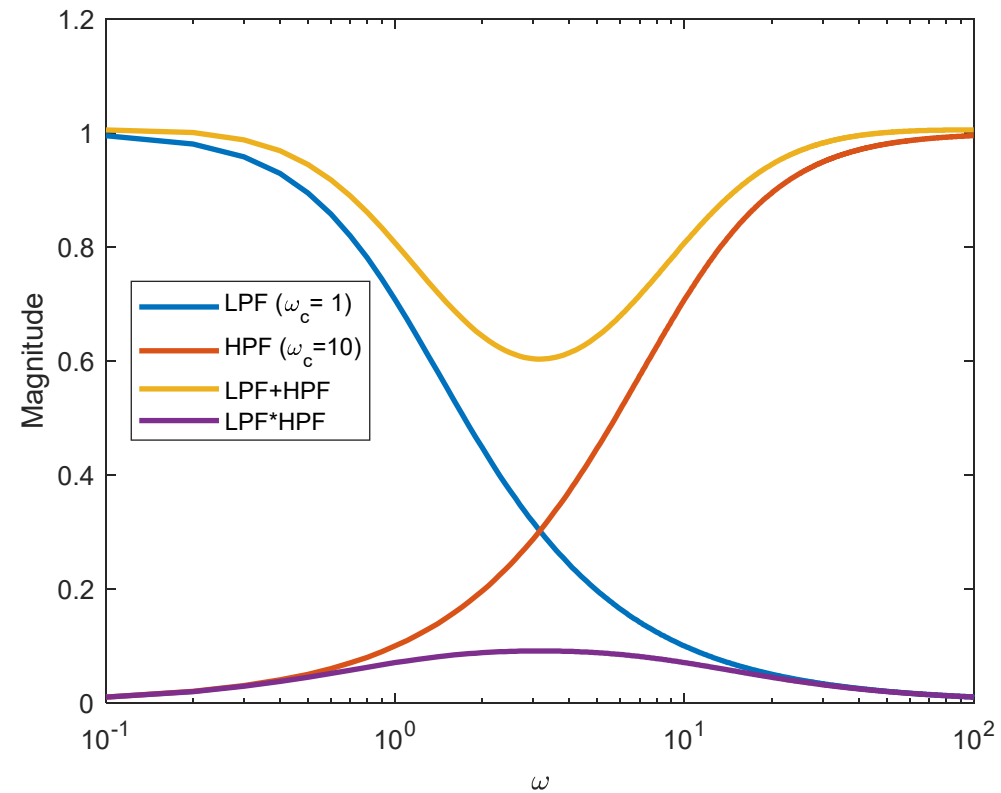

Parallel and series connection



Example 14.13 Design a bandpass filter in the form of Fig. 14.45 to pass frequencies between 250 Hz and 3,000 Hz and with $K = 10$. Select $R = 20 \text{ k}\Omega$.

Solution :

$$\omega_1 = 2\pi f_1 = 2\pi \times 250 = 500\pi \text{ (rad/s)}$$

$$\omega_2 = 2\pi f_2 = 2\pi \times 3,000 = 6,000\pi \text{ (rad/s)}$$


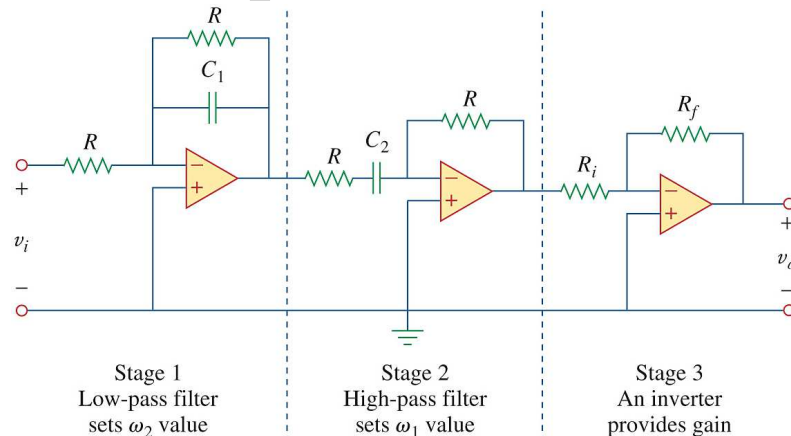


Figure 14.45 Active bandpass filter.

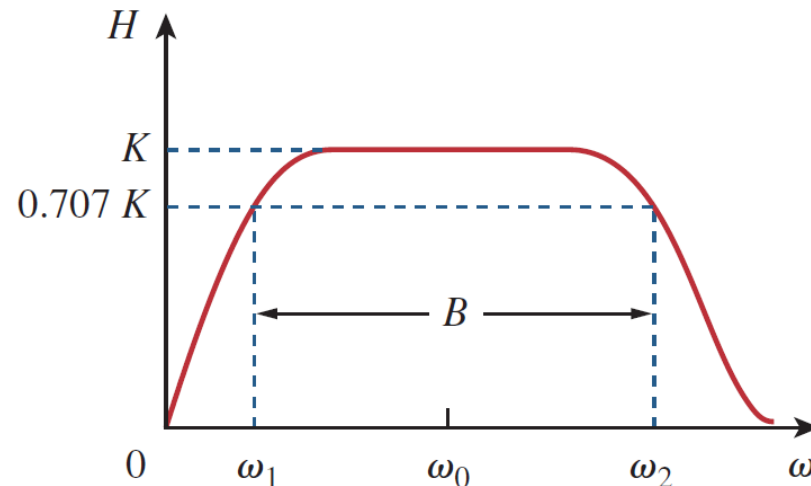

$$H(j\omega) = -\frac{R_f}{R_i} \frac{j\omega / \omega_1}{(1 + j\omega / \omega_1)(1 + j\omega / \omega_2)}$$

$$\omega_2 = 1 / (RC_1)$$

$$\omega_1 = 1 / (RC_2)$$

$$\omega_1 = \frac{1}{RC_2} \Rightarrow C_2 = \frac{1}{\omega_1 R} = \frac{1}{500\pi \times 20 \times 10^3}$$

$$\approx 3.1831 \times 10^{-8} \text{ (F)} \approx 31.83 \text{ nF}$$

$$\omega_2 = \frac{1}{RC_1} \Rightarrow C_1 = \frac{1}{\omega_2 R} = \frac{1}{6,000\pi \times 20 \times 10^3}$$

$$\approx 2.6526 \times 10^{-9} \text{ (F)} \approx 2.65 \text{ nF}$$

$$K = |H(j\omega_0)| = \frac{R_f}{R_i} \frac{\omega_2}{\omega_1 + \omega_2}$$

$$K = \frac{R_f}{R_i} \frac{\omega_2}{\omega_1 + \omega_2} \Rightarrow \frac{R_f}{R_i} = K \frac{\omega_1 + \omega_2}{\omega_2}$$
$$= 10 \times \frac{500\pi + 6,000\pi}{6,000\pi} \approx 10.8333$$

If we select $R_i = 10 \text{ k}\Omega$, then $R_f \approx 108.3 \text{ k}\Omega$.

Application – AM Radio

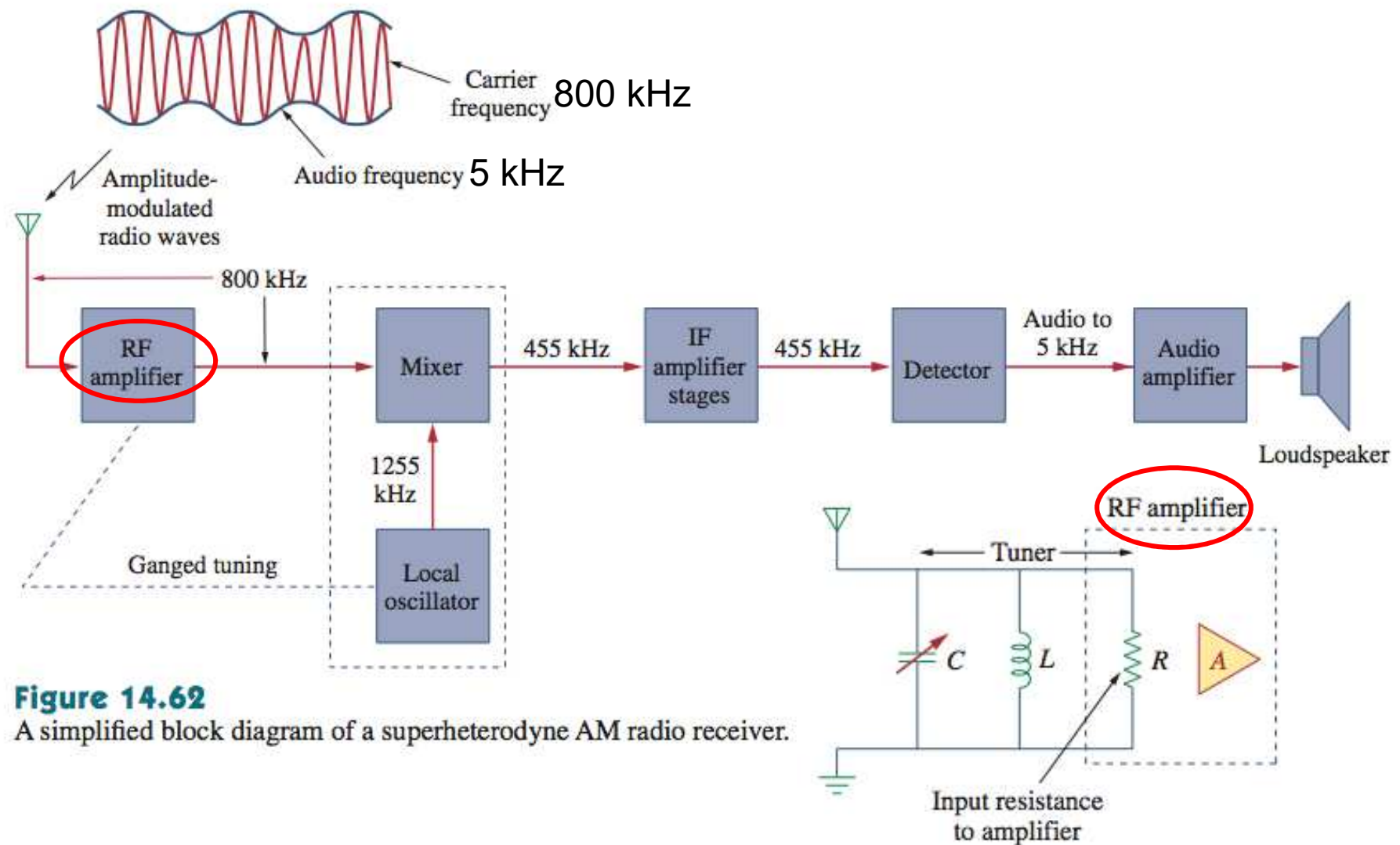


Figure 14.62

A simplified block diagram of a superheterodyne AM radio receiver.